

Digital System Design

Lecture 12

Combinational Logic Design

Binary Adder-Subtractor

Objectives:

1. Half Adder.
2. Full Adder.
3. Binary Adder.
4. Binary Subtractor.
5. Binary Adder-Subtractor.

1. Half Adder

Half Adder: is a combinational circuit that performs the addition of two bits, this circuit needs two binary inputs and two binary outputs.

| Inputs | | Outputs | |
|--------|---|---------|---|
| X | Y | C | S |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |



Truth table

The simplified Boolean function from the truth table:

$$\left. \begin{aligned} S &= \bar{X}Y + X\bar{Y} \\ C &= XY \end{aligned} \right\} \text{(Using sum of product form)}$$

Where **S** is the sum and **C** is the carry.
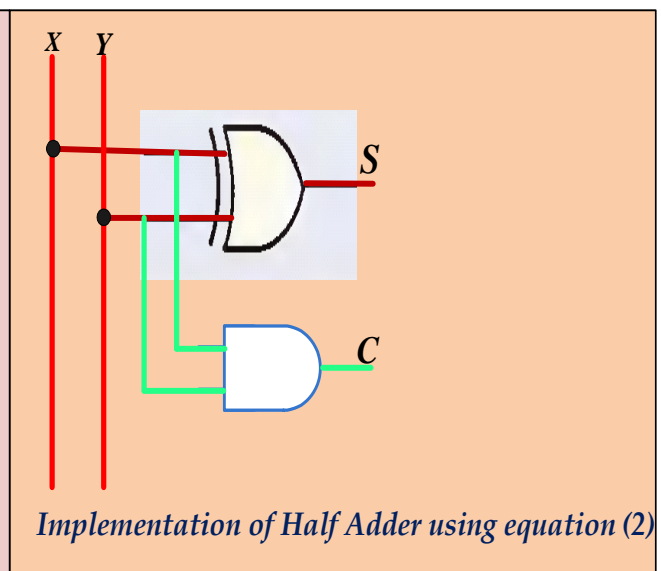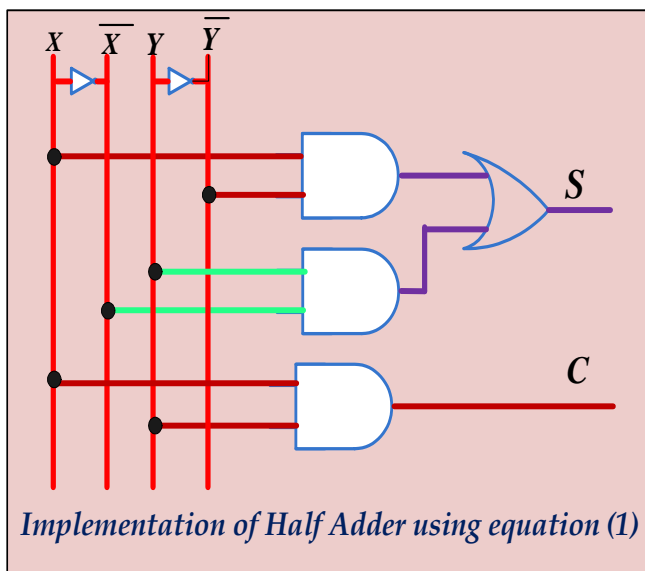
$$\left. \begin{aligned} S &= X \oplus Y \\ C &= XY \end{aligned} \right\} \text{(Using XOR and AND Gates)}$$



- The implementation of half adder using **exclusive-OR** and an **AND** gates is used to show that two half adders can be used to construct a full adder.
- The inputs to the **XOR** gate are also the inputs to the **AND** gate.

2. Full Adder

Full Adder is a combinational circuit that performs the addition of three bits (two significant bits and previous carry).

- It consists of **three inputs and two outputs**, two inputs are the bits to be added, the third input represents the carry from the previous position.
- The full adder is usually a component in a cascade of adders, which add 8, 16, etc, binary numbers.

| Inputs | | | Outputs | |
|----------|----------|-----------------------|----------|------------------------|
| <i>X</i> | <i>Y</i> | <i>C_{in}</i> | <i>S</i> | <i>C_{out}</i> |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

Truth table for the full adder

➤ The **S** output is equal to **1** when only one input is equal to **1** or when all three inputs are equal to **1**.

➤ The **C_{out}** output has a carry **1** if two or three inputs are equal to **1**.

➤ The Karnaugh maps and the simplified expression are shown in the following figures:

| | | | | |
|---|----|----|----|----|
| <i>X</i> \ <i>Y</i> <i>C_{in}</i> | 00 | 01 | 11 | 10 |
| 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |


$$S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C_{in}} + X\overline{Y}\overline{C_{in}} + XYC_{in}$$

| | | | | |
|---|----|----|----|----|
| <i>X</i> \ <i>Y</i> <i>C_{in}</i> | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 |

$$C_{out} = XY + XC_{in} + YC_{in}$$

$$\left. \begin{cases} S = \overline{X}\overline{Y}C_{in} + \overline{X}Y\overline{C_{in}} + X\overline{Y}\overline{C_{in}} + XYC_{in} \\ C_{out} = XY + XC_{in} + YC_{in} \end{cases} \right\} \mathbf{1} \text{ (Sum of products)}$$

 - The *logic diagrams* for the full adder implemented in *sum-of-products* form are the following:



- It can also be implemented using *two half adders* and *one OR gate* (using **XOR** gates).

$$\left\{ \begin{array}{l} S = C_{in} \oplus (X \oplus Y) \\ C_{out} = C_{in} \cdot (X \oplus Y) + XY \end{array} \right\}$$


Proof:

The sum:

$$\begin{aligned} S &= \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}\bar{C}_{in} + XYC_{in} \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\bar{X}\bar{Y} + XY) \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\overline{\bar{X}Y + X\bar{Y}}) \\ S &= C_{in} \oplus (X \oplus Y) \end{aligned}$$


The carry output:
 
$$\begin{aligned} C_{out} &= \bar{X}Y C_{in} + X\bar{Y} C_{in} + XY C_{in} + XY \bar{C}_{in} \\ &= C_{in}(\bar{X}Y + X\bar{Y}) + XY(C_{in} + \bar{C}_{in}) \\ C_{out} &= C_{in} \cdot (X \oplus Y) + XY \end{aligned}$$



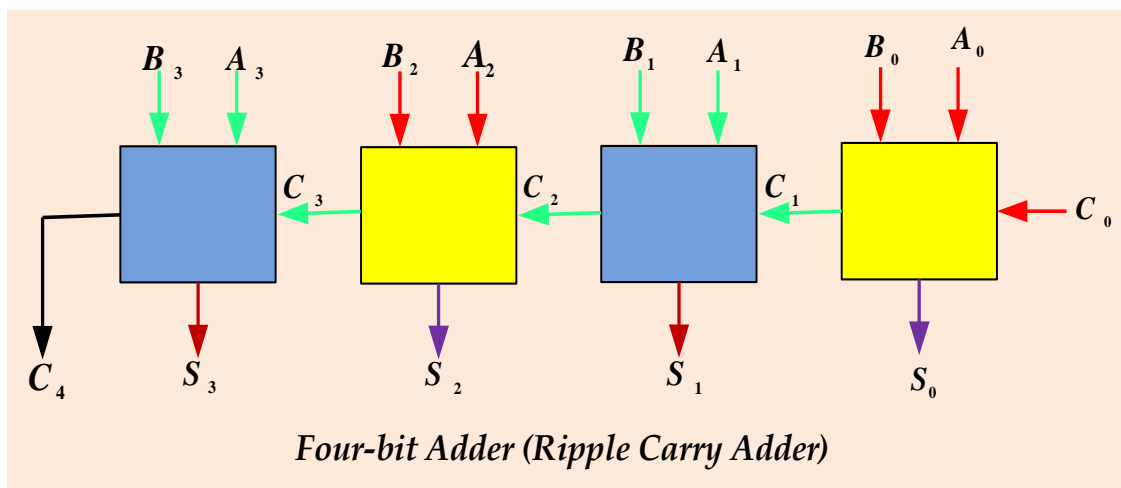3. Binary Adder (Asynchronous Ripple-Carry Adder)

- A binary adder is a digital circuit that produces the *arithmetic sum of two binary numbers*.
- A binary adder can be constructed with *full adders connected in cascade* with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- The *four-bit adder* is a typical example of a *standard component*. It can be used in many application involving arithmetic operations.



- The input carry to the adder is C_0 and it ripples through the full adders to the output carry C_4 .
- n -bit binary adder requires n full adders.

Example:


$A + B$ (A = 1011) and (B = 0011)

| Subscript i | 3 | 2 | 1 | 0 | |
|---------------|---|---|---|---|-----------|
| Input Carry | 0 | 1 | 1 | 0 | C_i |
| A | 1 | 0 | 1 | 1 | A_i |
| + | | | | | |
| B | 0 | 0 | 1 | 1 | B_i |
| Sum | 1 | 1 | 1 | 0 | S_i |
| Output Carry | 0 | 0 | 1 | 1 | C_{i+1} |

$C_0 = 0$

Carry Propagation

- The addition of $A + B$ binary numbers in *parallel* implies that all the bits of A and B are available for computation at the same time.
- As in any combinational circuit, the signal must **propagate** through the gates before the correct output sum is available.
- The output will not be correct unless the signals are given enough time to propagate through the gates connected from the input to the output.
- The longest **propagation delay time** in an adder is the time it takes the carry to propagate through the full adders.

 

- The signal from the carry input C_i to the output carry C_{i+1} propagates through an **AND** gate and an **OR** gate, which equals **2 gate levels**.
 - If there are **4** full adders in the binary adder, the output carry C_4 would have **$2 \times 4 = 8$ gate levels**, from C_0 to C_4
 - For an n -bit adder, **$2n$ gate levels** for the carry to propagate from input to output are required.

- The **carry propagation time** is an important attribute of the adder because it limits the speed with which two numbers are added.
- To reduce the carry propagation delay time:
 - 1) **Employ faster gates with reduced delays.**
 - 2) **Employ the principle of Carry Lookahead Logic.**

Proof: (using carry lookahead logic)

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

The output sum and carry are:

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$


- ✓ G_i -called a **carry generate**, and it produces a carry of **1** when both A_i and B_i are **1**.
- ✓ P_i -called a **carry propagate**, it determines whether a carry into stage i will propagate into stage $i + 1$.
- ✓ The **Boolean function** for the carry outputs of each stage and substitute the value of each C_i from the previous equations:

$$\left. \begin{array}{l} C_0 = \text{input carry} \\ C_1 = G_0 + P_0 C_0 \\ C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) \\ \quad = G_1 + P_1 G_0 + P_1 P_0 C_0 \\ C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ \quad = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{array} \right\}$$


- The three Boolean functions C_1 , C_2 and C_3 are implemented in the **carry lookahead generator**.

The two level-circuit for the output carry C_4 is not shown, it can be easily derived by the equation.

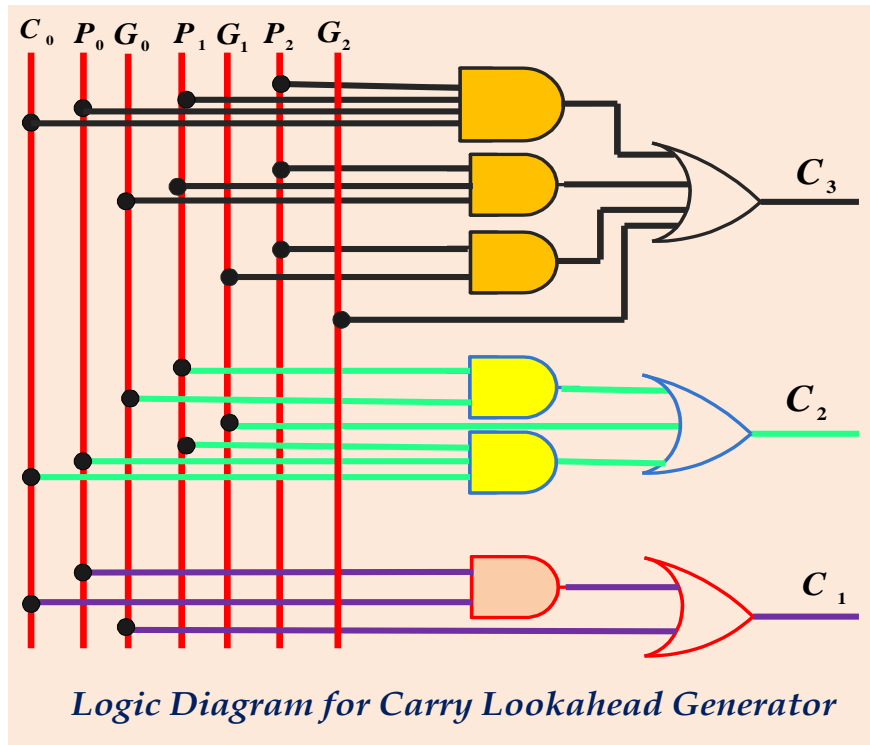- C_3 does not have to wait for C_2 and C_1 to propagate, in fact C_3 is propagated at the same time as C_1 and C_2 .



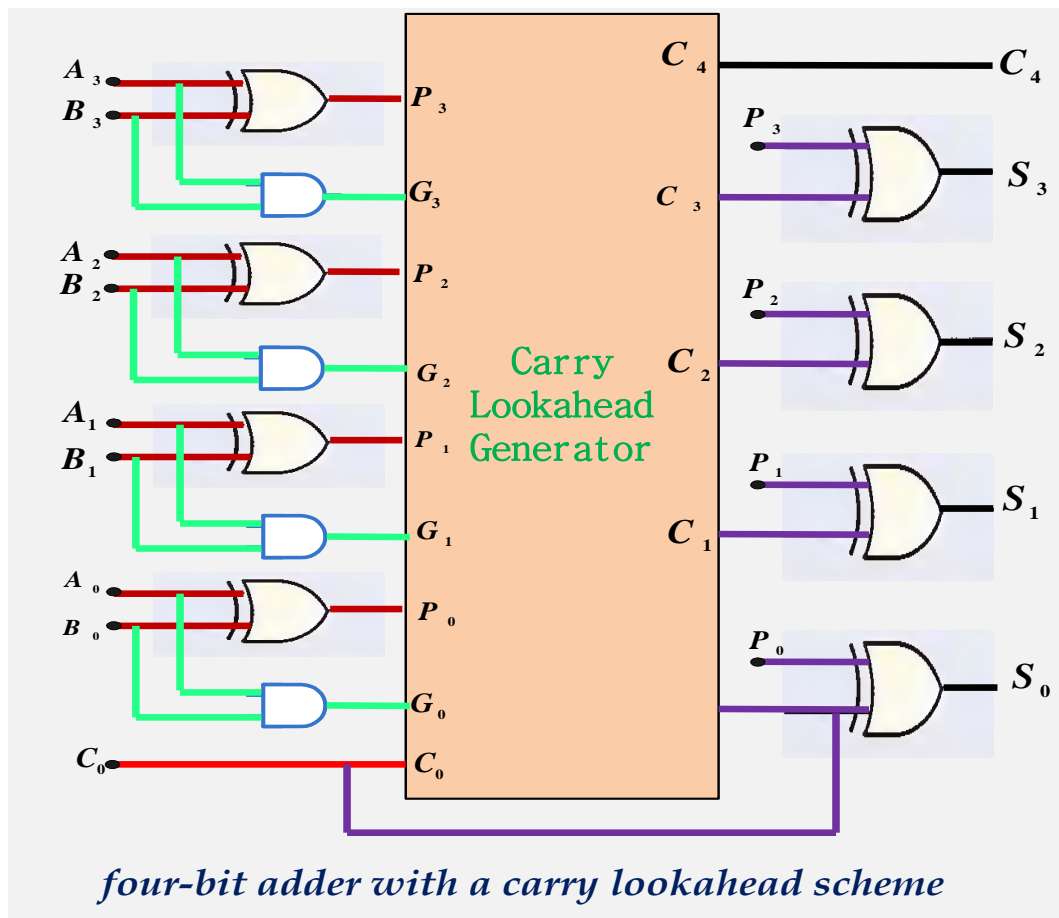- The construction of a *four-bit adder with a carry lookahead scheme* is the following:




4. Binary Subtractor

- To perform the subtraction $-B$, we can use the **2's complements**, so the subtraction can be converted to addition.
- **2's complement** can be obtained by taking the **1's complement** and adding **1** to the **LSD** bit.
 - 1) **1's complement** can be implemented with inverters.
 - 2) **1** can be added to the sum through the input carry.
- The circuit for subtracting $A - B$ consists of an adder with inverters placed between each data input B and the corresponding input of the full adder. The input carry C_0 must be equal to **1**.

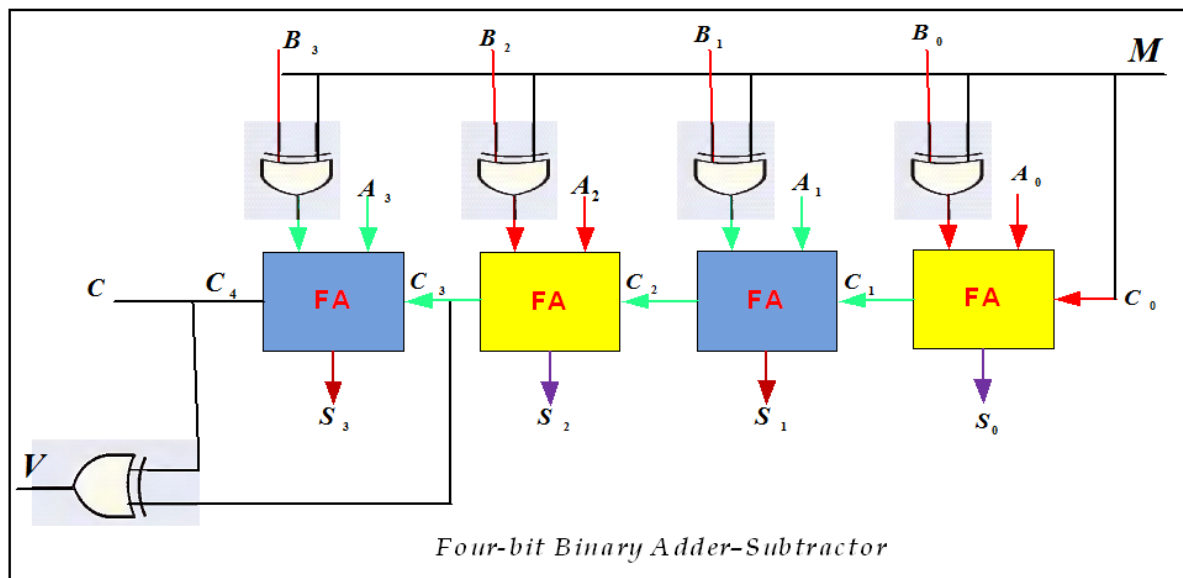5. Binary Adder-Subtractor

- The addition and subtraction operations can be combined into one circuit with one common binary adder by including an **exclusive-OR** gate with each full-adder.



The mode input M controls the operation as the following:

- ($M = 0$) → adder.
- ($M = 1$) → subtractor.
- Each **XOR** gate receives M signal and B
 - When $M = 0$ then $B \oplus 0 = B$ and the carry = **0**, then the circuit performs the operation $A + B$.
 - When $M = 1$ then $B \oplus 1 = \bar{B}$ and the carry = **1**, then the circuit performs the operation $A - B$.
- The **exclusive-OR** with output V is for detecting an overflow.