

# Digital System Design

## Lecture 13

### Combinational Logic Design

### Binary Multipliers and Decoders

#### Objectives:

#### 1. Multipliers:

- 1.1 Multiplication of two 2-bit numbers.
- 1.2 Combinational circuit of binary multiplier with more bits.


#### 2. Decoders:

- 2.1) 2x4 decoder (Active-high).
- 2.2) Active-low decoders.
- 2.3) Decoders with enable inputs.
- 2.4) Three-to-eight-line decoder circuit.
- 2.5) Larger decoder circuit.
- 2.6) Combinational logic implementation.

#### 1) Multipliers:


➤ Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers:
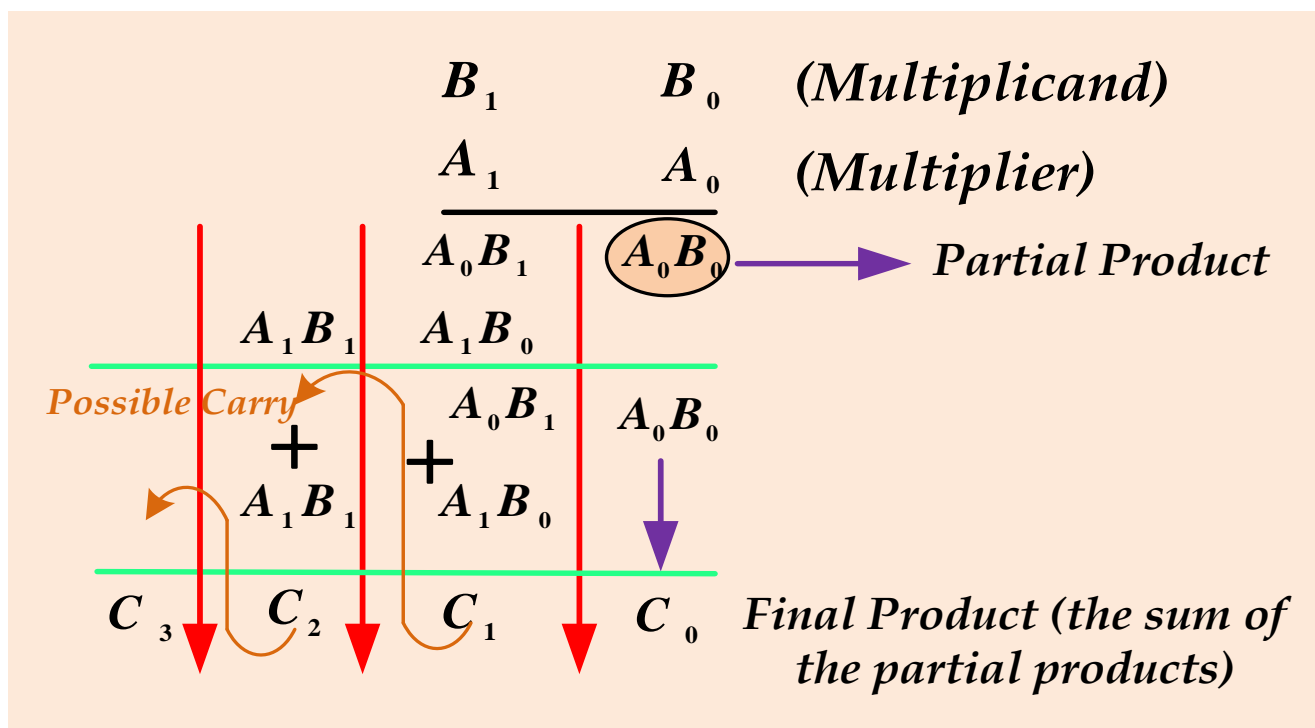
#### 1.1 Multiplication of two 2-bit numbers.


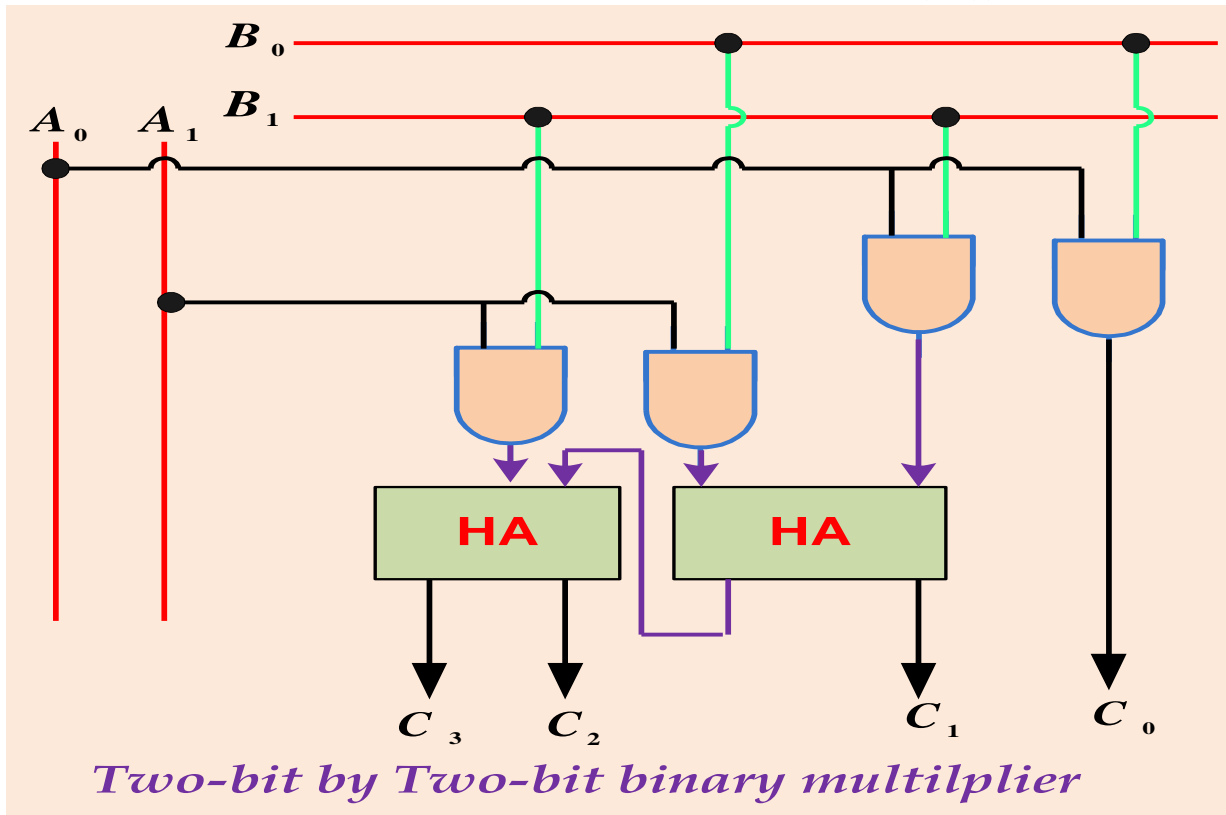
## Combinational circuit

- The multiplication of two bits such as  $A_0$  and  $B_0$  produces a  $1$  if both bits are  $1$ ; otherwise, it produces a  $0$ , this is identical to an **AND** operation.
- The two partial products are added with two half-adder (**HA**) circuits (if there are more than two bits, we must use full adder (**FA**)).



### 1.2 Combinational circuit of binary multiplier with more bits.

- For  $J$  bits *multiplier* and  $K$  bits *multiplicand*, we need:
  - $J \times K$  **AND** gates.
  - $(J - 1)K$ -bits adders to produce a product of  $J + K$  bits.

**Example:** - Create a logic circuit for

$$\begin{array}{r}
 B_3 \ B_2 \ B_1 \ B_0 \\
 \times \\
 A_2 \ A_1 \ A_0 \\
 \hline
 C_6 \ C_5 \ C_4 \ C_3 \ C_2 \ C_1 \ C_0 \ \text{Answer}
 \end{array}$$


**Solution:**

$$K = 4$$


$$J = 3$$

 **So:**

We need **12 AND** gates and **2 four-bit adders** to produce a product of **seven bits**:  $C_6C_5C_4C_3C_2C_1C_0$ .




**Circuit Implementation:**

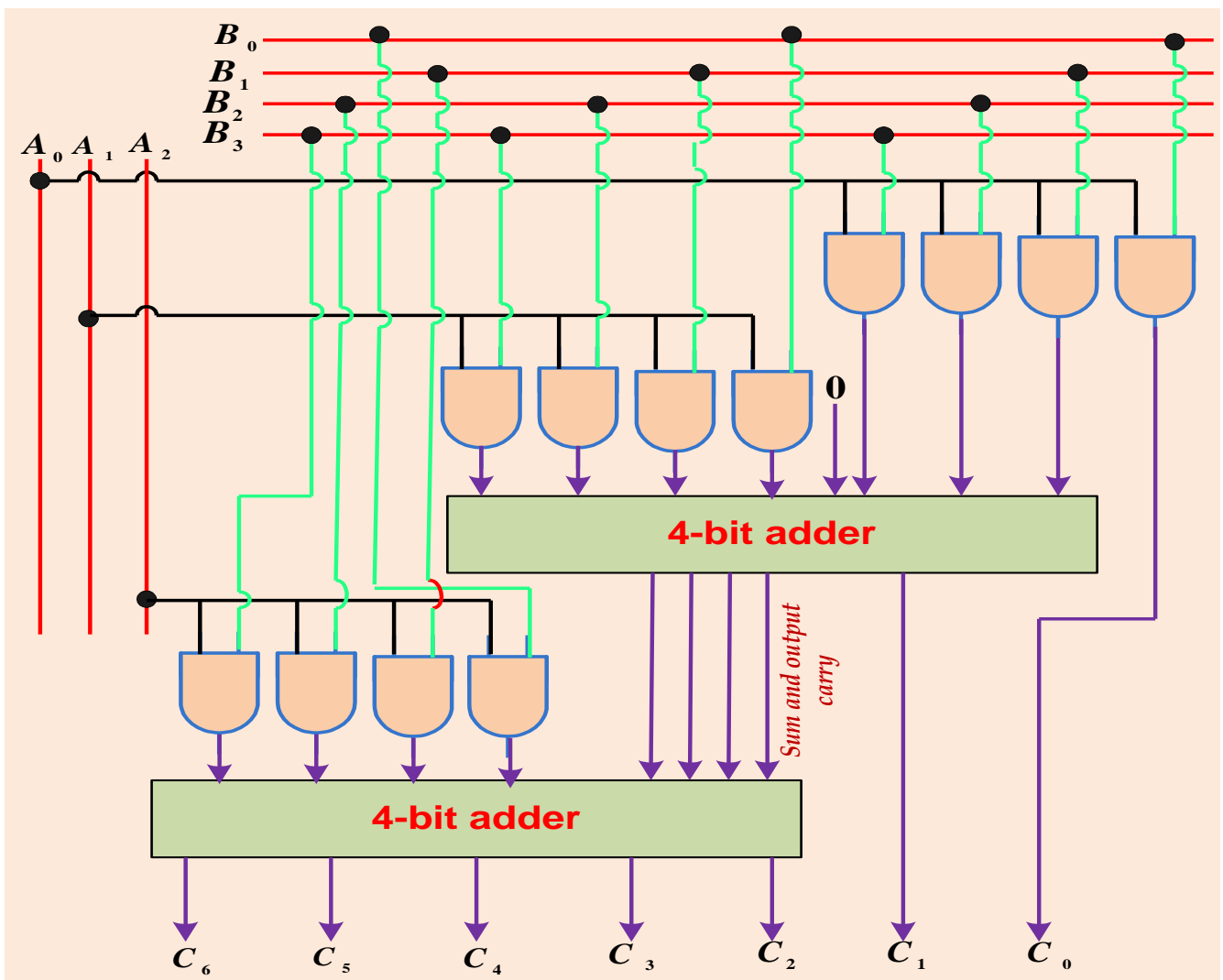

## 2) Decoders

- Information is represented in digital system by binary codes. A binary code of  $n$  bits is capable of representing up to  $2^n$  distinct elements of coded information.
- A **decoder** is a combinational circuit that covers binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.
- The decoders are called  $n$  – to –  $m$  line decoders, where  $m \leq 2^n$  (for example **BCD-to-seven-segment decoder**, **3 – to – 8** decoder).
- The purpose of the decoders is to **generate** the  $2^n$  (or fewer) minterms of  $n$  input variables.
- Decoder is a circuit that allows us to **activate an output line by specifying a control word**; it is either active-high or active-low.
  - **Active-high** sets a particular output to logic **1**. While remaining other outputs to logic **0**.
  - **Active-low** sets a particular output to logic **0**, other outputs to logic **1**.

### 2.1) 2x4 decoder (Active-high)

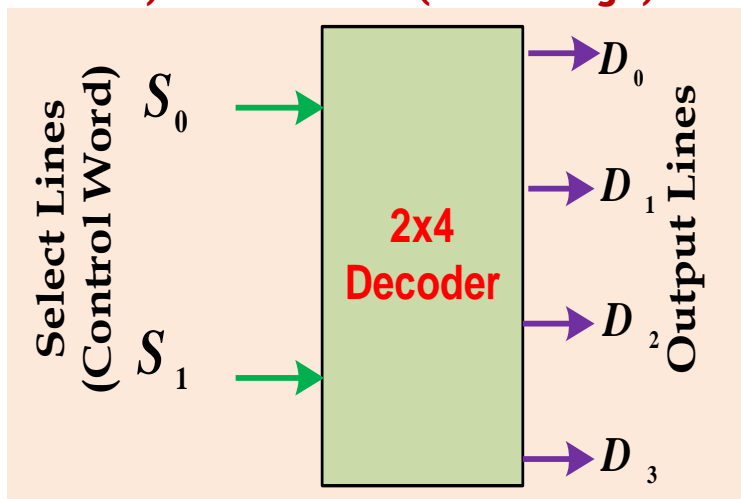


1.  $S_1 = 0, S_0 = 0 \Rightarrow D_0 = 1$   
 $D_0 = \overline{S_1} \cdot \overline{S_0}; D_1 = D_2 = D_3 = 0$
2.  $S_1 = 0, S_0 = 1 \Rightarrow D_1 = 1$   
 $D_1 = \overline{S_1} \cdot S_0; D_0 = D_2 = D_3 = 0$
3.  $S_1 = 1, S_0 = 0 \Rightarrow D_2 = 1$   
 $D_2 = S_1 \cdot \overline{S_0}; D_0 = D_1 = D_3 = 0$
4.  $S_1 = 1, S_0 = 1 \Rightarrow D_3 = 1$   
 $D_3 = S_1 \cdot S_0; D_0 = D_1 = D_2 = 0$


Inputs Select Lines		Output Output Lines			
$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Truth table

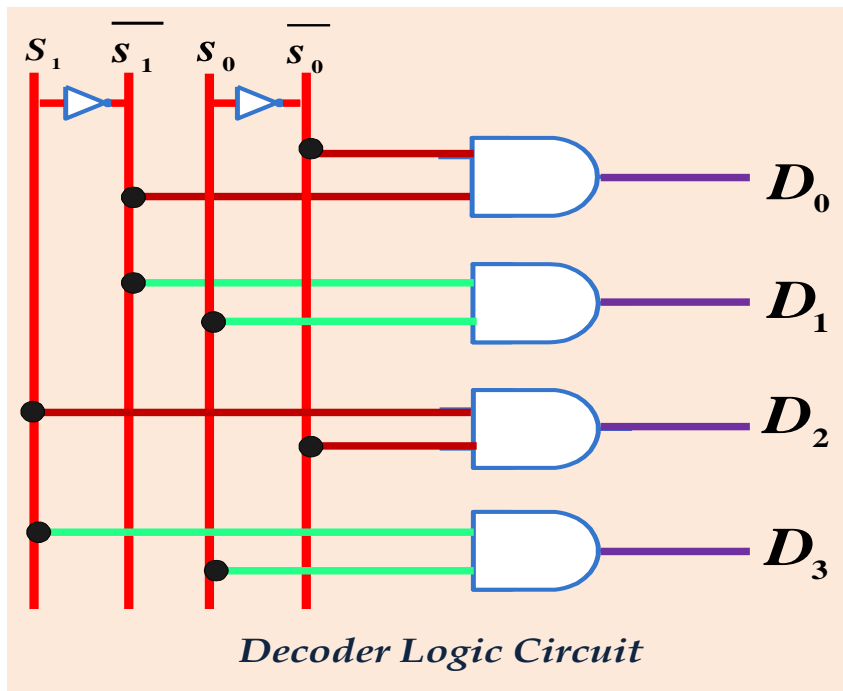- From truth table:
  - ✓ **Two inputs are decoded to 4 outputs.**
  - ✓ **Each output represents one of the minterms of the three input variables.**
  - ✓ **For each possible combination (input), there are 3 outputs that are equal to 0 and only one that is equal to 1.**



## 2.2) Active-low decoders

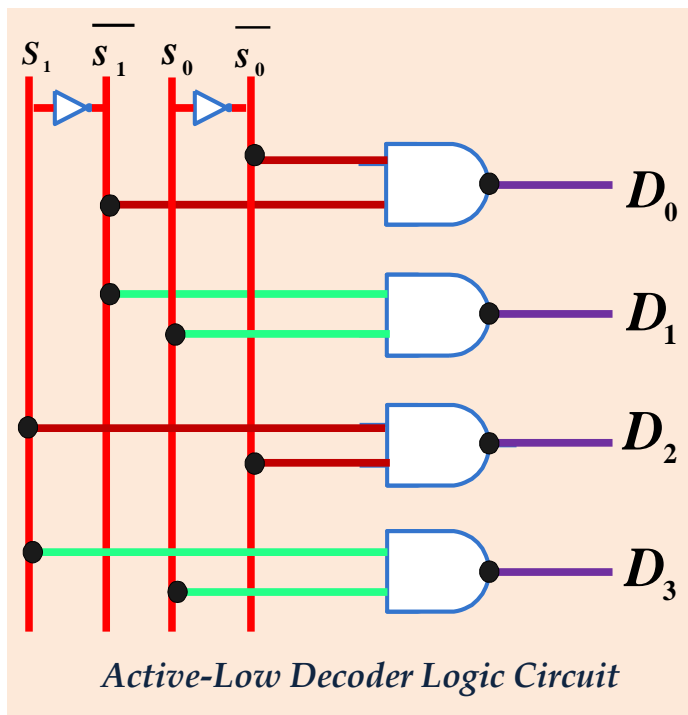

Inputs Select Lines		Output Output Lines			
$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

Truth table

### AND becomes NAND

$$D_0 = \overline{\overline{S_1} \cdot \overline{S_0}} \text{ Complement}$$


$$= S_1 + S_0$$

$$D_1 = \overline{\overline{S_1} \cdot S_0} = S_1 + \overline{S_0};$$

$$D_2 = \overline{S_1 + S_0};$$

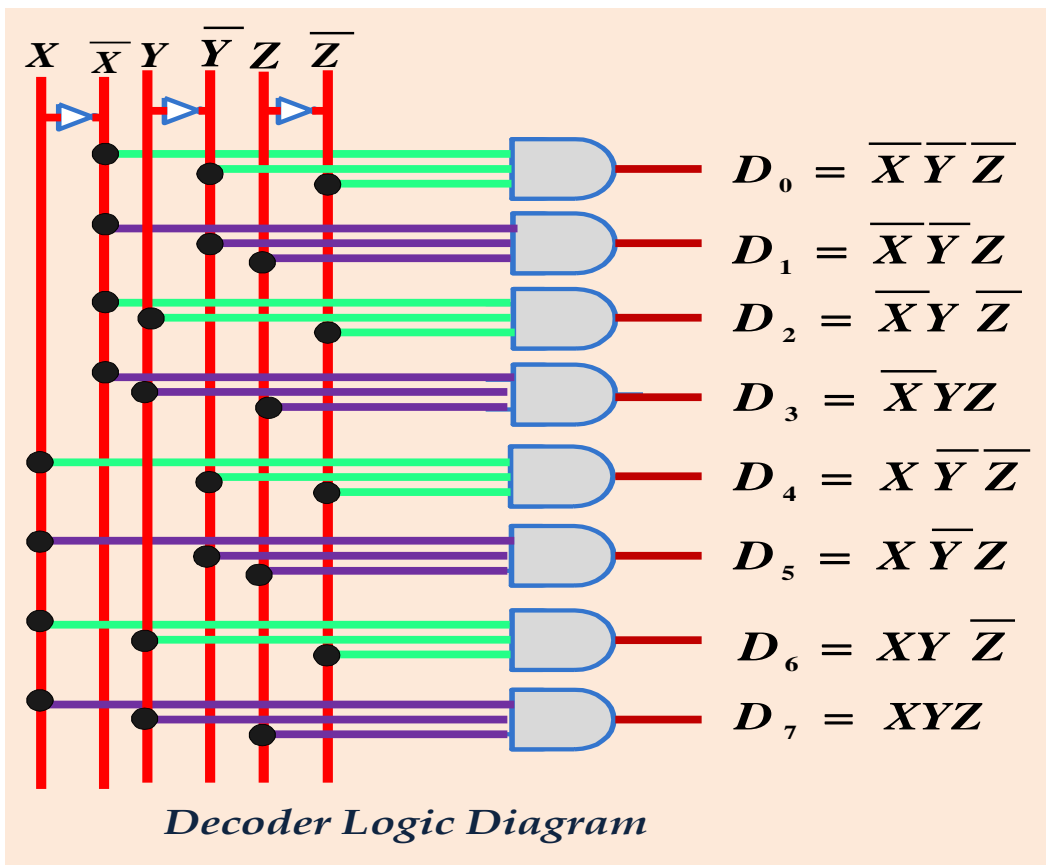
$$D_3 = \overline{S_1 + \overline{S_0}}$$





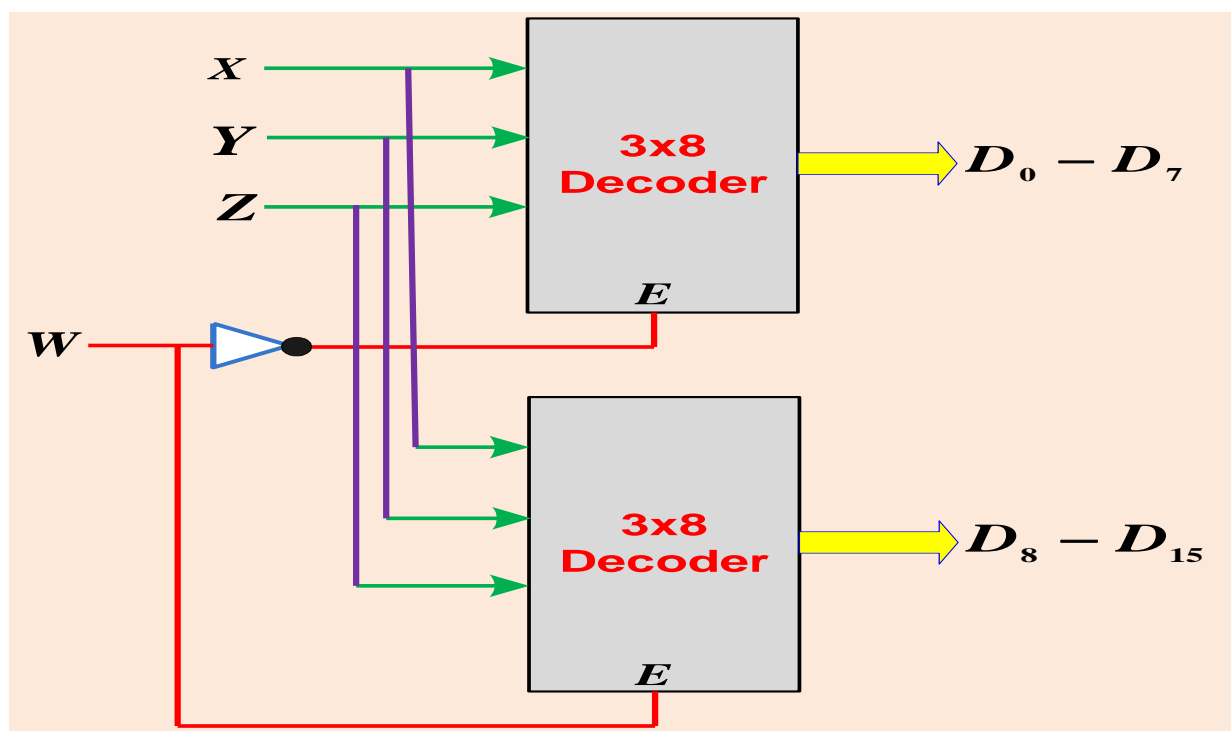**2.5) Larger decoder circuit.**

- Decoders with enable inputs can be connected together to form a larger decoder circuit.
- To design a 4 – to – 16 line decoder. Using two 3 – to – 8 decoders with enable inputs, we do the following connection:
  - ✓ When  $W = 0$  the top decoder is enable and the other is disable: The bottom decoder outputs are all 0's and the top eight outputs generate minterms 0000 to 0111.
  - ✓ When  $W = 1$  the enable condition is reversed, the bottom decoder outputs generate minterms 1000 to 1111.



## 2.6) Combinational logic implementation:

- Since, a decoder provides the  $2^n$  minterms of  $n$  input, and any Boolean function can be expressed in sum-of-minterms form, A decoder that generates the minterms of the functions, together with an **external OR gate** that forms their logical sum, provides a hardware implementation of the function.
- In this way, any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented using  $n$  - to -  $2^n$  **line decoder** and  $m$  **OR gates**.
- The **procedure** for implementing a combinational circuit by means of **decoders and OR gates** requires that the Boolean function for the circuit be **expressed as a sum of minterms**.

**Example:-Implementation a full-adder circuit using the decoders.**

- From the **truth table** of the full adder, we obtain the functions for the **sum** and **carry** in **sum-of-minterms** form:

$$S(X, Y, C_{in}) = \sum (1, 2, 4, 7)$$

$$C_{out}(X, Y, C_{in}) = \sum (3, 5, 6, 7)$$

- We have **3 inputs**: so, we need a **three-to-eight line decoder**.

