

Digital System Design

Lecture 14

Combinational Logic Design

Multiplexers, Demultiplexers and Encoders

Objectives:

1. Multiplexers:
 - a. 4-to-1 Multiplexers.
 - b. Design of 8:1 Multiplexers.
2. Demultiplexers.
3. Encoders.
4. Examples.


1. Multiplexers

- A Multiplexers (**MUX**) is a combinational logic component that has several inputs and only one output.
- **MUX** directs one of the inputs to its output line by using a control bit word (**selection line**) to its select lines.
- Multiplexer contains the followings:
 - 2^n data inputs
 - n selection inputs
 - a **single** output
 - Selection input determines the input that should be connected to the output.
- The multiplexer sometime is called data selector.
- The multiplexer acts like an electronic switch that selects one from different.
- A multiplexer may have an enable input to control the operation of the unit.

a) 4-to-1 Multiplexers


- ✓ 4-data input MUX
- ✓ s_1, s_0 - Select lines.
- ✓ p_0, p_2, p_3, p_1 - Input lines.
- ✓ F - Single output line.

Select lines		Output
S_1	S_0	F
0	0	P_0
0	1	P_1
1	0	P_2
1	1	P_3

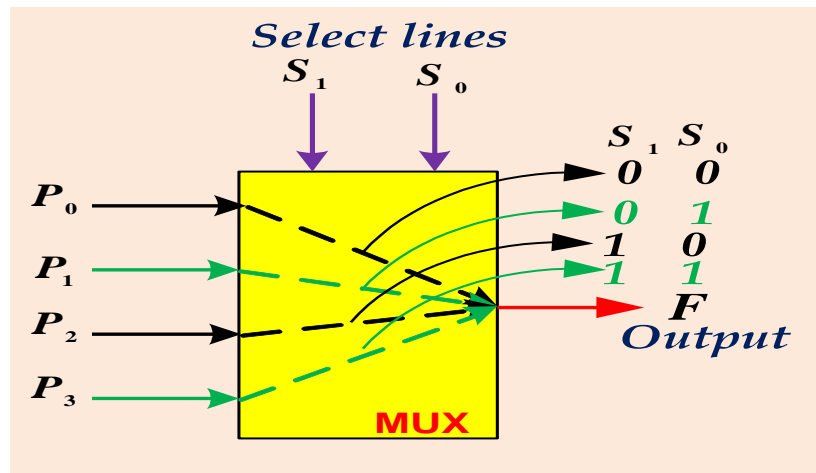

$$F = \overline{S_1} \overline{S_0} P_0 + \overline{S_1} S_0 P_1 + S_1 \overline{S_0} P_2 + S_1 S_0 P_3$$

MUX implementation




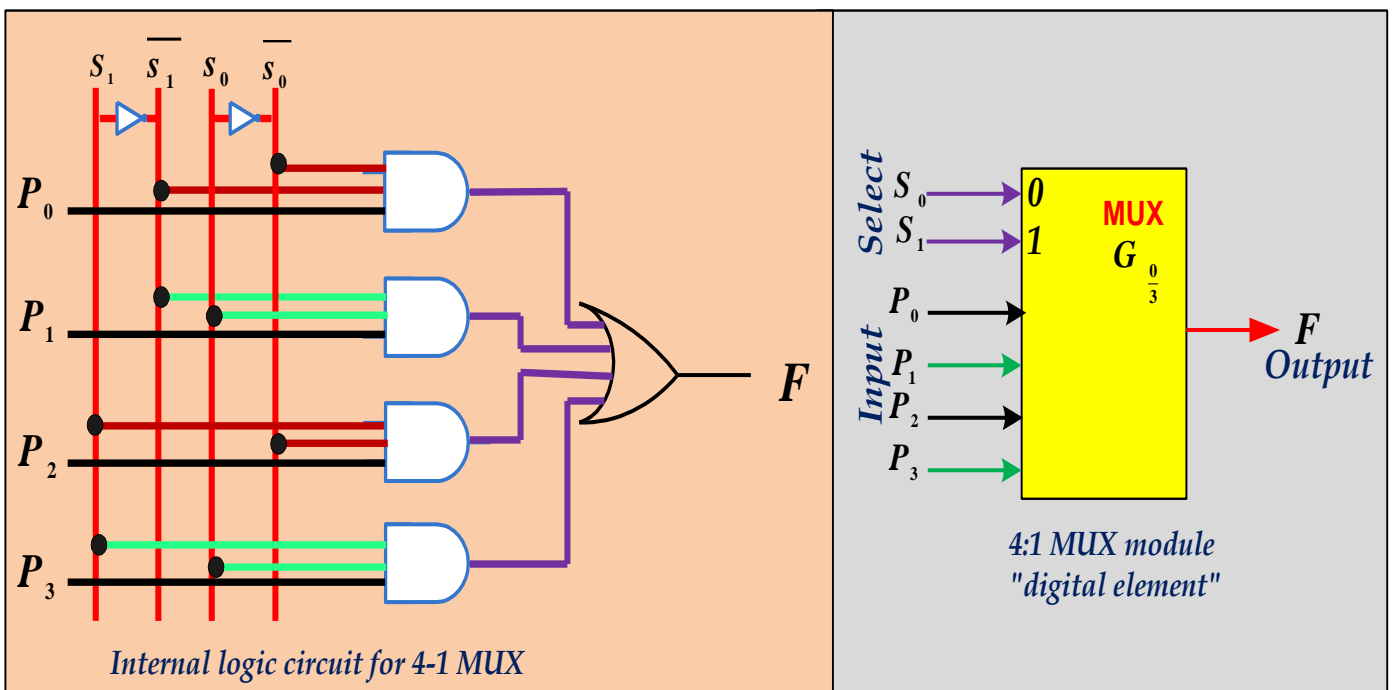


b) Design of a 8:1 multiplexer


- How to construct a **8:1 MUX** from two **4:1 MUX**.
- ✓ X_1 and X_2 are the two output lines of two **4:1 MUX**

$$X_1 = \overline{S_1} \overline{S_0} P_0 + \overline{S_1} S_0 P_1 + S_1 \overline{S_0} P_2 + S_1 S_0 P_3$$
    
$$X_2 = \overline{S_1} \overline{S_0} P_0 + \overline{S_1} S_0 P_1 + S_1 \overline{S_0} P_2 + S_1 S_0 P_3$$



Design for a 8:1 MUX network


 


(a) Connection diagram


(b) Logic symbol

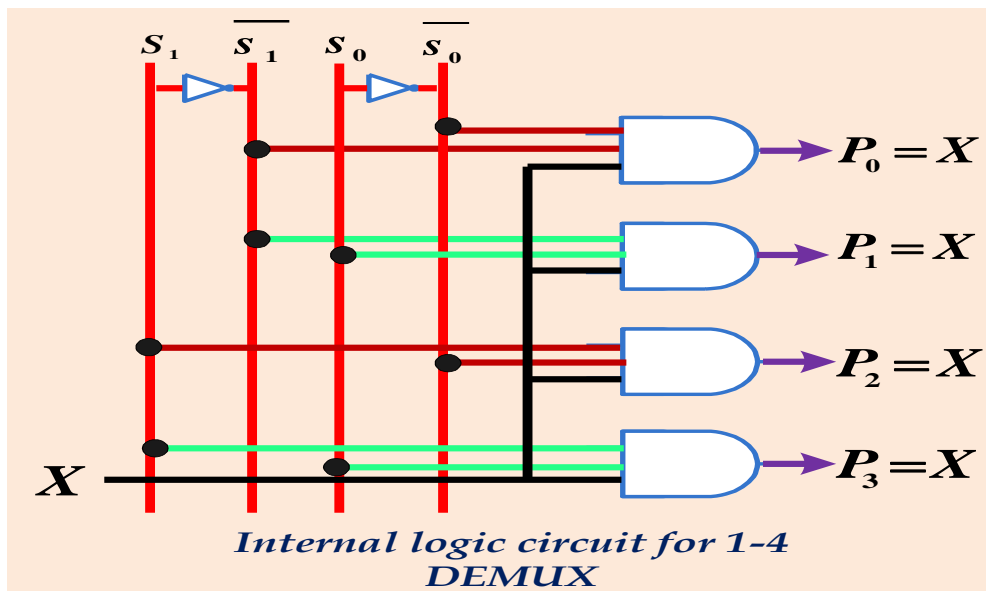 2. Demultiplexers

- The demultiplexer is a combinational logic circuit that performs the **reverse operation** of multiplexer (Several output lines, one input line).



Explain:

 

Two select lines four outputs

$$\overline{S_1} \overline{S_0} = 00 \Rightarrow P_0 = X$$

$$S_1 \overline{S_0} = 01 \Rightarrow P_1 = X$$

$$\overline{S_1} S_0 = 10 \Rightarrow P_2 = X$$

$$S_1 S_0 = 11 \Rightarrow P_3 = X$$

inputs		Output
X	C	F
0	0	0
0	1	0
1	0	0
1	1	1

3. Encoders

- An encoder is a digital circuit that performs the **inverse operation** of a **decoder**.
- An encoder has 2^n (or fewer) input lines and n output lines.
- The encoder can be implemented with **OR gate** whose inputs are determined directly from the truth table.

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1


- Output X is equal to 1 when the input digit is $4, 5, 6$ or 7 .
- Output Y is equal to 1 when the input digit is $2, 3, 6$ or 7 .
- Output Z is equal to 1 when the input digit is $1, 3, 5$ or 7 .

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

- We need **three OR gates**.

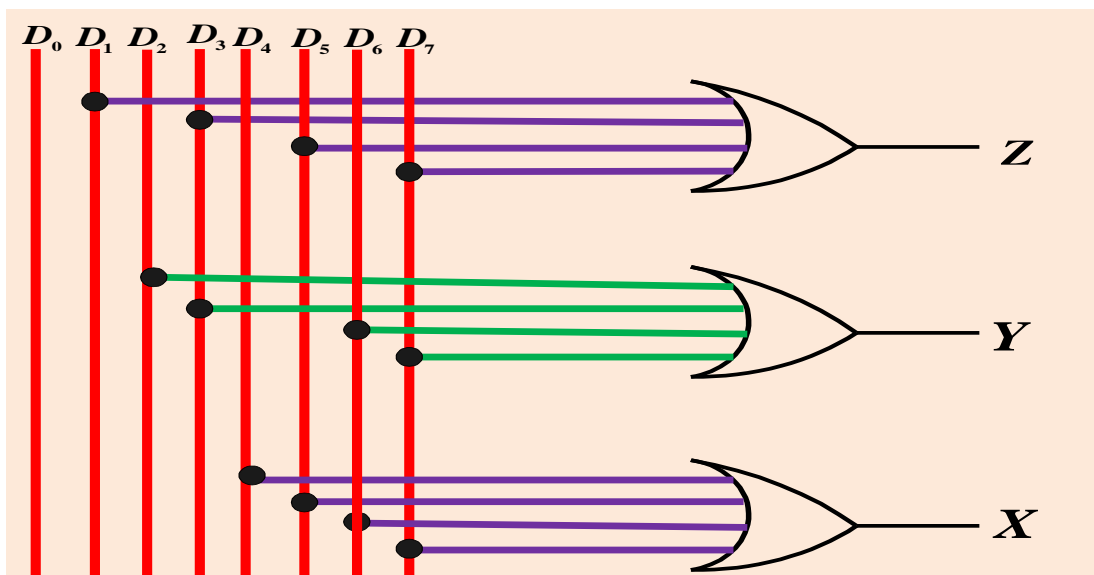


4. Examples

4.1) Active-low decoder:

- So we can use **active-low decoders** to implement arbitrary functions too, but as a **product of maxterms**.
- For example, the implementation of the function

$$f(x, y, z) = \prod M(4, 5, 7)$$

Using an active-low decoder is:

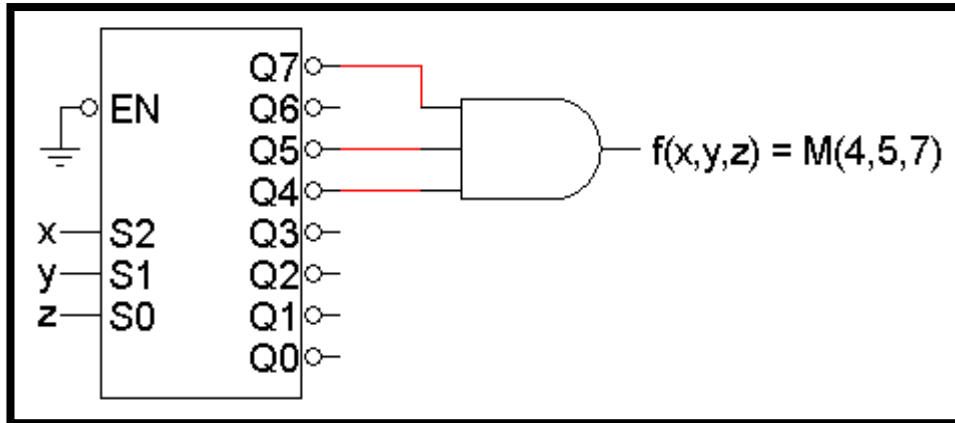

- The **“ground”** symbol connected to **EN** represents logical **0**, so this decoder is always enabled.
- Remember that you need an **AND gate** for a product of sums.


4.2) Implement the following combinational functions using active-high decoder.

$$P_1 = \sum_m(1, 2, 5, 6, 8, 11, 12, 15)$$

$$P_2 = \sum_m(1, 3, 4, 6, 8, 10, 13, 15)$$

$$P_4 = \sum_m(2, 3, 4, 5, 8, 9, 14, 15)$$

Solution:

 

4.3) A certain logic circuit has four inputs A, B, C, and D. The output X of the circuit is logic 1 if two or more inputs are logic 1.

a) Write the truth table for this circuit.


Solution:

A	B	C	D	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

b) Implement the function using one decoder with active low output.

A	B	C	D	X	Maxterm
0	0	0	0	0	$M_0 = A + B + C + D$
0	0	0	1	0	$M_1 = A + B + C + \bar{D}$
0	0	1	0	0	$M_2 = A + B + \bar{C} + D$
0	0	1	1	1	
0	1	0	0	0	$M_4 = A + \bar{B} + C + D$
0	1	0	1	1	
0	1	1	0	1	
0	1	1	1	1	
1	0	0	0	0	$M_8 = \bar{A} + B + C + D$
1	0	0	1	1	
1	0	1	0	1	
1	0	1	1	1	
1	1	0	0	1	
1	1	0	1	1	
1	1	1	0	1	
1	1	1	1	1	
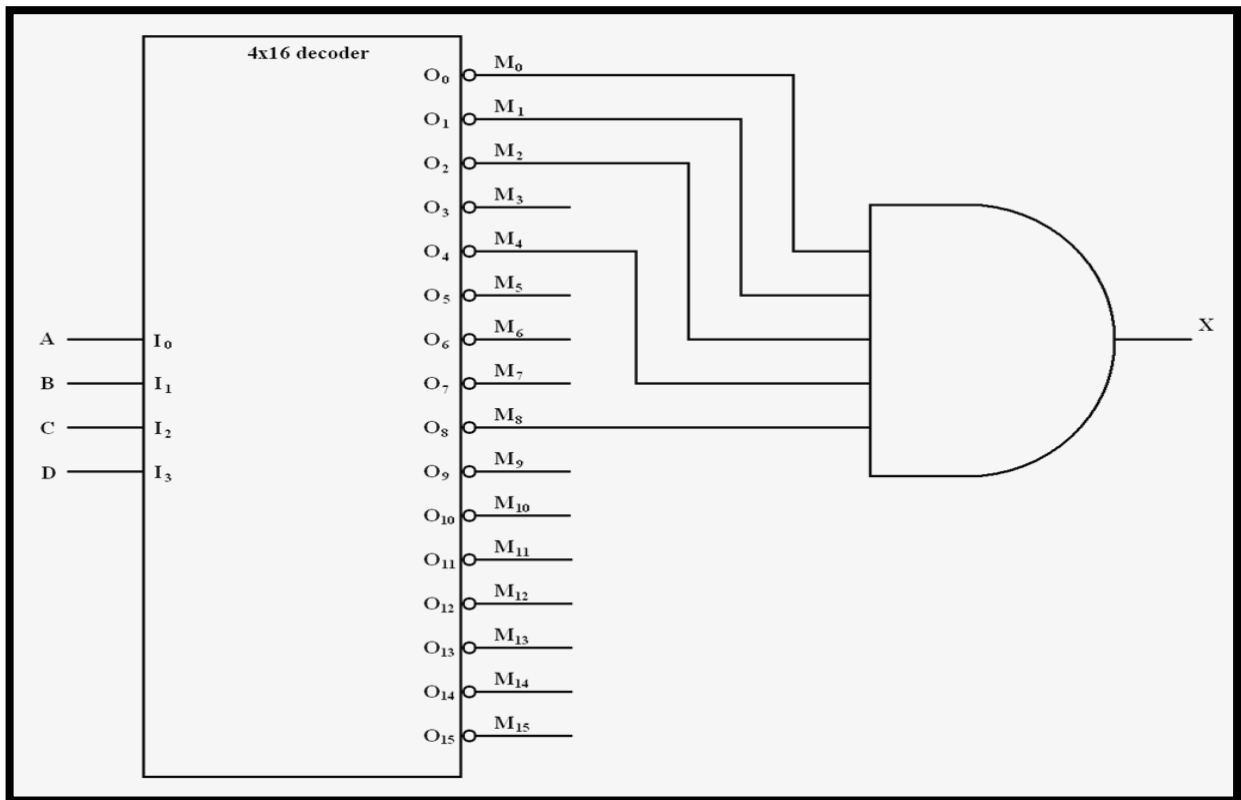
$$X(A, B, C, D) = \prod(M_0, M_1, M_2, M_4, M_8)$$




4.4) Implement the logic function f using a single multiplexer; assume that the inputs and their complements are available at the input of the multiplexer.


$$f(x, y, z) = \prod(2, 3, 4, 7)$$

Solution:

x	y	z	f	
0	0	0	1	I₀
0	0	1	1	
0	1	0	0	I₁
0	1	1	0	
1	0	0	0	I₂
1	0	1	1	
1	1	0	1	I₃
1	1	1	0	

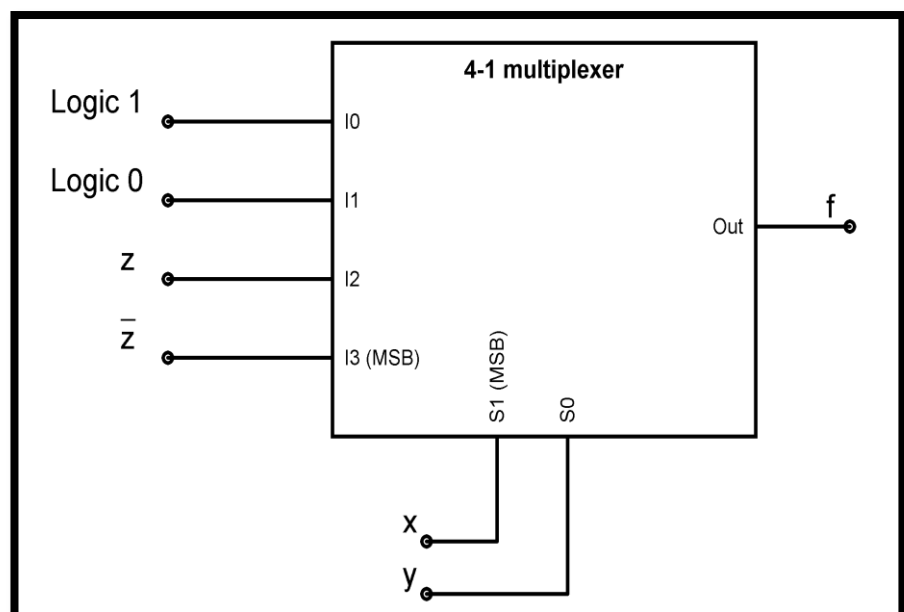

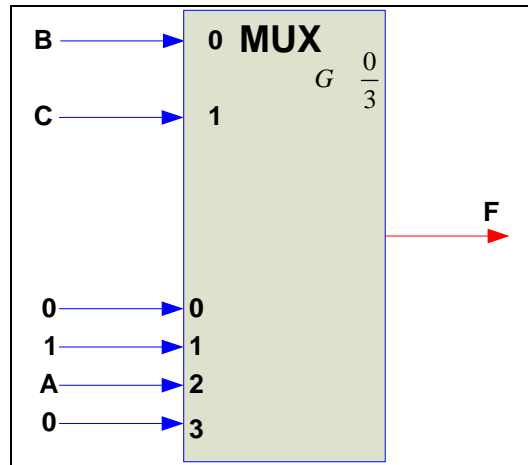4.5) The following figure shows a 4-input multiplexer connected to implement a function F of three Boolean variables A , B , C .



Complete the following truth table:

Logical Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0