

# Digital System Design

## Lecture 16


### Sequential Circuits

# Latches and Flip-Flops

#### Objectives:

1. RS latch implementation using A NOR gate.
2. RS latch using NAND gates.
3. Clocked RS latch uses a clock signal.
4. D Latch
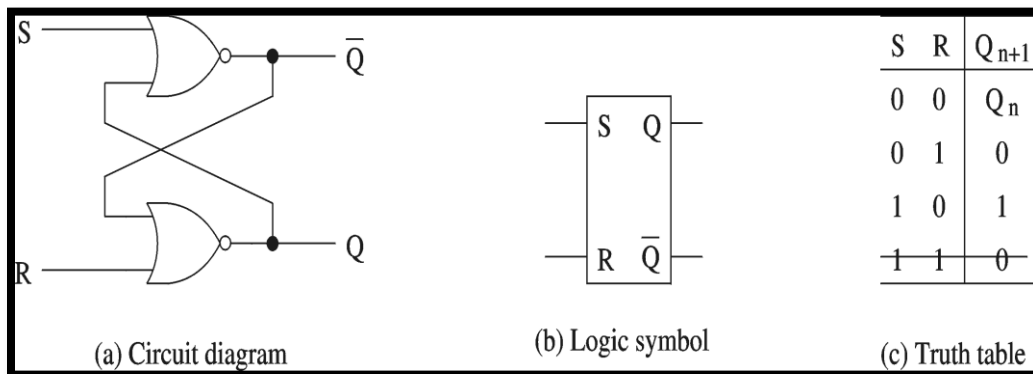
#### 1. RS latch implementation using A NOR gate



- **SR** latch have
  - two inputs **S** and **R**:
    - **S** is called **set** and it is used to produce **HIGH** on **Q** (i.e. store **1**).
    - **R** is called **reset** and it is used to produce **LOW** on **Q** (i.e. store **0**).
  - **Q'** is **Q** complementary output.
- The **output** of the **SR** latch depends on **current** as well as **previous inputs or state** (can be changed as soon as its inputs change).
- The **truth table** of **RS** latch is shown below:

S	R	Q	Q +	Comment
0	0	0	0	<b>Hold state</b>
0	0	1	1	
0	1	X	0	<b>Reset state</b>
1	0	X	1	<b>Set state</b>
1	1	X	Invalid	<b>Avoid state</b>

➤ The output equations:

○  $Q = \overline{(R + \overline{Q})}$

○  $\overline{Q} = \overline{(S + Q)}$

➤ **Cases** according to the truth table:

- **Case 1.1:**  $S = 0, R = 0$  and initial condition:  $Q = 1, \overline{Q} = 0$ .

The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \overline{Q})} = 1$$

And the complement output would be:

$$\overline{Q} = \overline{(S + Q)} = 0$$

- **Case 1.2:**  $S = 0, R = 0$  and initial condition:  $Q = 0, \overline{Q} = 1$ .

The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \overline{Q})} = 0$$

And the complement output would be:

$$\overline{Q} = \overline{(S + Q)} = 1$$

**When both  $S$  and  $R$  inputs are LOW, the output is retained as before (i.e. there is **no state change**).**

- **Case 2.1:**  $S = 1, R = 0$  and initial condition:  $Q = 1, \overline{Q} = 0$ .

The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \overline{Q})} = 1$$

And the complement output would be:

$$\overline{Q} = \overline{(S + Q)} = 0$$

- **Case 2.2:**  $S = 1, R = 0$  and initial condition:  $Q = 0, \overline{Q} = 1$ .

The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \overline{Q})} = 1$$

And the complement output would be:

$$\overline{Q} = \overline{(S + Q)} = 0$$

**When  $S$  is HIGH and  $R$  is LOW, the output  $Q$  is HIGH (i.e. **set mode**).**

- **Case 3.1:**  $S = 0, R = 1$  and initial condition:  $Q = 1, \overline{Q} = 0$ .

The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \overline{Q})} = 0$$

And the complement output would be:

$$\overline{Q} = \overline{(S + Q)} = 1$$

- **Case 3.2:**  $S = 0, R = 1$  and initial condition:  $Q = 0, \overline{Q} = 1$ .

The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \overline{Q})} = 0$$

And the complement output would be:

$$\bar{Q} = \overline{(S + Q)} = 1$$

**When  $S$  is LOW and  $R$  is HIGH, the output  $Q$  is LOW (Reset mode).**

- **Case 4.1:**  $S = 1, R = 1$  and initial condition:  $Q = 1, \bar{Q} = 0$ .  
The output  $Q$  after input is applied would be:

$$Q = \overline{(R + \bar{Q})} = 0$$

And the complement output would be:

$$\bar{Q} = \overline{(S + Q)} = 0$$

- **Case 4.2:**  $S = 1, R = 1$  and initial condition:  $Q = 0, \bar{Q} = 1$ .  
The output  $Q$  after input is applied would be:


$$Q = \overline{(R + \bar{Q})} = 0$$

And the complement output would be:

$$\bar{Q} = \overline{(S + Q)} = 0$$

 
**When both  $S$  and  $R$  inputs are HIGH, the outputs are invalid (undefined state).**

- The **waveform** below shows the operation of **RS Latch based NOR gates**.


 
## 2. RS latch using NAND gates

- It is possible to construct the RS latch using **NAND gates**.
- The circuit and Truth table of RS latch using NAND is shown below:



$S$	$R$	$Q$	$Q+$
1	1	0	0
1	1	1	1
0	1	X	0
1	0	X	1
0	0	X	<b>Invalid</b>


When  $R = 0$   
and  $S = 0$   
becomes the  
**invalid case.**

$\bar{S}$	$\bar{R}$	$Q$	$\bar{Q}$
0	0	1	1
0	1	1	0
1	0	0	1
1	1	Q	$\bar{Q}$

**Weird state**  
**Set state**  
**Reset state**  
**Hold state**

I1	I2	F
0	0	1
0	1	1
1	0	1
1	1	0
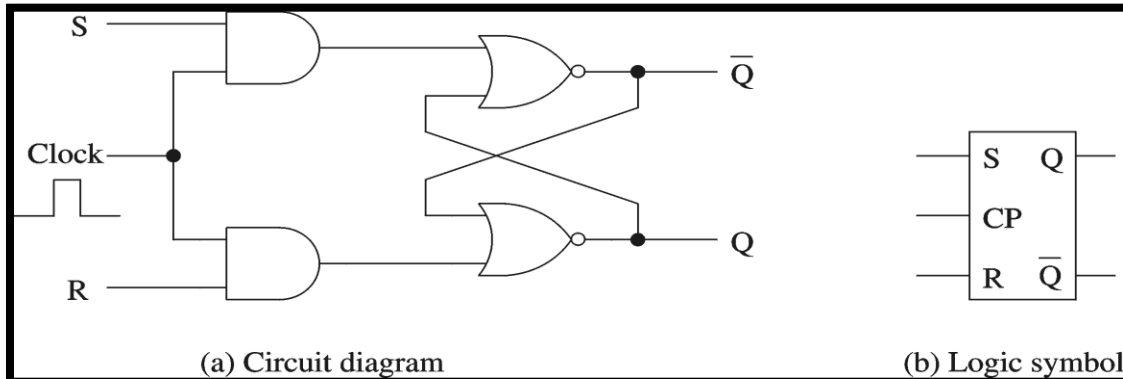
### 3. Clocked RS latch uses a clock signal




- The circuit below shows the level sensitive **RS** latch. Control signal "**Enable**" **E** is used to gate the input **S** and **R** to the **RS** Latch.
  - When Enable **E** is **HIGH**, both the **AND** gates act as **buffers** and thus **R** and **S** appears at the **RS** latch input and it functions like a normal **RS** latch.
  - When Enable **E** is **LOW**, it drives **LOW** to both inputs of **RS** latch ( $\therefore S = 0, R = 0$ , i.e. the not change mode).



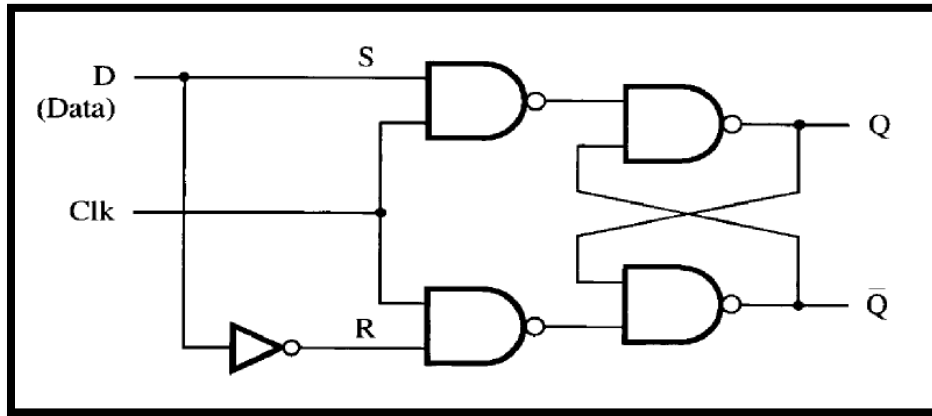
### 4. D Latch

- An RS-flip flop is rarely used in actual sequential logic; however, it is the fundamental building block for the very useful.
- The RS latch contains an invalid state; to eliminate this state we can ensure that S and R are never equal (Avoids the SR = 11 state).
- To eliminate this state, we connect S and R together with an inverter. Thus we have D Latch.
- The D-flip flop has only a single data input, this input is called D or Data input.
- That data input is connected to the S input of an RS-flip flop, while the inverse of D is connected to the R input.
- D latch is called delay flip-flop or delay latch also.

➤ Below is the truth table and circuit of D latch.



<b>D</b>	<b>Q</b>	<b>Q+</b>
<b>1</b>	<b>X</b>	<b>1</b>
<b>0</b>	<b>X</b>	<b>0</b>

 

- In real world designs (ASIC/FPGA Designs) only D latches/Flip-Flops are used.
- To allow the flip flop to be in a holding state, a D-flip flop has a second input called "Enable."

