

Digital System Design

Digital Lecture 10

Karnaugh Map Methods- II

Objectives:

1. Four variables maps.
2. Simplification using prime implicants.
3. "Don't care" conditions.
4. Summary.

1. Four variables Karnaugh maps

A	B	C	D	Minterms
0	0	0	0	$\overline{A}\overline{B}\overline{C}\overline{D}$
0	0	0	1	$\overline{A}\overline{B}\overline{C}D$
0	0	1	0	$\overline{A}\overline{B}C\overline{D}$
0	0	1	1	$\overline{A}\overline{B}CD$
0	1	0	0	$\overline{A}B\overline{C}\overline{D}$
0	1	0	1	$\overline{A}B\overline{C}D$
0	1	1	0	$\overline{A}BC\overline{D}$
0	1	1	1	$\overline{A}BCD$
1	0	0	0	$A\overline{B}\overline{C}\overline{D}$
1	0	0	1	$A\overline{B}\overline{C}D$
1	0	1	0	$A\overline{B}C\overline{D}$
1	0	1	1	$A\overline{B}CD$
1	1	0	0	$AB\overline{C}\overline{D}$
1	1	0	1	$AB\overline{C}D$
1	1	1	0	$ABC\overline{D}$
1	1	1	1	$ABCD$

AB \ CD		C			
		$\overline{C}\overline{D}$ 00	$\overline{C}D$ 01	CD 11	$C\overline{D}$ 10
\overline{A}	00 $\overline{A}\overline{B}$	m0 $\overline{A}\overline{B}\overline{C}\overline{D}$	m1 $\overline{A}\overline{B}\overline{C}D$	m3 $\overline{A}\overline{B}C\overline{D}$	m2 $\overline{A}\overline{B}CD$
	01 $\overline{A}B$	m4 $\overline{A}B\overline{C}\overline{D}$	m5 $\overline{A}B\overline{C}D$	m7 $\overline{A}B\overline{C}D$	m6 $\overline{A}B\overline{C}\overline{D}$
A	11 $A\overline{B}$	m12 $A\overline{B}\overline{C}\overline{D}$	m13 $A\overline{B}\overline{C}D$	m15 $A\overline{B}C\overline{D}$	m14 $A\overline{B}CD$
	10 AB	m8 $AB\overline{C}\overline{D}$	m9 $AB\overline{C}D$	m11 $ABC\overline{D}$	m10 $ABCD$
		\overline{D}	D	\overline{D}	

CD \ AB		AB			
		00	01	11	10
CD	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

CD \ AB		AB			
		00	01	11	10
CD	00	$A'B'C'D'$	$A'BC'D'$	$ABC'D'$	$AB'C'D'$
	01	$A'B'C'D$	$A'BC'D$	$ABC'D$	$AB'C'D$
	11	$A'B'CD$	$A'BCD$	$ABCD$	$AB'CD$
	10	$A'B'CD'$	$A'BCD'$	$ABC'D'$	$AB'CD'$

➤ The rows and columns are numbered in a *gray code sequence*.

- ✓ One square represents one minterm with four literals.
- ✓ Two adjacent squares represent one term with 3 literals.
- ✓ Four adjacent squares represent one term with 2 literals.
- ✓ Eight adjacent squares represent one term with 1 literal.

Examples:

Example 1: Simplify the Boolean function

$$F(w, x, y, z) = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

Solution:

yz	00	01	11	10
wx 00	m0 1	m1 1	m3 0	m2 1
01	m4 1	m5 1	m7 0	m6 1
11	m12 1	m13 1	m15 0	m14 1
10	m8 1	m9 1	m11 0	m10 0

$\overline{w} y z + w y z = \overline{w} z$

$x y z + x y \overline{z} = x z$

\overline{y}

$F(w, x, y, z) = \overline{y} + \overline{w} z + x z$


The simplified function:

$$F(w, x, y, z) = \overline{y} + \overline{w} z + x z$$

Example 2: plot the following 4-variable expression on a Karnaugh map

$$f(a, b, c, d) = acd + \bar{a}b + \bar{d}$$


Solution:

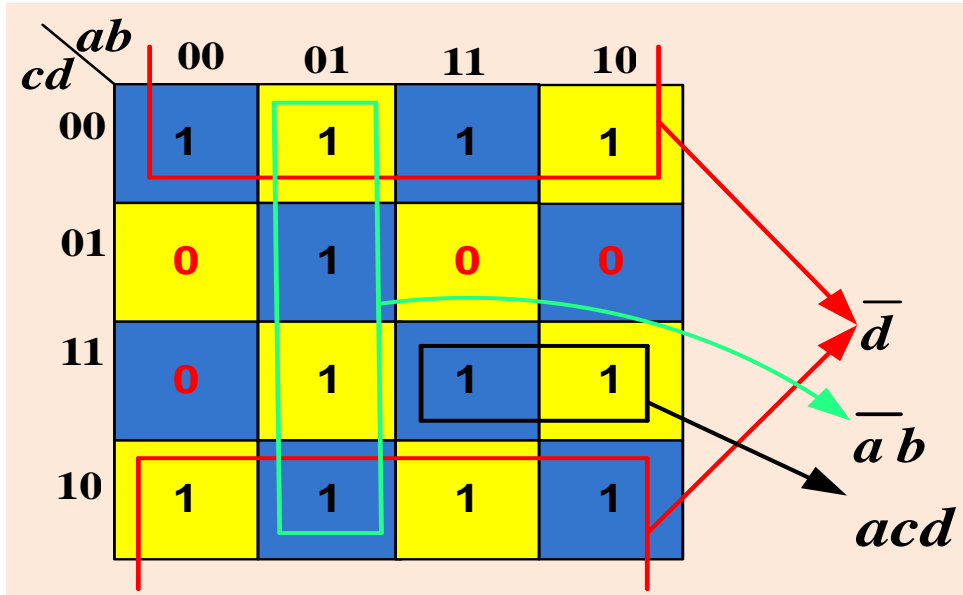


Example 3: simplify the following function:

$$f(a, b, c, d) = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$$

Solution:

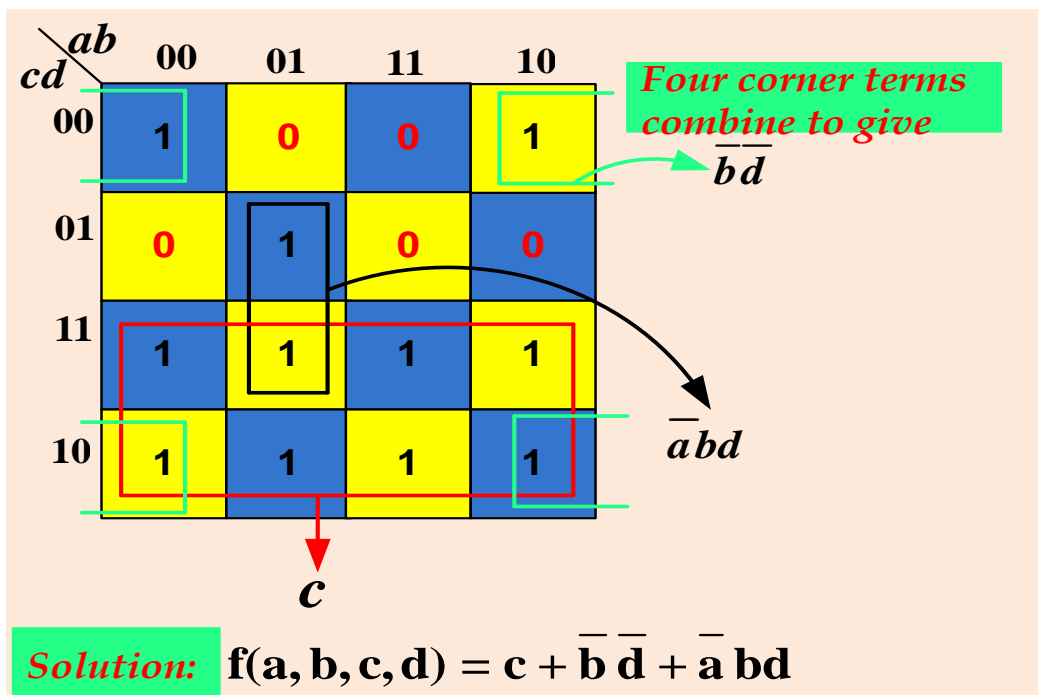

Example 4: For the following k-map with four variables, obtain the simplified logic expression:

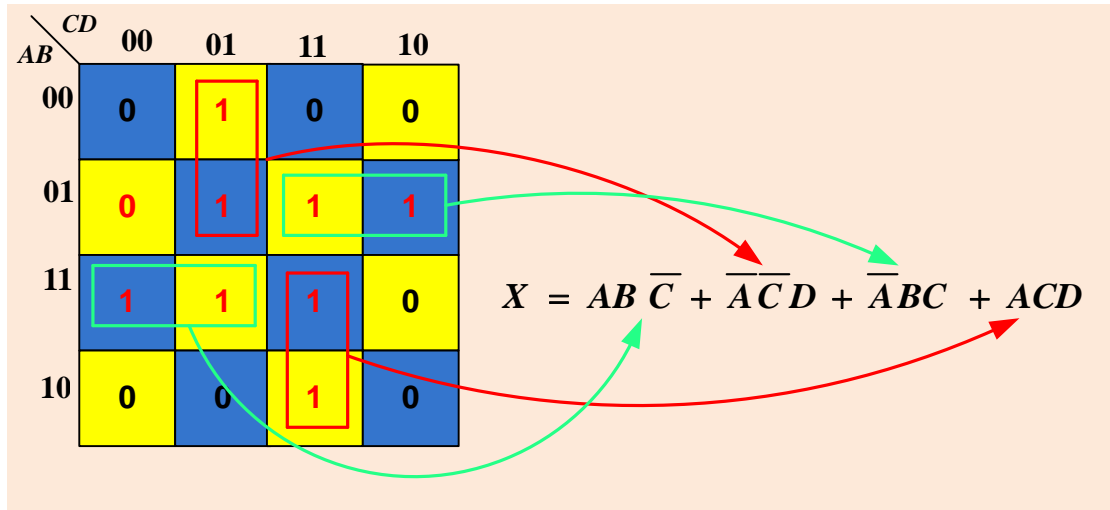

Example 5: Use a k-map to simplify


$$Y = \bar{C}(\bar{A}\bar{B}\bar{D} + D) + \bar{A}\bar{B}C + \bar{D}$$

Solution:

- Multiply out

$$Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{C}D + \bar{A}\bar{B}C + \bar{D}$$

- Fill the terms in k-map:

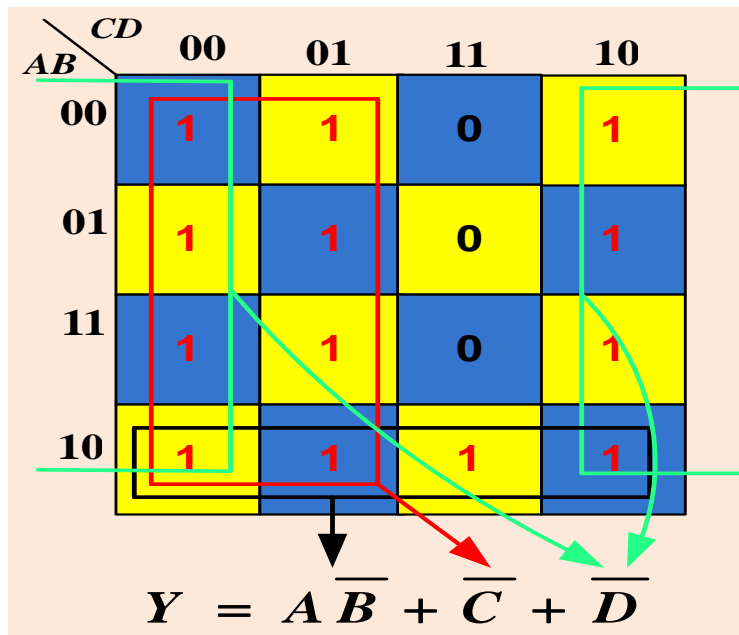

- Simplify:

$$Y = \bar{A}\bar{B} + \bar{C} + \bar{D}$$

2. Simplification using prime implicants

Definitions:

- ✓ **Prime implicant (PI):** is a product term obtained by *combining the maximum possible number of adjacent squares in the map*.
- ✓ **Essential prime implicant:** If a minterm in a square is *covered by only one prime implicant* that prime implicant is said to be *essential*, and it *must be included* in the final expression.


Note:

All of the prime implicants of a function are generally not needed in forming the minimum sum of products.

Procedure for selecting implicants:


1. Find **essential** prime implicants.
2. Find a minimum set of prime implicants which cover the remaining **1's** on the map.

Example 1:

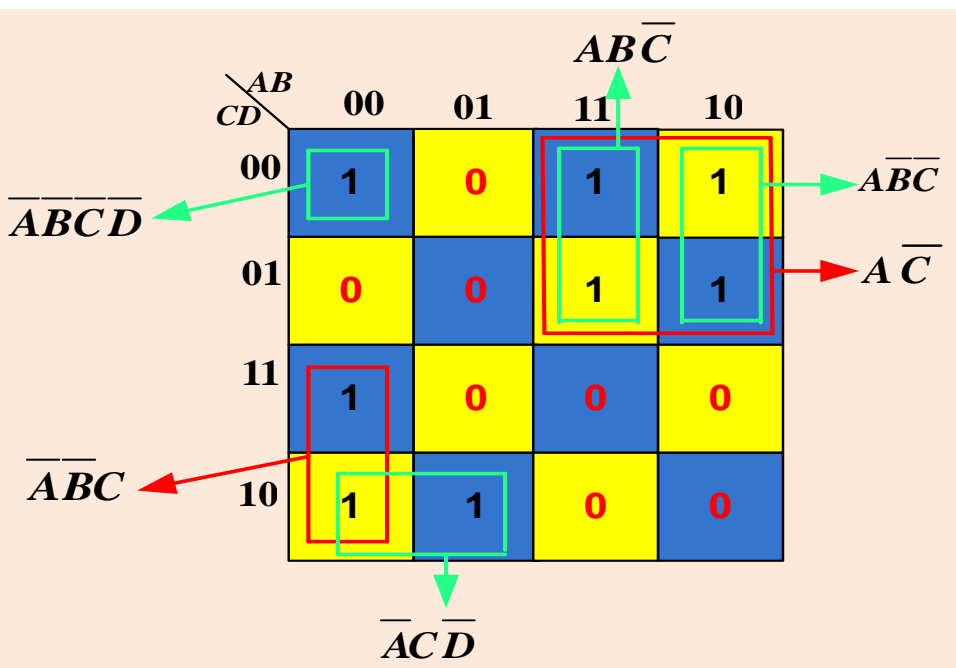

- ✓ $\overline{A}\overline{B}\overline{C}, \overline{A}\overline{C}\overline{D}, A\overline{C}$ are prime implicants.
- ✓ $\overline{A}\overline{B}\overline{C}\overline{D}, \overline{A}\overline{B}\overline{C}, \overline{A}\overline{B}\overline{C}$ are not prime implicants.

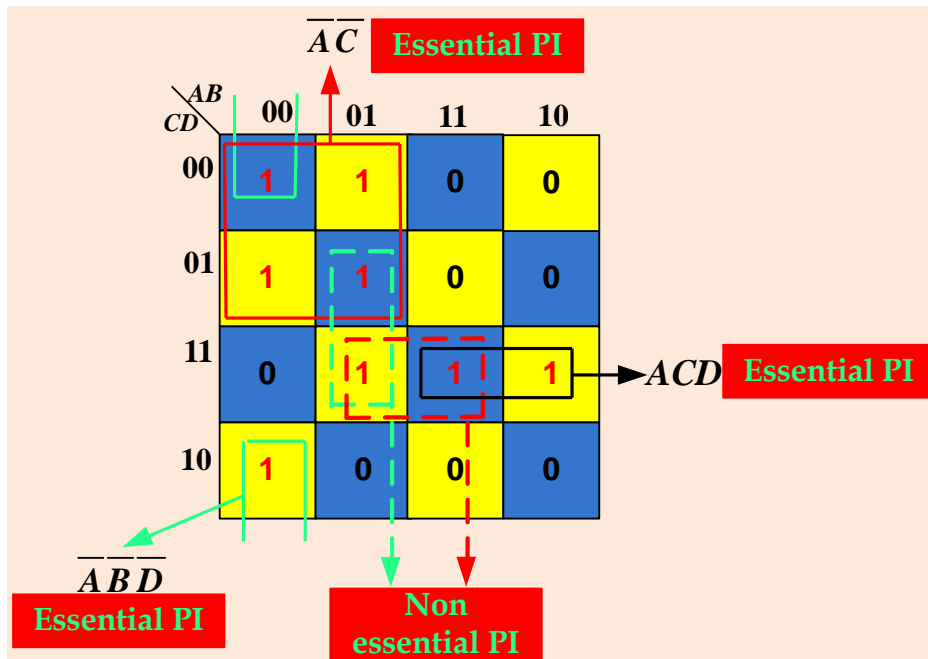Example 2: find the minimum solution for the following Karnaugh map.




- ✓ $\overline{AC}, ACD, \overline{ABD}$ are essential prime implicants, to complete the minimum solution, one of the non-essential prime implicants is needed:
- ✓ **The final solution:**

$$F = \overline{AC} + \overline{ABD} + ACD + \{\overline{ABD} | BCD\}$$

Example 3:

$$F(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

Simply using k-map:

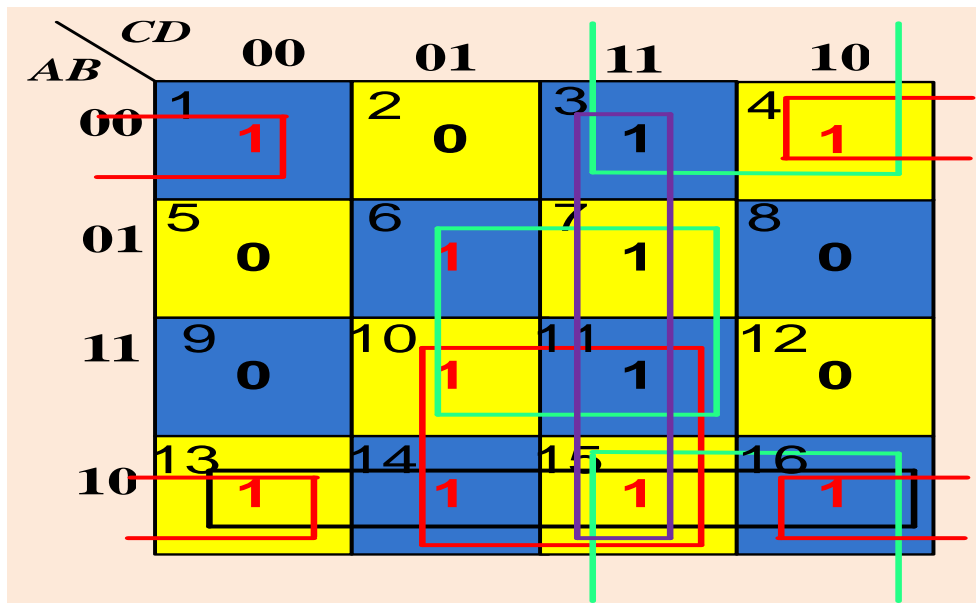

Groups (terms number)	Implicants	Simplification
1, 4, 13, 16	Essential prime implicant	$\overline{B}\overline{D}$
6, 7, 10, 11	Essential prime implicant	BD
3, 4, 15, 16	Prime implicant	$\overline{B}C$
3, 7, 11, 15	Prime implicant	CD
10, 11, 14, 15	Prime implicant	AD
13, 14, 15, 16	Prime implicant	$A\overline{B}$
2 essentials and four prime implicants		

- ✓ **Square 3** can be covered with either prime implicants CD or $\overline{B}C$.
- ✓ **Square 14** can be covered with either prime implicants AD or $A\overline{B}$.
- ✓ **Square 15** can be covered with any one of four prime implicants.
 - **Final solution:** two essential PI with any two prime implicants that cover minterms **3, 14, 15**: four possible ways:

$$1) F = BD + \overline{B}\overline{D} + CD + AD$$

$$2) F = BD + \overline{B}\overline{D} + CD + A\overline{B}$$

$$3) F = BD + \overline{B}\overline{D} + \overline{B}C + AD$$

$$4) F = BD + \overline{B}\overline{D} + \overline{B}C + A\overline{B}$$

3. "Don't care" conditions


- Some logic circuits can be designed so that there are *certain input conditions for which there are no specified output levels* (can't happen).
- A circuit designer is *free* to make the output for any "don't care condition" either a **0** or a **1** in order to produce the simplest output.

Example 1: For the following truth table, use K-map to minimize the function Z

inputs			Output
A	B	C	Z(x, y, z)
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	X
1	0	0	X
1	0	1	1
1	1	0	1
1	1	1	1

Don't Care Condition


Solution:

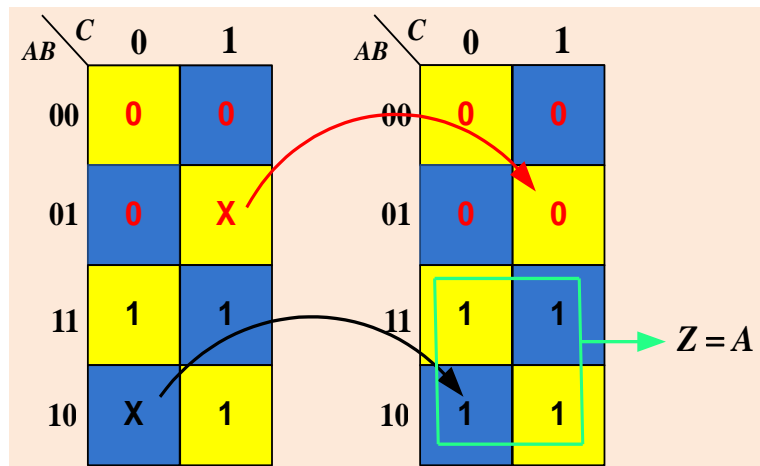

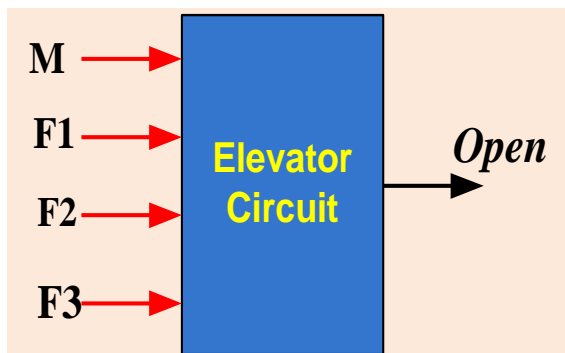
Example 2: Design a logic circuit that controls an elevator door in a three-story building.

Solution:

M: Moving signal: ($M = 1$: moving), ($M = 0$: stopped),
F1, F2, F3: Floor indicator signals.




Truth Table				
M	F1	F2	F3	Open
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	X
0	1	0	0	1
0	1	0	1	X
0	1	1	0	X
0	1	1	1	X
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	X
1	1	0	0	0
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

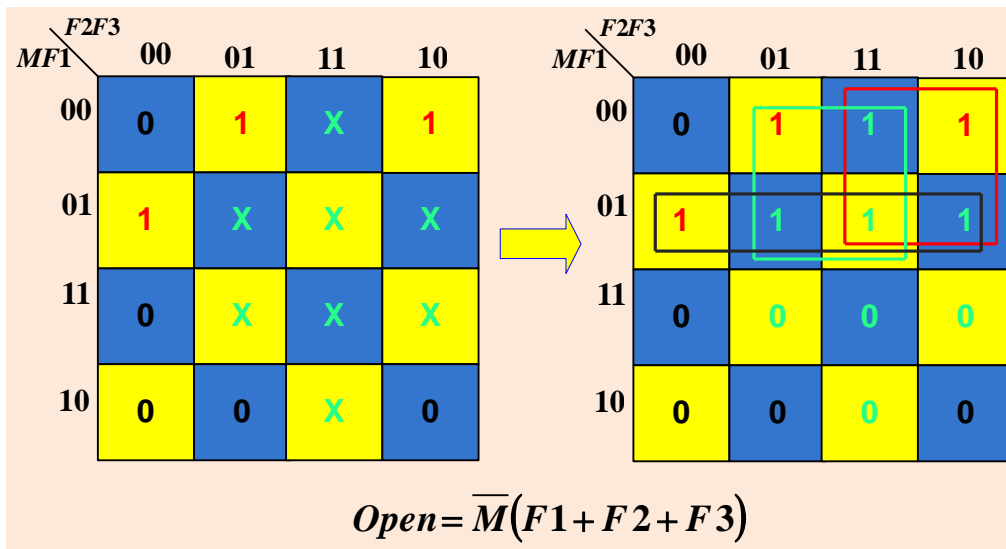

Example 3: For the following logical expression, use K-map to minimize the function F .

$$F = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$$


Solution:

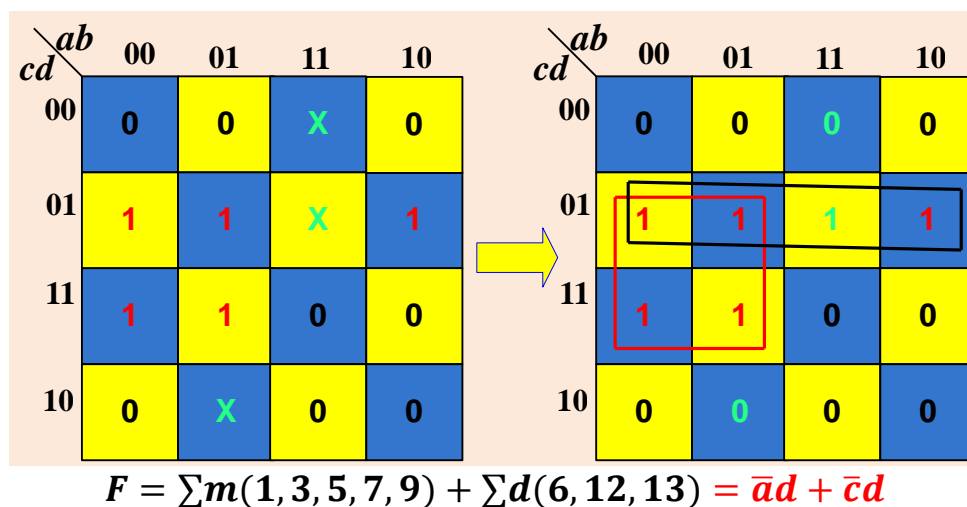


4. Summary

- Looping a pair of adjacent 1's in a k-map eliminate the variable that appears in complemented and uncomplemented form.
- Looping a quad (4) of adjacent 1's eliminates the two variables that appear in complemented and uncomplemented form.
- Looping an octet (8) of adjacent 1's eliminates the three variables that appear in complemented and uncomplemented form.

o Looping groups of two pairs:

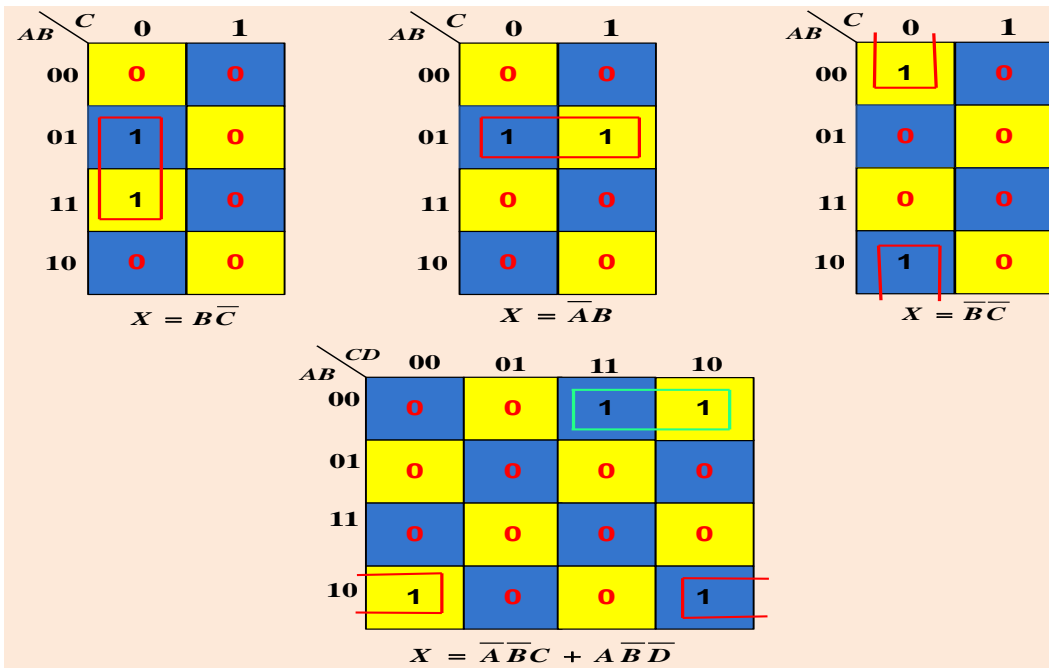

o Looping groups of four (quads):

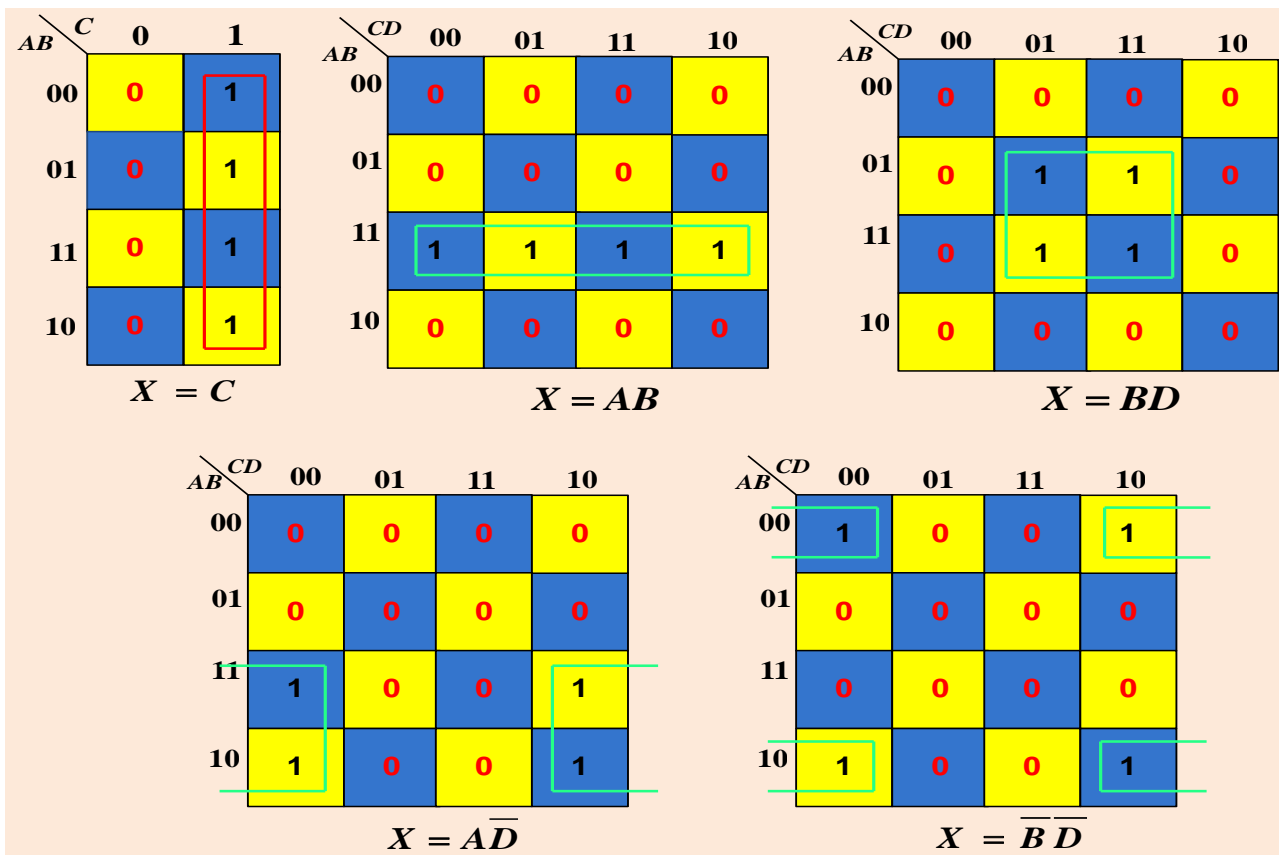

o Looping groups of eight (octet):

