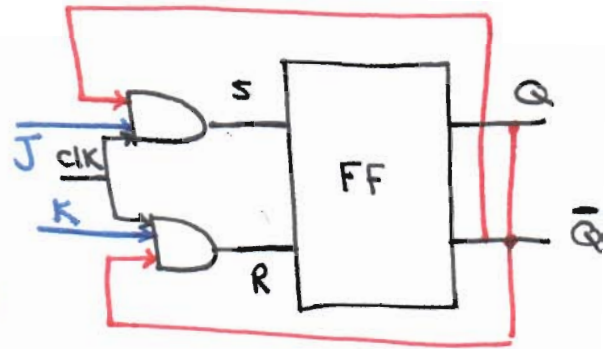


③ J-K Flip-flop

①

The J-K flip-flop combines the features of the S-R and T flip-flops.

CLK	J	K	Q(t+1)
↑	0	0	Q(t) - No change
↑	0	1	0 - Reset
↑	1	0	1 - Set
↑	1	1	$\bar{Q}(t)$ - Complement




1) **Characteristics Table**: A characteristics table defines the logical properties of a flip-flop by describing its operation in tabular form, it defines the next state (the state that results from a clock transition) as a function of inputs and the present state $Q(t)$.

2) **Characteristic Equation**:

$$Q(t+1) = J\bar{Q} + \bar{K}Q$$

To get the characteristic equation

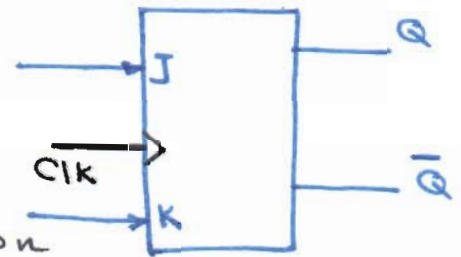We use the truth table and Karnaugh map to minimize the output:



Inputs		Q	Q(t+1)
J	K		
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$Q(t+1) = Q(t)$ (no change)

$Q(t+1) = 0$ (Reset)

$Q(t+1) = 1$ (Set)

$Q(t+1) = \bar{Q}(t)$ → Complement

this table called "Next-State table"

JK	00	01	11	10
Q(t) 0	0	0	1	1
Q(t) 1	1	0	0	1

$$Q(t+1) = J\bar{Q} + \bar{K}Q$$


Characteristics (Next state) equation.

3) Excitation Table :

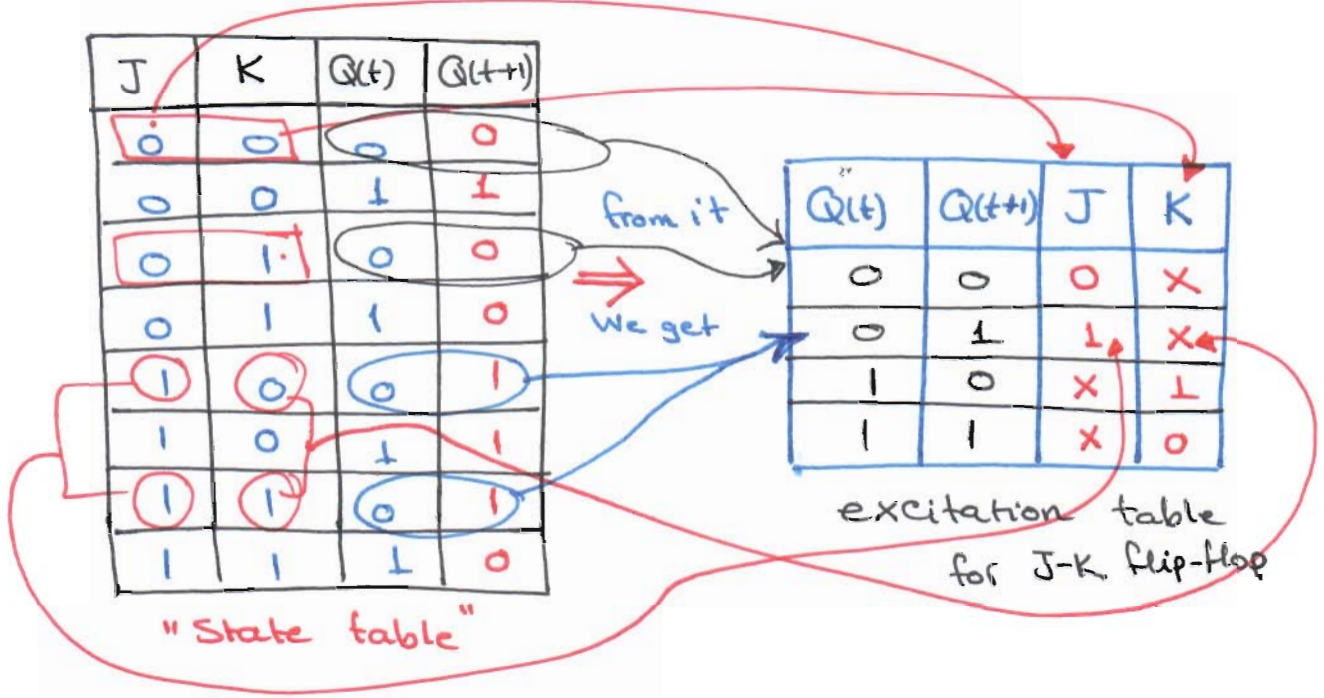(2)

During the design process we usually know the transition from present state to the next state and wish to find the flip-flop input conditions that will cause the required transition.

We can derive the excitation table from the truth table.



4) T- flip flop (Trigger flip-flop)

1) T- flip-flop characteristics table (Next-state table)




T	Q(t+1)
0	Q(t) (No change)
1	$\overline{Q(t)}$ (complement)

Q(t)	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

State table

Q(t)	Q(t+1)	T
0	0	0
0	1	1
1	0	1
1	1	0

excitation table

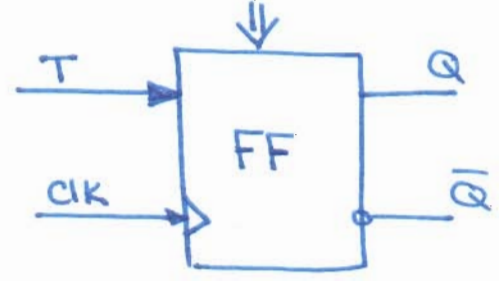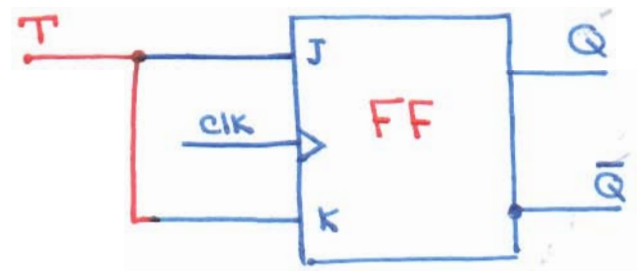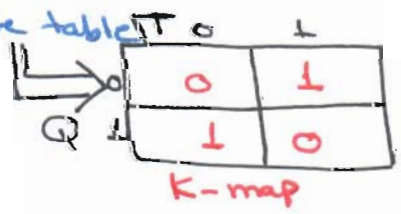

Graphic symbol for T-trigger

$$Q(t+1) = T \oplus Q(t) = T\overline{Q(t)} + \overline{T}Q(t)$$
 Characteristics equation (State equation) for T-trigger.

S-R flip flop:

S	R	Q(t)	Q(t+1)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

Next State table

Q(t)	Q(t+1)	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0

"excitation table"

SR	00	01	11	10
Q(t) = 0	0	0	X	1
Q(t) = 1	1	0	X	1

* Any illegal input combinations should be treated as don't cares

$$Q(t+1) = S + Q(t) \cdot \bar{R}$$

"State equation for S-R flip-flop."

D - flip flop

D	Q(t+1)
0	0 "Reset"
1	1 "Set"

State table

D	Q(t)	Q(t+1)
0	0	0
0	1	0
1	0	1
1	1	1

truth table (state)

$$Q(t+1) = D$$

State-equation

Q(t)	Q(t+1)	D
0	0	0
0	1	1
1	0	0
1	1	1


excitation table

* Clocked Flip-flops with clear and Reset Inputs. (Direct Inputs)

Clocked integrated circuit flip-flops often have additional inputs which can be used to set the flip-flop to an initial state independent of the clock.

in most cases the logic "0" is used (required) to clear or set the flip-flop

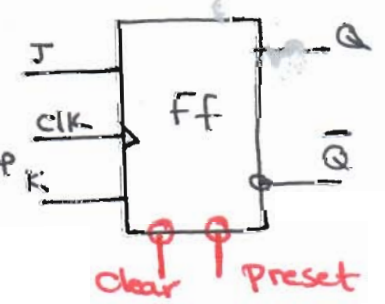
* These inputs can be used for other flip-flops.



⑤

Master-slave \rightarrow flip-flop.

④

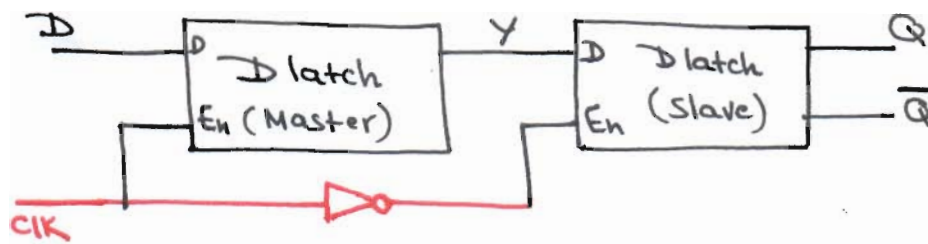

The construction of a D flip-flop with two latches and an inverter. (The first is called the master and the second the slave)

• CLK = 0 : The slave latch is enabled and its output Q is equal to the master output Y , the master is disabled because $CLK = 0$.

• CLK = 1 :

master D latch is enabled: the data from the external D input are transferred to the master, the slave is disabled.

Any change in the input changes the master output at Y , but cannot affect the slave output.

We can construct Master-slave design with other flip-flop kinds.

Analysis of clocked Sequential Circuits

Analysis describes what a given circuit will do under certain operating conditions.


The outputs and the next state are both a function of the inputs and the present state.

Analysis steps:

1. Construct the state table.
2. Construct the state diagram.
3. Write the state equations.
4. State Reduction.
5. State assignment.
6. Construct the excitation table

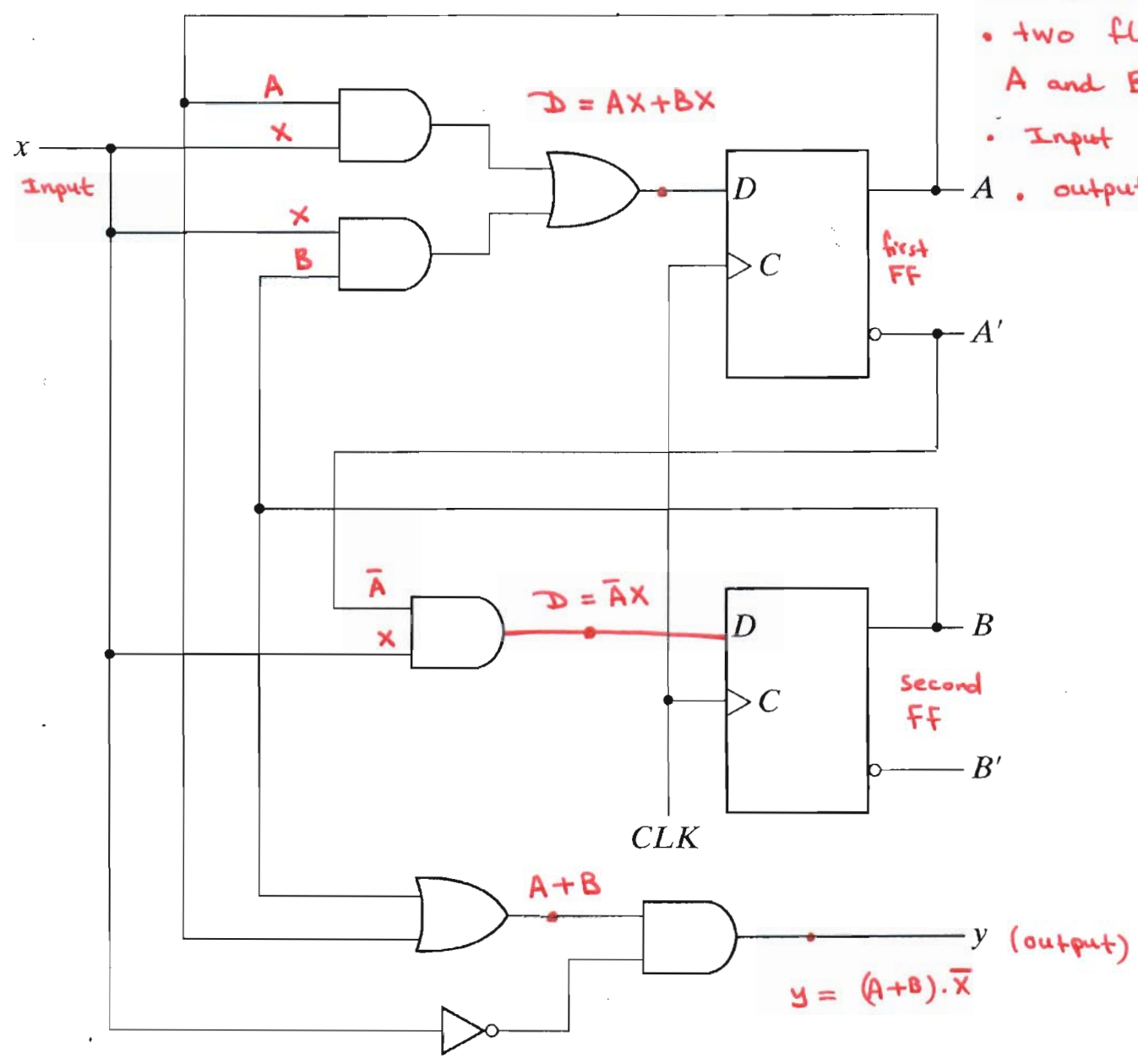Example: Consider the sequential circuit shown in figure: (5)

- We have
- two flip-flops A and B.
 - Input X
 - output Y.



The behavior of a clocked sequential circuit can be described by **state equation (or transition equation)** specifies the next state as a function of the present state and inputs.

① The state equations for the circuits are the following: \Rightarrow

$$A(t+1) = A(t)X(t) + B(t)X(t)$$

$$B(t+1) = \bar{A}(t) \cdot X(t)$$

Boolean expression that specifies the present state and input conditions that make the next state equal to 1.

next state of the flip-flop one clock edge later

* The boolean expressions for the state equations can be derived directly from the gates that form the combinational circuit part

of the sequential circuit.

* The present state value of the output equal

$$y(t) = [A(t) + B(t)] \cdot \bar{x}(t)$$

Simply, we can write :

$$y = (A + B) \cdot \bar{x}$$

State Table for Circuit

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Table for Circuit : Table 1

② State Table

The state table (also called a transition table) consists of four sections: ^(Table 1) present state, input, next state and output.

- present state: states of flip-flops A and B at any given time t.
- input section gives a value of x for each possible present states

• next state section: **Two-Dimensional State Table for the Circuit**

Shows the states of flip-flops after one clock cycle later, at time t+1

• The output section gives the value of y at time t.

Present state		Next state				Output	
		X = 0		X = 1		X = 0	X = 1
A	B	A	B	A	B	Y	Y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

Two-Dimensional State Table for the Circuit : Table 2

* The next state values are calculated from the state equations

* The output values are calculated from the output equation.

Some times the state table is expressed using ⁽⁷⁾ Two-dimensional state table as Table 2.

(The input conditions are enumerated under the next-state and output sections.

3. State Diagram :

The information available in a state table can be represented graphically in the form of a state diagram

- State is represented by circle.

- Transitions between states are indicated by directed lines

* The state diagram provides the same information as the state table and is obtained directly from table 1 or table 2


* The state table is easier to derive from a given logic diagram or/and the state equation.

first number input value during the present state.

* The state diagram gives a pictorial view of state transitions

The state of flip-flops

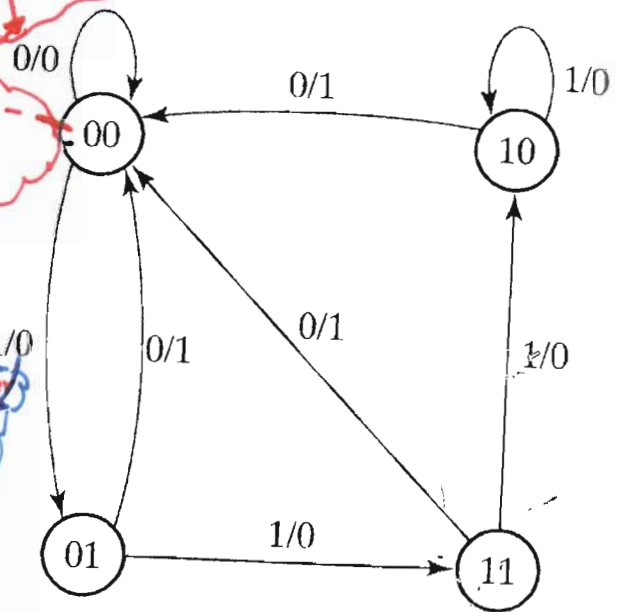second number output value during the present state



State Diagram of the Circuit

Flip-Flop Input Equation (Important !!)

* The knowledge of the type of flip-flops and a list of the boolean expressions of the combinational circuit provide the information needed to draw the logic diagram of the sequential circuit.

output equations: The part of the combinational circuit that generates external output.

input equations: (excitation equation): The part of the circuit that generates the inputs to flip-flop.

examples:

8

① $D_q = x + y$

this input equation specifies the OR gate with inputs x and y connected to the D input of a flip-flop.

② The logic diagram of the circuit (in previous section) can be expressed algebraically with two flip-flop input equations and one output equation:

$$D_A = AX + BX$$

$$D_B = \bar{A}X$$

$$Y = (A + B)\bar{X}$$

The three equations provide the necessary information for drawing the logic diagram of the sequential circuit.