

# Digital System Design

## Lecture 7

# Boolean Algebra - I

### Objectives:-

1. Binary operators and their representations.
2. Relationships between Boolean expressions, Truth tables and Logic circuits.
3. Logic gates' postulates, laws and properties.

### 1. Binary operators and their representations

- *Boolean algebra* is the basic mathematics needed for logic design of digital systems; Boolean algebra uses *Boolean (logical) variables with two values (0 or 1)*.


"Two- valued Boolean algebra"

### Basic operations:

- The basic operations of Boolean algebra are **AND**, **OR**, and **NOT** (*complement*).
- a) **NOT operation (NOT Gate):-**

$$\bar{1} = 0; \bar{0} = 1$$

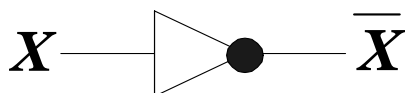- The **not** operator is also called the *complement* or the *inverse*:
- $\bar{x}$  is the complement of **x**.
- Output is *opposite* of input.
- **Truth table**: truth table describes inputs and outputs in terms of **1<sub>2</sub>** and **0<sub>2</sub>** rather physical (voltage) levels.



*Not gate representation*

### Truth table:


Input <i>x</i>	Output $\bar{x}$
0	1
1	0

1 – high  
0 – low

**b) AND operation (AND gate).**


- The output is **1** only if all inputs are **1**, if any of the input is **0**, then the output is **0**.
- The truth table of **AND gate (2-inputs, 1-output)** as the following:

Inputs		Output
<i>A</i>	<i>B</i>	$Y = A \cdot B$
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>0</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>

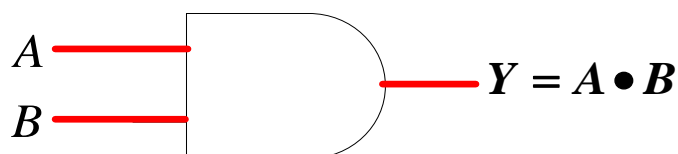

*The AND operation is referred to as logical multiplication*

**c) OR operation (OR gate)**

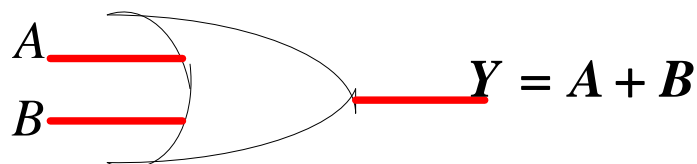


*The output is 1 if A is 1 or if B is 1*

- The truth table of **OR gate (2-inputs, 1-output)** as the following:

Inputs		Output
<i>A</i>	<i>B</i>	$Y = A + B$
<b>0</b>	<b>0</b>	<b>0</b>
<b>0</b>	<b>1</b>	<b>1</b>
<b>1</b>	<b>0</b>	<b>1</b>
<b>1</b>	<b>1</b>	<b>1</b>

*OR operation is sometimes referred to as "inclusive OR" or logical addition.*


**d) NAND gate: (Not AND gate)**

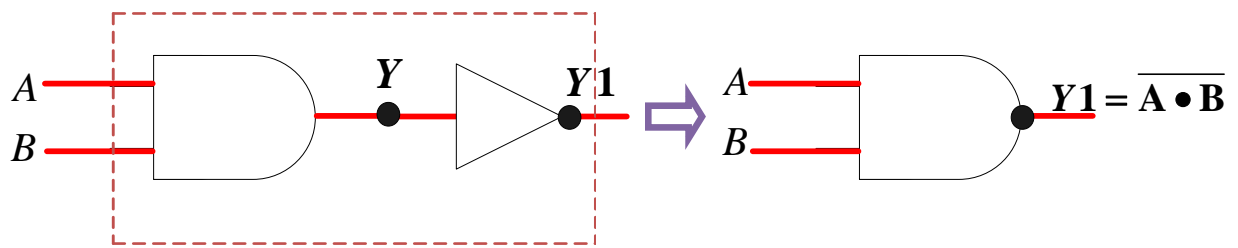

➤ The truth table of **NAND** gate (2-inputs, 1-output ) as the following:

inputs		outputs	
A	B	$Y = A \cdot B$	$Y1 = \overline{A \cdot B}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


**e) NOR gate (Not OR gate):**

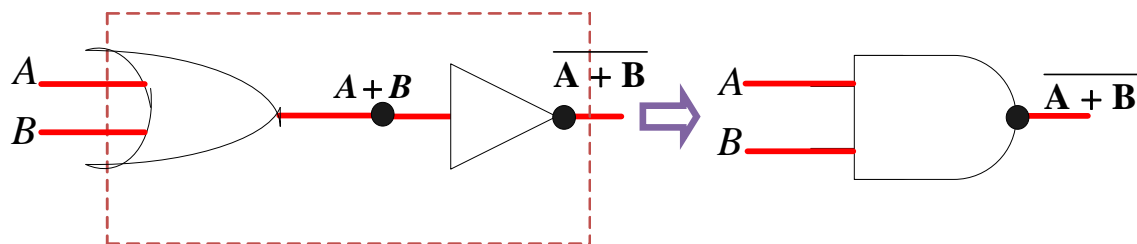

The truth table of **NOR** gate (2-inputs, 1-output ) as the following:

inputs		outputs	
A	B	$A + B$	$\overline{A + B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

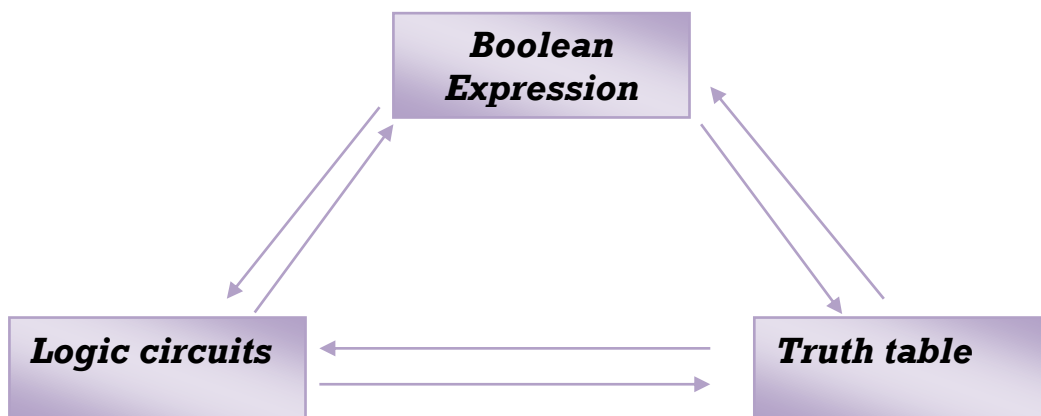**2. Relationships between Boolean expression, truth tables and logic circuits**




- If one is given, we can get the other.

**To draw a circuit from a Boolean expression:**

- ✓ From the left, make an **input line** for each variable.
- ✓ Next, put a **Not** gate in for each variable, that appears negated in the expression.
- ✓ Still working, from left to right.


**Example 1:-**  $Z = A\bar{B}$

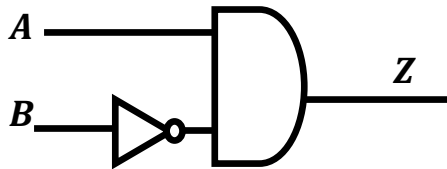

**Precedence of operators:**

1. Parenthesis
2. NOT
3. AND
4. OR

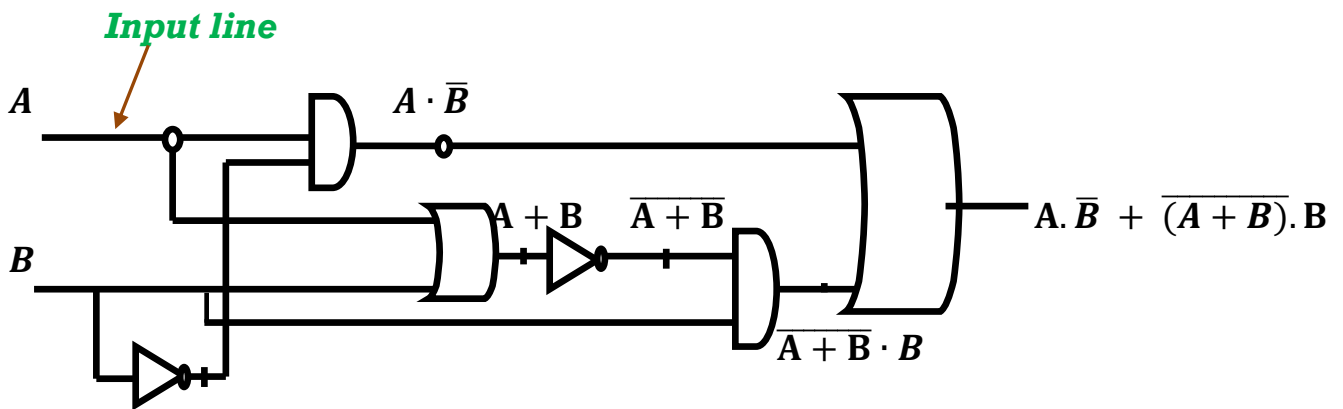**Example 2:-**  $A \cdot \bar{B} + \overline{(A + B)} \cdot B$



**3. Logic gate's postulates, laws and properties**

- Postulates are used to deduce the rules, theorems and properties.

**a) Postulates of Boolean algebra**

Postulate	For OR Gate	For AND Gate
<b>P1</b>	$A + 0 = A$	$A \cdot 1 = A$
<b>P2</b>	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
<b>P3</b>	$A + B = B + A$	$A \cdot B = B \cdot A$
<b>P4</b>	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + B \cdot C = (A + B) \cdot (A + C)$

**Duality principle**

- **Duality principle** states that every algebraic expression is deducible if *the operators and the identity elements are interchanged.*

**Identity elements:**

0 for or gate

1 for and gate

## b) Boolean algebra theorems:

➤ There are six theorems of Boolean algebra:

Theorem	For OR Gate	For AND Gate
<b>T1:</b> <i>Idempotent laws</i>	$A + A = A$	$A \cdot A = A$
<b>T2:</b> <i>operations with 0 and 1</i>	$A + 1 = 1$	$A \cdot 0 = 0$
<b>T3:</b> <i>associative laws</i>	$A + (B + C) = (A + B) + C$	$A \cdot (B \cdot C) = (A \cdot B) \cdot C$
<b>T4:</b> <i>de Morgan laws (inversion law)</i>	$\overline{A + B} = \bar{A} \cdot \bar{B}$	$\overline{A \cdot B} = \bar{A} + \bar{B}$
<b>T5:</b> <i>Absorption laws</i>	$A + A \cdot B = A$	$A \cdot (A + B) = A$
<b>T6:</b> <i>involution law</i>	$\overline{\bar{A}} = A$	

➤ To *proof* these theorems and other logic expressions, we can use *two ways*:

[1] **Truth table**

**Example 1: proof that  $A + A \cdot B = A$**

A	B	$A \cdot B$	$A + A \cdot B$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

**Example 2: verify the de Morgan's laws using a truth table.**


A	B	$\bar{A}$	$\bar{B}$	$A + B$	$\overline{A + B}$	$\bar{A} \cdot \bar{B}$	$A \cdot B$	$\overline{A \cdot B}$	$\bar{A} + \bar{B}$	
0	0	1	1	0	1	1	0	1	1	
0	1	1	0	1	0	0	0	1	1	
1	0	0	1	1	0	0	0	1	1	
1	1	0	0	1	0	0	1	0	0	
					$\overline{A + B} = \bar{A} \cdot \bar{B}$					
							$\overline{A \cdot B} = \bar{A} + \bar{B}$			

**Some Details:**

- The duality principle is formed by *replacing AND with OR, OR with AND, 0 with 1, 1 with 0, variables and complements are left unchanged.*
- de Morgan's laws Allow us to *convert between types of gates*; we can generalize them to **n** variables:

$$\overline{(x_1 + x_2 + x_3 + \dots + x_n)} = \overline{x_1} \cdot \overline{x_2} \cdot \overline{x_3} \cdot \dots \cdot \overline{x_n}$$
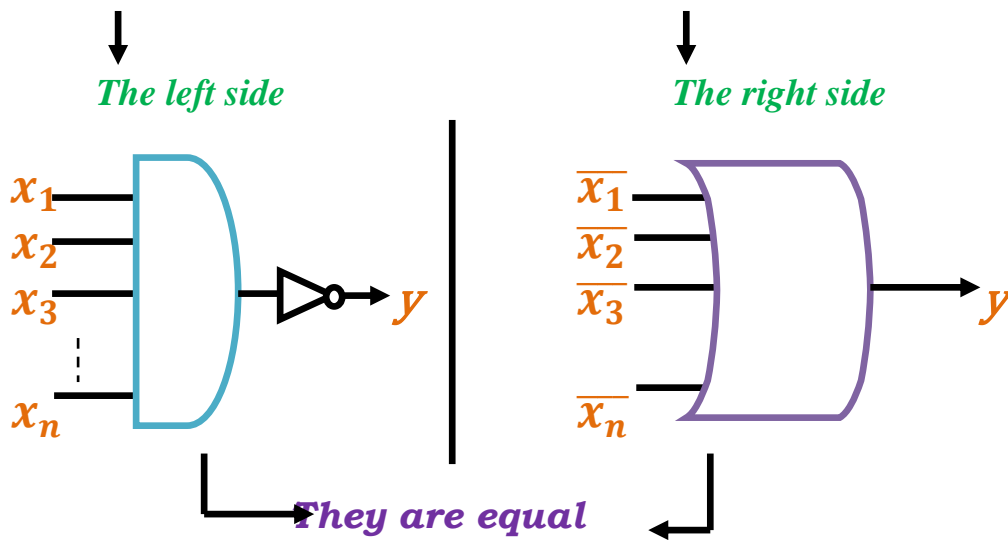
$$\overline{(x_1 x_2 x_3 \dots x_n)} = \overline{x_1} + \overline{x_2} + \overline{x_3} + \dots + \overline{x_n}$$



**[2] Algebraically using basic theorems.**

**Example 1: verify that**

**a)  $A + A \cdot B = A$**

**b)  $A(A + B) = A$**

**Proof (a):**

$$A + A \cdot B = A \cdot 1 + A \cdot B = A(1 + B) = A \cdot 1 = A$$

**Proof (b):**


$$A(A + B) = A \text{ by duality.}$$

**Example 2**

**a)  $(\overline{A} + 0) \overline{E} + 1 = 1$**

**b)  $(\overline{A} + 0) \overline{(\overline{A} + 0)} = 0$**

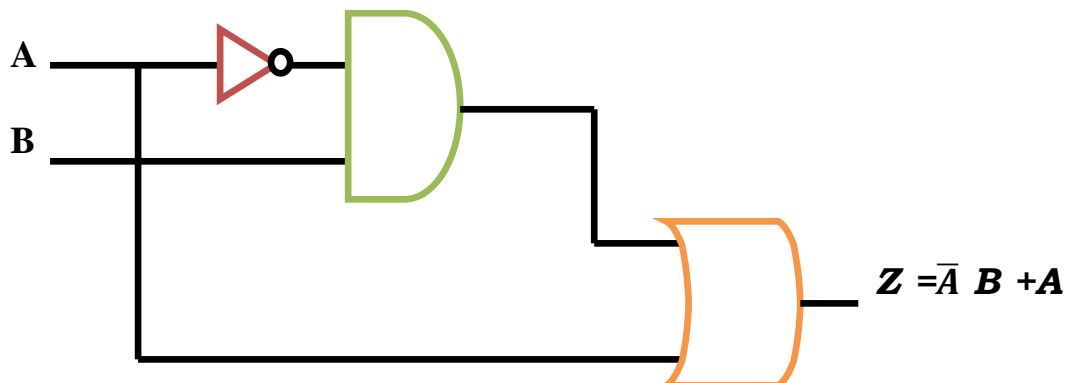**c) An input  $A$  is inverted and applied to an **AND** gate. The other input is  $B$ . the output of the **AND** gate is applied to an **OR** gate.  $A$  is the second input to **OR** gate. *Draw the logic circuit and the truth table.***



<i>A</i>	<i>B</i>	<i>Z</i>
0	0	0
0	1	1
1	0	1
1	1	1

*Truth table*

**d)** Proof the following Boolean expression "*Theorems*".

a)  $X + XY = X$

*Proof:*

$$x + xy = x \cdot 1 + xy = x(1 + y) = x \cdot 1 = x$$

b)  $X(X + Y) = X$

*Proof:*

$$x(x + y) = x \cdot x + x \cdot y = x + xy = x(1 + y) = x \cdot 1 = x$$

c)  $X\bar{Y} + Y = X + Y$

*Proof:*

$$x\bar{y} + y = y + x\bar{y} = (y + x)(y + \bar{y}) = (y + x) \cdot 1 = y + x$$

*Homework: proof that*

a)  $(x + y)(x + \bar{y}) = x$

b)  $(x + \bar{y})y = xy$