

Digital System Design

Digital System Design Lecture 8

Boolean Algebra - II

Simplifying Logic Circuits

Objectives:

1. Deriving of logical expression from truth tables.
2. Logical expression simplification methods:
 - a. Algebraic manipulation.
 - b. Karnaugh map (k-map).

1. Deriving of logical expression from truth tables

Definitions:

Literal: *Non-complemented* or *complemented* version of a variable (A or \bar{A}).

Product term: a *series of literals* related to one another through the **AND** operator (Example: $A \cdot \bar{B} \cdot C$).

Sum term: A *series of literals* related to one another through the **OR** operator (Example: $(A + \bar{B} + \bar{C})$).

SOP form: (*Sum –of-products form*):

- The *logic-circuit simplification* require the logic expression to be in **SOP** form , for example:

$$AB + \bar{A}\bar{B}\bar{C} + \bar{C}\bar{D}$$

POS form (*product-of-sum form*):

- This form *sometimes* used in logic circuit, example:

$$(A + C) \cdot (C + \bar{D}) \cdot (\bar{B} + C)$$

- The methods of circuit simplification and design that will be used are based on **SOP** form.

Canonical and standard form

- *Product terms* that consist of the variables of function are called "**Canonical product terms**" or "**Minterms**".
- The term ABC is a *minterm* in a *three variable logic function*, but will be a non-minterm in a four variable logic function.
- *Sum terms* which contain all the variables of a Boolean function are called "**Canonical sum terms**" or "**Maxterms**".

Example: $A + \bar{B} + C$ is a *maxterm* in a *three variable logic function*.

- for two variables A and B , there are four combination: $\bar{A}\bar{B}, \bar{A}B, A\bar{B}, AB$ called minterms or standard products

A	B	Minterm
0	0	$\bar{A}\bar{B}$
0	1	$\bar{A}B$
1	0	$A\bar{B}$
1	1	AB

- for n variables there are 2^n minterms

Example: *minterms and maxterms for 3 variables:*

inputs			Minterm	Designation	Maxterm	Designation
A	B	C				
0	0	0	$\bar{A}\bar{B}\bar{C}$	$m0$	$A + B + C$	$M0$
0	0	1	$\bar{A}\bar{B}C$	$m1$	$A + B + \bar{C}$	$M1$
0	1	0	$\bar{A}B\bar{C}$	$m2$	$A + \bar{B} + C$	$M2$
0	1	1	$\bar{A}BC$	$m3$	$A + \bar{B} + \bar{C}$	$M3$
1	0	0	$A\bar{B}\bar{C}$	$m4$	$\bar{A} + B + C$	$M4$
1	0	1	$A\bar{B}C$	$m5$	$\bar{A} + B + \bar{C}$	$M5$
1	1	0	$AB\bar{C}$	$m6$	$\bar{A} + \bar{B} + C$	$M6$
1	1	1	ABC	$m7$	$\bar{A} + \bar{B} + \bar{C}$	$M7$

Two important properties:

- ❖ *Any Boolean function can be expressed as a sum of minterms.*
- ❖ *Any Boolean function can be expressed as a product of maxterms.*

Example: Majority function: (for 3 variables)

Output is one whenever majority of inputs is 1

inputs			Output	Minterms
A	B	C	F	SOP Form
0	0	0	0	-----
0	0	1	0	-----
0	1	0	0	-----
0	1	1	1	$\bar{A}BC$
1	0	0	0	-----
1	0	1	1	$A\bar{B}C$
1	1	0	1	$AB\bar{C}$
1	1	1	1	ABC

➤ Four product terms, because, there are 4 rows with a 1 output.

➤ **Final expression:**

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

inputs			Output	Maxterms
A	B	C	F	POS Form
0	0	0	0	$A + B + C$
0	0	1	0	$A + B + \bar{C}$
0	1	0	0	$A + \bar{B} + C$
0	1	1	1	-----
1	0	0	0	$\bar{A} + B + C$
1	0	1	1	-----
1	1	0	1	-----
1	1	1	1	-----

➤ Four sum terms, because, there are 4 rows with a 0 output.

➤ **Final expression:**

$$F = (A + B + C) \cdot (A + B + \bar{C}) \cdot (A + \bar{B} + C) \cdot (\bar{A} + B + C)$$

Derivation of logical expression form truth tables

Summary

- ✓ Sum-of-product (SOP) form.
- ✓ Product-of-sums (POS) form.
 - SOP form :

- Write an **AND** term for each input combination that produces a 1 output.
- Write the variable if its value is 1 , complement otherwise.
- **OR** the **AND** terms to get the final expression.

2. logical expression simplification methods:

Two basic methods:

a) Algebraic manipulation:

- Use *Boolean laws* to simplify the expression: (difficult to use and don't know if you have the simplified form.

b) Karnaugh map (k-map) method:

- *Graphical* method.
- *Ease* to use.
- Can be used to simplify logical expressions *with a few variables*.

a) Algebraic manipulation

Example 1:

Design a logic circuit that has three inputs, **A**, **B** and **C** and whose output will be **high** only when a majority of the input are high .(complete design procedure).

Solution:

Step 1: set up the truth table (see previous section)

Step 2: write the **AND** term for each case where the output is a **1** :(see previous section)

Step 3: write the sum-of-products expression for the output

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Step 4: simplify the output expression

- Find the *common* term(s): **ABC** -common term.
- Use the common term (**ABC**) to *factor* with other terms:


$$F = \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$

- Factoring the appropriate pairs of terms:

$$F = BC(\bar{A} + A) + AC(B + \bar{B}) + AB(\bar{C} + C)$$

$$F = BC + AC + AB$$

Step 5: implement the circuit for the final expression.

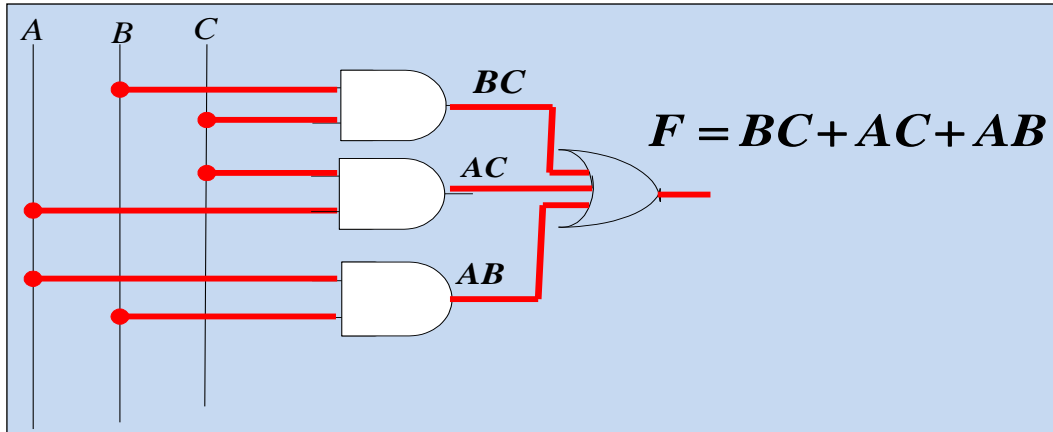

Example 2: simplify the Boolean function.

$$F = AB + \bar{A}C + BC$$

Solution:

$$F = AB + \bar{A}C + BC \cdot 1 \quad (\text{Common term})$$

$$= AB + \bar{A}C + BC(A + \bar{A})$$

$$= AB + ABC + \bar{A}C + \bar{A}BC$$

$$= AB(1 + C) + \bar{A}C(1 + B)$$

$$= AB + \bar{A}C \quad (\text{The result})$$

Example 3: simplify the following Boolean function to a minimum number of literals.

$$X = BC + \bar{A}C + AB + BCD$$

Solution:

$$X = BC(1 + D) + \bar{A}C + AB$$

$$= BC + \bar{A}C + AB = BC + A(\bar{C} + B)$$

Example 4: simplify the expression.

$$Z = A\bar{B}\bar{C} + A\bar{B}C + ABC$$

Solution: (the expression is in SOP form)

$$Z = A\bar{B}(\bar{C} + C) + ABC$$

$$= A\bar{B}(1) + ABC = A\bar{B} + ABC$$

$$Z = A(\bar{B} + BC) = A(\bar{B} + B)(\bar{B} + C) = A(\bar{B} + C)$$

Example 5: simplify the expression.

$$Z = \bar{A}C(\overline{ABD}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

Solution:

✓ First, use Demorgan's theorem on the first term:

$$Z = \bar{A}C(\bar{A} + \bar{B} + \bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$Z = \bar{A}C(A + \bar{B} + \bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

✓ Multiply, we get:

$$Z = \bar{A}CA + \bar{A}C\bar{B} + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

($\bar{A}A = 0$) then

$$Z = \bar{A}B\bar{C} + \bar{A}C\bar{D} + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

✓ Check for the largest common factor between any two or more product terms:

$$Z = \bar{B}C(\bar{A} + A) + \bar{A}\bar{D}(C + B\bar{C})$$

\downarrow
 1

\downarrow
 $C + B$

✓ We get:

$$Z = \bar{B}C + \bar{A}\bar{D}(B + C)$$

✓ The result can be obtained with other choices

Example 6: Find the complement of the following Boolean function:

$$Z = (B\bar{C} + \bar{A}D)(\bar{A}\bar{B} + C\bar{D})$$

Solution:

✓ Use Demorgan's theorem :

$$\begin{aligned} \bar{Z} &= \overline{(B\bar{C} + \bar{A}D)(\bar{A}\bar{B} + C\bar{D})} \\ &= \overline{(B\bar{C} + \bar{A}D)} + \overline{(\bar{A}\bar{B} + C\bar{D})} \\ &= \overline{B\bar{C}} \cdot \overline{\bar{A}D} + \overline{\bar{A}\bar{B}} \cdot \overline{C\bar{D}} \\ &= (\bar{B} + \bar{\bar{C}}) \cdot (\bar{\bar{A}} + \bar{D}) + (\bar{\bar{A}} + \bar{\bar{B}})(\bar{C} + \bar{\bar{D}}) \\ &= (\bar{B} + C) \cdot (A + \bar{D}) + (\bar{A} + B) \cdot (\bar{C} + D) \end{aligned}$$

✓ It's not in standard form

Example 7:

Express the following function in a sum of minterms and product of maxterms.

$$Z = (AB + C)(B + AC)$$

a) **Sum of minterms:**

✓ Multiply, we get:

$$\begin{aligned} Z &= ABB + AABC + BC + ACC \\ &= AB + ABC + BC + AC \\ &= ABC + AB(C + \bar{C}) + BC(A + \bar{A}) + AC(B + \bar{B}) \\ &= ABC + ABC + ABC\bar{C} + ABC + \bar{A}BC + ABC + A\bar{B}C \\ Z &= \color{red}{ABC\bar{C}} + \color{red}{\bar{A}BC} + \color{red}{\bar{A}BC} + \color{red}{A\bar{B}C} \end{aligned}$$

$C + \bar{C} = 1$
$A + \bar{A} = 1$
$B + \bar{B} = 1$
$A + A = A$

$$\begin{matrix} \downarrow & \downarrow & \downarrow & \downarrow \\ m6 & m7 & m3 & m5 \end{matrix}$$

✓ So, we can write:

$$Z(A, B, C) = \sum m(3, 5, 6, 7)$$

inputs			Minterm	z
A	B	C		
0	0	0	m0	0
0	0	1	m1	0
0	1	0	m2	0
0	1	1	m3	1
1	0	0	m4	0
1	0	1	m5	1
1	1	0	m6	1
1	1	1	m7	1

Sum of minterms

b) Sum of maxterms

✓ Using distributive law:

$$\underline{(A + BC) = (A + B)(A + C)}$$

✓ In the

$$Z = (AB + C)(B + AC)$$

✓ We get:

$$= (A + C)(B + C)(B + A)(B + C)$$

$$= (A + B)(B + C)(C + A)$$

$$Z = (A + B)(B + C)(C + A)$$

- In $A + B$ we need C
- In $B + C$ we need A
- In $C + A$ we need B

✓ We can write

$$(A + B) = (A + B + 0) = (A + B + C\bar{C})$$

$$(A + B) = (A + B + C)(A + B + \bar{C})$$

$$(B + C) = (B + C + 0) = (B + C + A)(B + C + \bar{A})$$

$$(C + A) = (C + A + B)(C + A + \bar{B})$$

✓ Substitute all of these term in Z , we get:

$$Z = (A + B)(B + C)(C + A)$$

$$= (A + B + C)(A + B + \bar{C})(B + C + A)(B + C + \bar{A})(C + A + B)(C + A + \bar{B})$$


$$Z = (A + B + C)(A + B + \bar{C})(B + C + \bar{A})(C + A + \bar{B})$$

$$Z = (A + B + C)(A + B + \bar{C})(\bar{A} + B + C)(A + \bar{B} + C)$$

$$Z = M_0 \cdot M_1 \cdot M_4 \cdot M_2$$

inputs			Z	Maxterm
A	B	C		
0	0	0	0	M ₀
0	0	1	0	M ₁
0	1	0	0	M ₂
0	1	1	1	M ₃
1	0	0	0	M ₄
1	0	1	1	M ₅
1	1	0	1	M ₆
1	1	1	1	M ₇

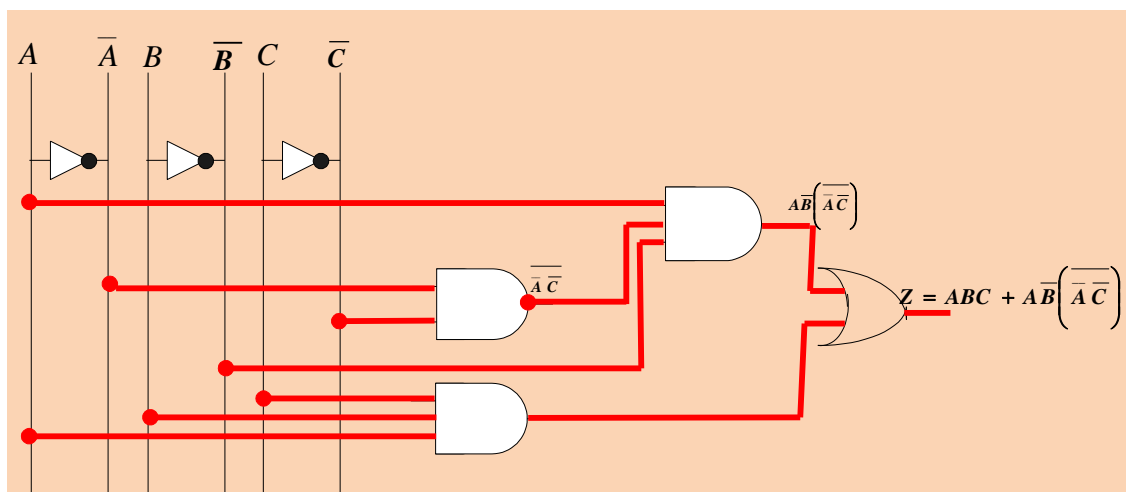Example 8: simplify the logic circuit shown in the following figure.



Solution:

✓ The output of the circuit is

$$Z = abc + \bar{a}\bar{b}\bar{c}$$

✓ Using Demorgan's law and multiply out all terms:

$$Z = abc + \bar{a}\bar{b}(\bar{a} + \bar{c})$$

$$Z = abc + a\bar{b}(a + c)$$

$$Z = abc + a\bar{b}a + a\bar{b}c$$

$$Z = abc + a\bar{b}a + a\bar{b}c$$

$$Z = abc + a\bar{b} + a\bar{b}c$$

SOP Form

$$Z = abc + a\bar{b} + a\bar{b}c$$

$$Z = ac(b + \bar{b}) + a\bar{b}$$

$$Z = ac \cdot 1 + a\bar{b} = ac + a\bar{b} = a(c + \bar{b})$$

