

Digital System Design

Lecture 9

Karnaugh Map Methods- I

Objectives:

1. Karnaugh Map definition.
2. Karnaugh map construction.
 - Two variables K-maps.
 - Three variables K-maps.
 - Four variables K-maps.
3. Summary


1) Karnaugh map definition

- The karnaugh map (k-map) is a *graphical tool* used to simplify (minimize) the logic functions, so that it can be implemented with minimum number of gates (minimum number of product terms and minimum number of literals).
- The K-map is used to *convert* a truth table to its corresponding logic circuit.

2) Karnaugh map construction

- **Two variables K-maps.**
 - A two- variable function has four possible minterms, we can rearrange these minterms into a karnaugh map:


x	y	Minterms
0	0	$\bar{x}\bar{y}$
0	1	$\bar{x}y$
1	0	$x\bar{y}$
1	1	xy

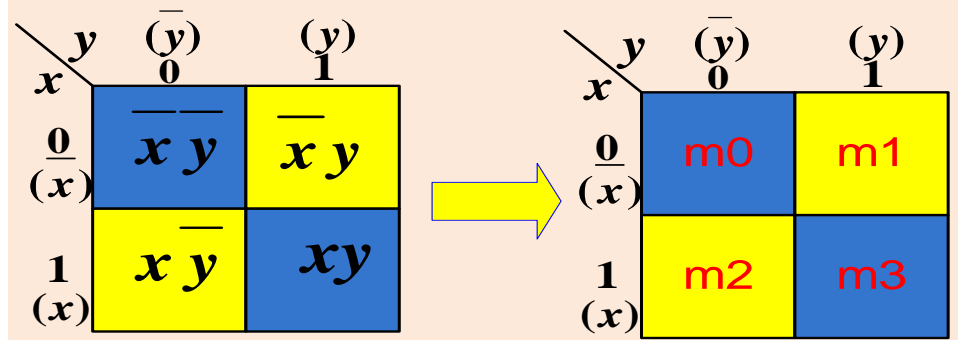

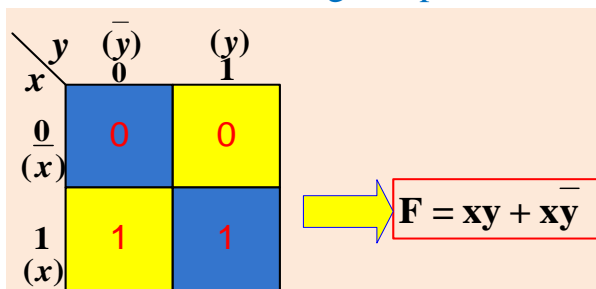Example:

$$F = xy + x\bar{y}$$

- The Karnaugh map for this function will be:



Note: we can easily from the k-map see which *minterms contain common literal*:

- Minterms on the left and right sides contain \bar{y} and y respectively.

- Minterms in the top and bottom rows contain \bar{x} and x respectively.

		\bar{y}		y	
		0	1	0	1
x	0	$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	xy
	1	$x\bar{y}$	xy	$\bar{x}y$	xy

Note: each case in the truth table corresponds to a square in the K-map

- Karnaugh map simplification:**

- The K-map squares labeled so that *horizontally adjacent* square differ only in one variable.

Example 1:- Imagine a two-variable sum of minterms, both of these minterms appear in the top row of a karnaugh map, which means that they both contain the literal \bar{x} .

		\bar{y}		y	
		0	1	0	1
x	0	$\bar{x}\bar{y}$	$\bar{x}y$	$x\bar{y}$	xy
	1	$x\bar{y}$	xy	$\bar{x}y$	xy

$F = \bar{x}\bar{y} + \bar{x}y = \bar{x}(y + \bar{y}) = x$

Example 2: $f = \bar{x}y + xy$ -minimize it using K-map.

Solution:

- Both minterms appear in the right- side where y is uncomplemented.
- Thus, we can reduce $\bar{x}y + xy =$ just to y .


		\bar{y}		y	
		0	1	0	1
x	0	0	1	0	1
	1	0	1	0	1

$F = y$

$$f = \bar{x}y + xy = y(x + \bar{x}) = y$$

Example 3: $z = \bar{x}\bar{y} + \bar{x}y + xy$ –minimize it using K-map.

Solution:

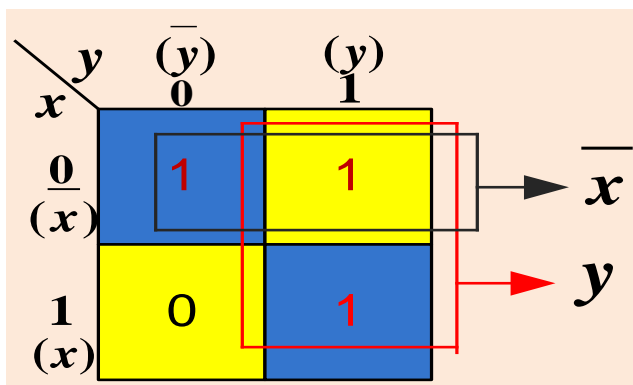


- We have $\bar{x}\bar{y} + \bar{x}y$ in the top row, corresponding to \bar{x}
- There's also $\bar{x}y + xy$ in the right side corresponding to y .
- The result $z = \bar{x} + y$.

Using algebraic simplification:


$$z = \bar{x}\bar{y} + \bar{x}y + xy = \bar{x}(\bar{y} + y) + xy = \bar{x} + xy = (x + \bar{x})(\bar{x} + y) = \bar{x} + y$$

• **Three- variables K-map**

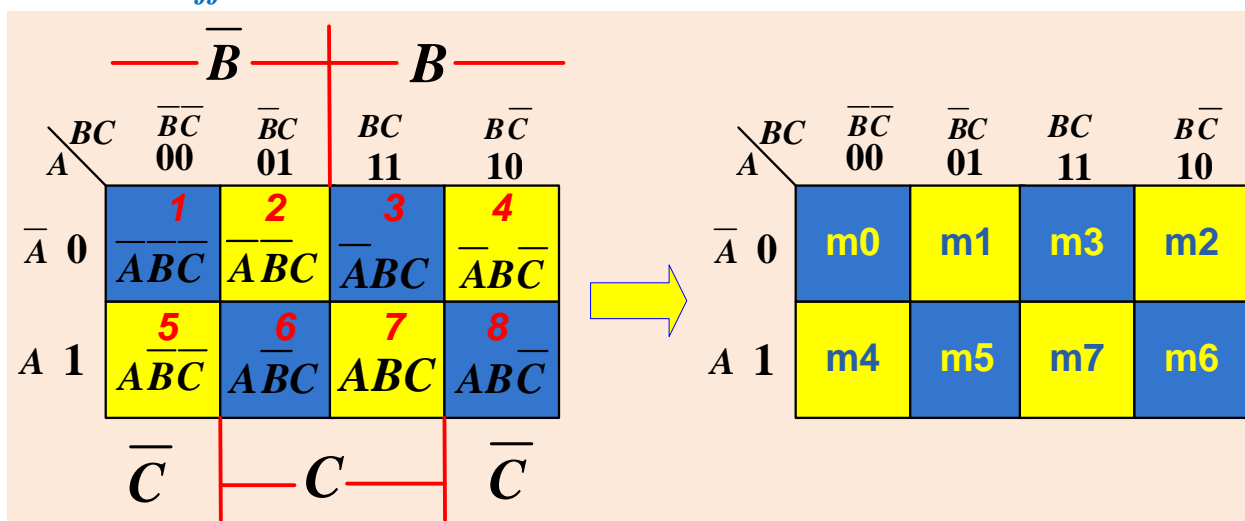- For $F(A, B, C)$ there are $2^3 = 8$ minterms.
- **Representation** truth table using K-map
 - *Different versions:*



Or

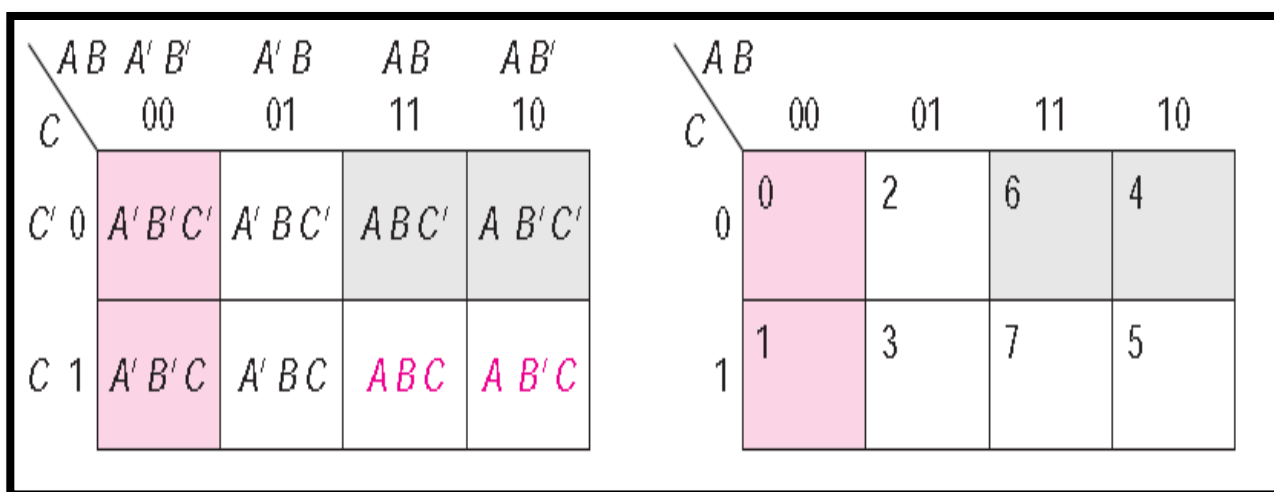

Grouping (ordering, looping)

- The groups can be 2, 4, or 8 adjacent squares:
 - ✓ 2 squares → 1 variable can be canceled.
 - ✓ 4 squares → 2 variables can be canceled.
 - ✓ 8 squares → 3 variables can be canceled.


➤ Examples:-

Squares	Common Literal (s)
(1) and (2)	$\bar{A} \bar{B}$
(2) and (3)	$\bar{A} C$
(1) and (4)	$\bar{A} \bar{C}$
(1), (2), (5) and (6)	\bar{B}
(3), (4), (7) and (8)	B
(1), (2), (3) and (4)	\bar{A}
(5), (6), (7) and (8)	A
(1), (5), (4) and (8) (Wrapping case is also adjacent)	\bar{C}

- To *proof* the wrapping case (the last one in the table) algebraically, we can write:

$$\begin{aligned}
 F &= \bar{A} \bar{B} \bar{C} + A \bar{B} \bar{C} + \bar{A} B \bar{C} + A B \bar{C} \\
 &= \bar{C}(\bar{A} \bar{B} + A \bar{B} + \bar{A} B + AB) \\
 &= \bar{C}(\bar{B}(\bar{A} + A) + B(\bar{A} + A)) \\
 &= \bar{C}(\bar{B} + B) = \bar{C}
 \end{aligned}$$

- "Adjacency" includes wrapping around the left and right side.

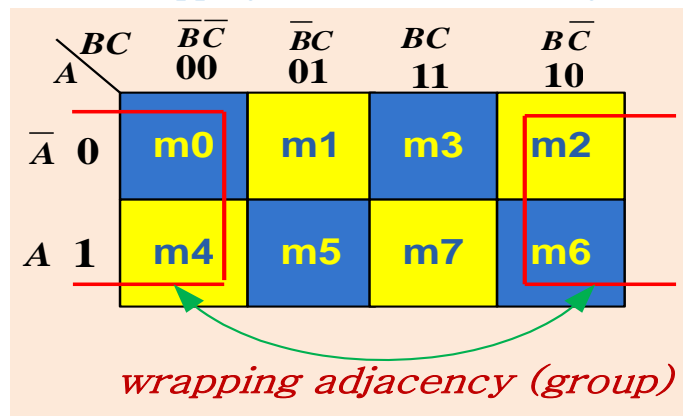

Example 1: Simplify the following logical function using K-map.

$$F(x, y, z) = xy + \bar{y}z + xz$$

Solution:

Step 1: the expression must be in a sum of minterms form, so we should convert it:(two ways to do that):

1. Using logical rules (algebraically).

$$\begin{aligned} F &= xy + \bar{y}z + xz \\ &= xz(z + \bar{z}) + \bar{y}z(x + \bar{x}) + xz(y + \bar{y}) \\ &= xyz + xy\bar{z} + x\bar{y}z + \bar{x}\bar{y}z + \cancel{xyz} + \cancel{x\bar{y}z} \\ &= xyz + xy\bar{z} + x\bar{y}z + \bar{x}\bar{y}z \\ &= m_1 + m_5 + m_6 + m_7 \end{aligned}$$

2. Make the truth table and read the minterms.

$$F = xy + \bar{y}z + xz$$

inputs			Output	Terms replacement
x	y	z	$F(x, y, z)$	
0	0	0	0	
0	0	1	1	$\bar{y}z$
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	xz and $\bar{y}z$
1	1	0	1	xy
1	1	1	1	xy and xz

$$\begin{aligned} F(x, y, z) &= \bar{x}\bar{y}z + x\bar{y}z + xy\bar{z} + xyz \\ &= m_1 + m_5 + m_6 + m_7 \end{aligned}$$

Step 2: fill one's (for the minterms) in karnaugh map; zero's for other squares.

x \ yz	00	01	11	10
0	0	1	0	0
1	0	1	1	1

$\bar{y}z$ xy

Step 3: grouping (looping):

2 groups: (m1) and (m5)
(m6) and (m7)

Step 4: simplify:

$$F = xy + \bar{y}z$$

➤ To **proof** the result:

$$\begin{aligned}
 F &= \bar{x}\bar{y}z + x\bar{y}z + xyz + xy\bar{z} \\
 &= \bar{y}z(x + \bar{x}) + xy(z + \bar{z}) \\
 &= \bar{y}z + xy
 \end{aligned}$$

Grouping the minterms:-


- Grouping together all the **1_s** in the K-map.
 - **Make rectangles** of 2^n (1, 2, 4, ...).
 - All the **1_s** in the map should be included in at least one rectangle.
 - **Do not** include any of the **0_s**.
 - Each group corresponds to one product term.
 - Make each rectangle **as large as possible**.
 - We can **overlap the rectangles**, if that makes them larger.

Example 2: Simplify the following logical function using K-map.

$$Z = AB + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}$$

Solution:


$$Z = AB + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + AB\bar{C} + \bar{A}\bar{B}\bar{C}$$

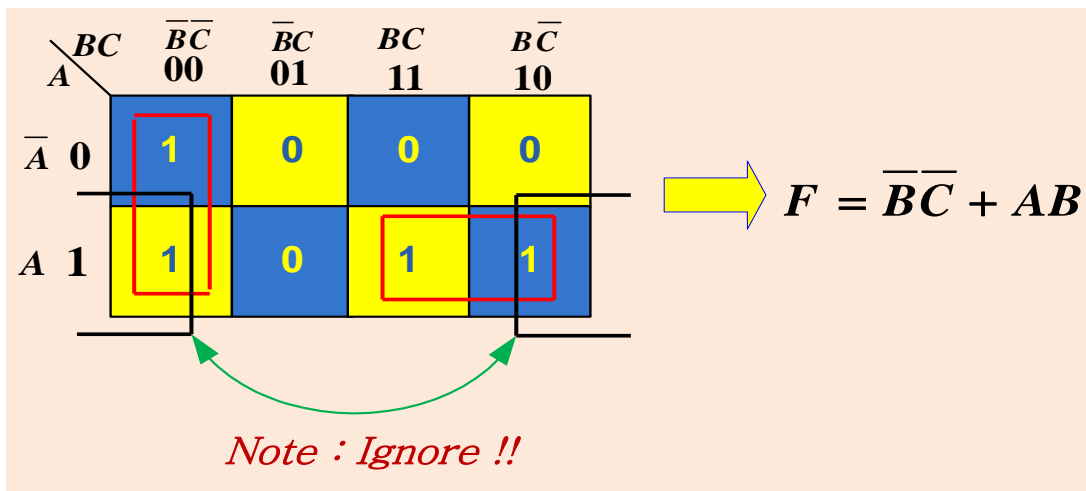

Example 3: Simplify the following logical function using K-map.

$$Z = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + ABC$$

Solution:

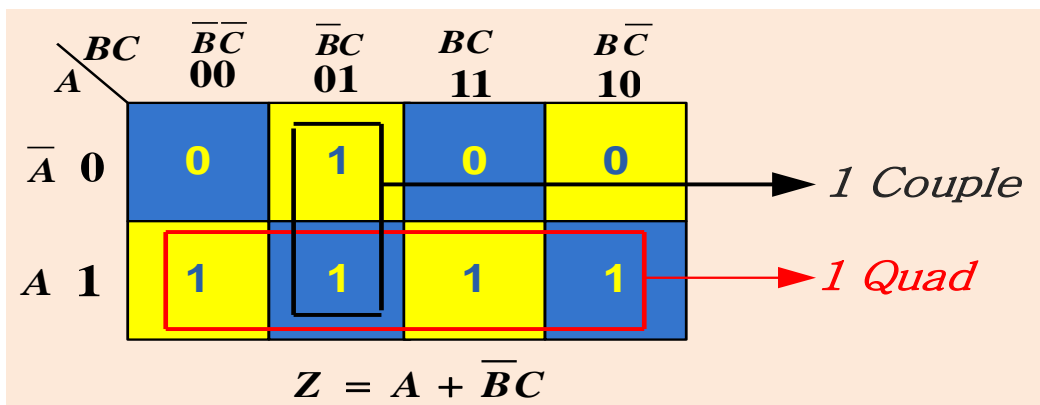

Quad:

$$\begin{aligned} \overline{A}BC + A\overline{B}\overline{C} + AB\overline{C} + ABC &= A(\overline{B}C + \overline{B}\overline{C} + B\overline{C} + BC) \\ &= A(\overline{B}(C + \overline{C}) + B(\overline{C} + C)) = A(\overline{B} + B) = \mathbf{A} \end{aligned}$$

Couple:

$$\overline{A}\overline{B}C + A\overline{B}C = \overline{B}C(A + A) = \mathbf{\overline{B}C}$$