



*Philadelphia University*  
*Faculty of Engineering*

## **Marking Scheme**

Exam Paper

BSc CE

### **Logic Circuits (630211)**

Final Exam

Second semester

Date: 02/06/2019

Section 1

Weighting 40% of the module total

Lecturer:

Dr. Qadri Hamarsheh

Coordinator:


Dr. Qadri Hamarsheh

Internal Examiner:

Dr. Naser Halasa



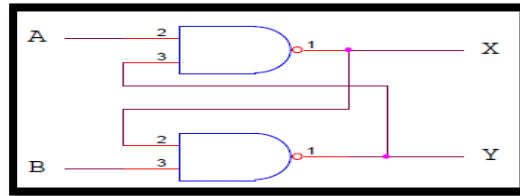9) If the input combination  $\mathbf{A=0, B=1}$  is applied to this circuit, the (steady state) output will be:



a)  $\mathbf{X=0, Y=0}$

b)  $\mathbf{X=0, Y=1}$

c)  $\mathbf{X=1, Y=0}$

d)  $\mathbf{X=1, Y=1}$

10) The characteristic equation for the T-Flip Flop is:

a)  $\mathbf{Q(t+1) = T \cdot \bar{Q} + \bar{T} \cdot Q}$

b)  $\mathbf{Q(t+1) = \bar{T} \cdot \bar{Q} + T \cdot Q}$

**Question 2** This question is attributed with **6 marks** if answered properly; the answers are the following:

a)

(1.5 marks)

**Solution**

**Three weighted Binary codes codes are:**

1. **BCD (8421)**
2. **6311**
3. **2421**
4. **642-3**
5. **84-2-1**

b)

(2.5 marks)

**Solution**

$$\begin{aligned}
 D &= (\overline{AB + \bar{C}})(A + C) = (\overline{ABC})(A + C) = [(A + \bar{B})C](A + C) \\
 &= (A + \bar{B})(AC + CC) = (A + \bar{B})(AC + C) = AAC + AC + A\bar{B}C + \bar{B}C \\
 &= AC + AC + \bar{B}C(A + 1) = AC + \bar{B}C(1) = AC + \bar{B}C \\
 &= (A + \bar{B})C
 \end{aligned}$$

c)

(2 marks)

**Solution**

$$\begin{aligned}
 D &= A(B + \bar{B}) + (A + \bar{A})\bar{B}C = AB + A\bar{B} + A\bar{B}C + \bar{A}\bar{B}C \\
 D &= AB(C + \bar{C}) + A\bar{B}(C + \bar{C}) + A\bar{B}C + \bar{A}\bar{B}C \\
 &= ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}\bar{B}C \\
 D &= \bar{A}\bar{B}C + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC \\
 &= m_1 + m_4 + m_5 + m_6 + m_7 = \Sigma(1, 4, 5, 6, 7)
 \end{aligned}$$

**Question 3** This question is attributed with 7 marks if answered properly; the answers are the following:

a) (4 marks)

**Solution**

Inputs			Outputs	
X	Y	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth table for the full adder

$$\left\{ \begin{aligned} S &= C_{in} \oplus (X \oplus Y) \\ C_{out} &= C_{in} \cdot (X \oplus Y) + XY \end{aligned} \right\}$$

**Proof:**

**The sum:**


$$\begin{aligned} S &= \bar{X}\bar{Y}C_{in} + \bar{X}Y\bar{C}_{in} + X\bar{Y}C_{in} + XY\bar{C}_{in} \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\bar{X}\bar{Y} + XY) \\ &= \bar{C}_{in}(\bar{X}Y + X\bar{Y}) + C_{in}(\overline{\bar{X}\bar{Y}} + \overline{XY}) \end{aligned}$$

$$S = C_{in} \oplus (X \oplus Y)$$

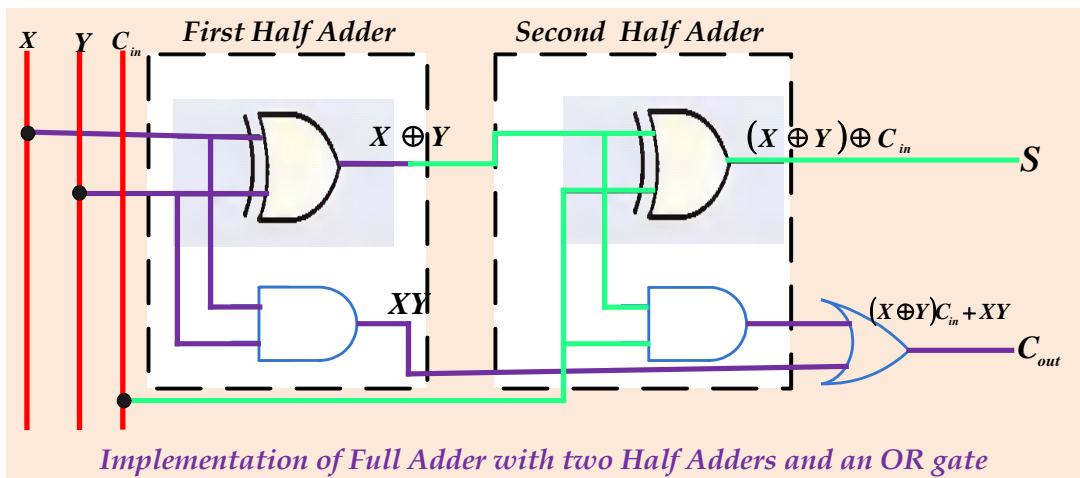**The carry output:**

$$\begin{aligned} C_{out} &= \bar{X}Y C_{in} + X\bar{Y} C_{in} + XY C_{in} + XY \bar{C}_{in} \\ &= C_{in}(\bar{X}Y + X\bar{Y}) + XY(C_{in} + \bar{C}_{in}) \end{aligned}$$

$$C_{out} = C_{in} \cdot (X \oplus Y) + XY$$



b) (3 marks)

**Solution**

CHARACTERISTIC EQUATION	EXCITATION TABLE																				
$Q_{(next)} = S + R'Q$ $SR = 0$	<table border="1"> <thead> <tr> <th>Q</th> <th>Q<sub>(next)</sub></th> <th>S</th> <th>R</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Q	Q <sub>(next)</sub>	S	R	0	0	0	X	0	1	1	0	1	0	0	1	1	1	X	0
	Q	Q <sub>(next)</sub>	S	R																	
	0	0	0	X																	
	0	1	1	0																	
1	0	0	1																		
1	1	X	0																		
$Q_{(next)} = JQ' + K'Q$	<table border="1"> <thead> <tr> <th>Q</th> <th>Q<sub>(next)</sub></th> <th>J</th> <th>K</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>X</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>X</td> </tr> <tr> <td>1</td> <td>0</td> <td>X</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>X</td> <td>0</td> </tr> </tbody> </table>	Q	Q <sub>(next)</sub>	J	K	0	0	0	X	0	1	1	X	1	0	X	1	1	1	X	0
	Q	Q <sub>(next)</sub>	J	K																	
	0	0	0	X																	
	0	1	1	X																	
1	0	X	1																		
1	1	X	0																		

**Question 4** This question is attributed with **7 marks** if answered properly; the answers are the following:

a)

(3 marks)

**Solution**

$$F1 = \overline{(X + Z)} + XYZ = X'Z' + XYZ = X'Z'(Y + Y') + XYZ = X'Y'Z' + X'YZ' + XYZ$$


$$= m0 + m2 + m7$$

$$F2 = \overline{(X + Z)} + X'YZ = X'Z' + X'YZ = X'Z'(Y + Y') + X'YZ = X'Y'Z' + X'YZ' + X'YZ$$

$$= m0 + m2 + m3$$

$$F3 = XY'Z + \overline{(X + Z)} = XY'Z + X'Z' = XY'Z + X'Z'(Y + Y') = XY'Z + X'Y'Z' + X'YZ'$$


$$= m5 + m0 + m2$$

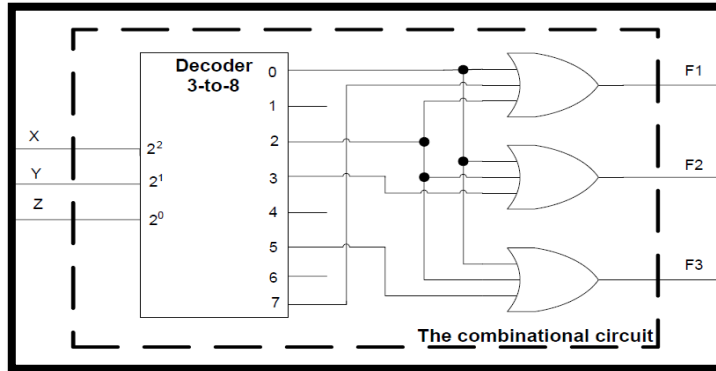

b)

(2 marks)


**Solution**

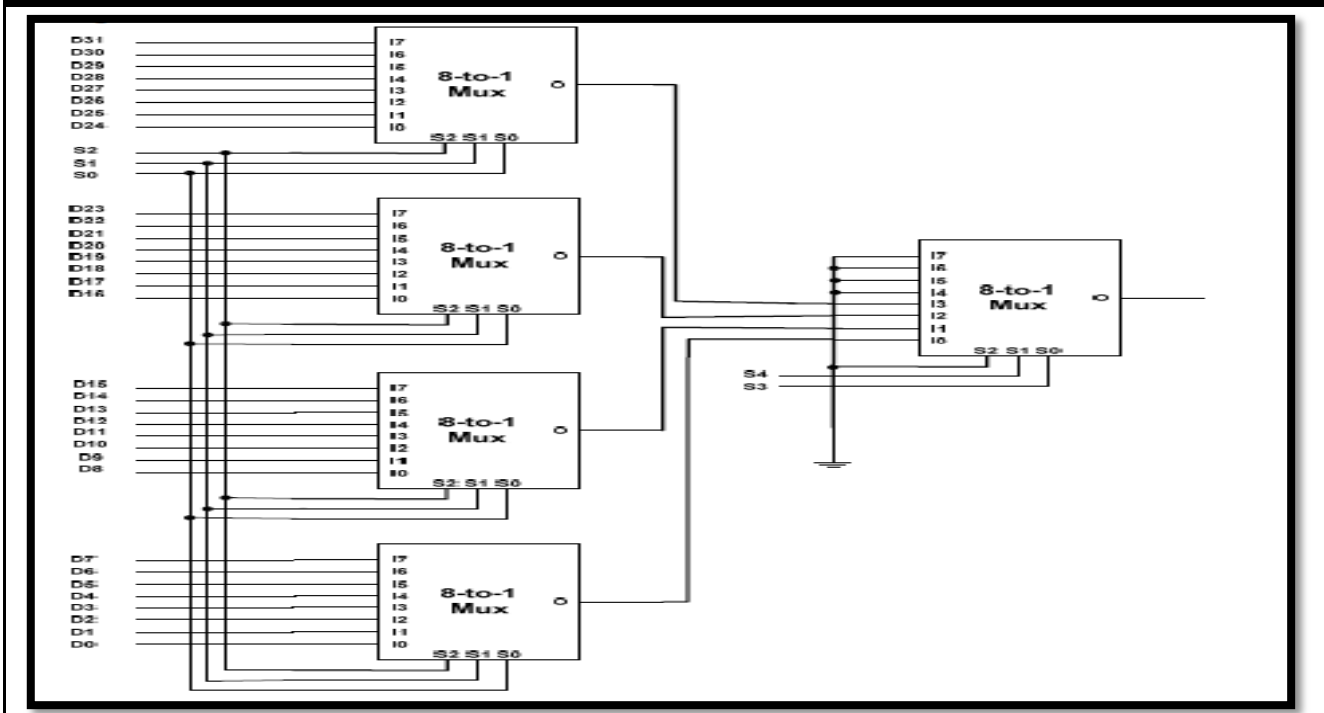

c)

(2 marks)

**Solution**

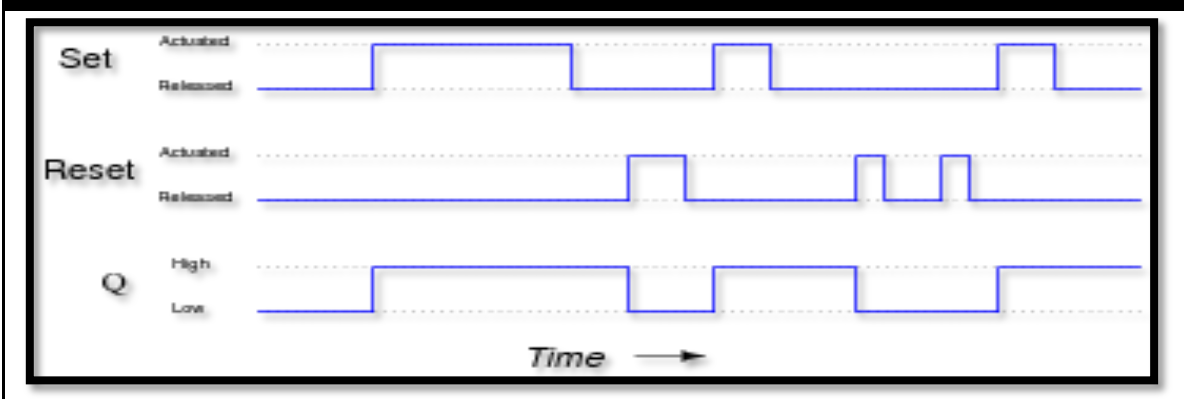




**Question 6** This question is attributed with *5 marks* if answered properly; the answers are the following:

**Solution**


Present State		Input	Next State		Flip-Flop Inputs			
A	B	x	A	B	$J_A$	$K_A$	$J_B$	$K_B$
0	0	0	0	0	0	X	0	X
0	0	1	0	1	0	X	1	X
0	1	0	1	0	1	X	X	1
0	1	1	0	1	0	X	X	0
1	0	0	1	0	X	0	0	X
1	0	1	1	1	X	0	1	X
1	1	0	1	1	X	0	X	0
1	1	1	0	0	X	1	X	1

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

(2 marks)

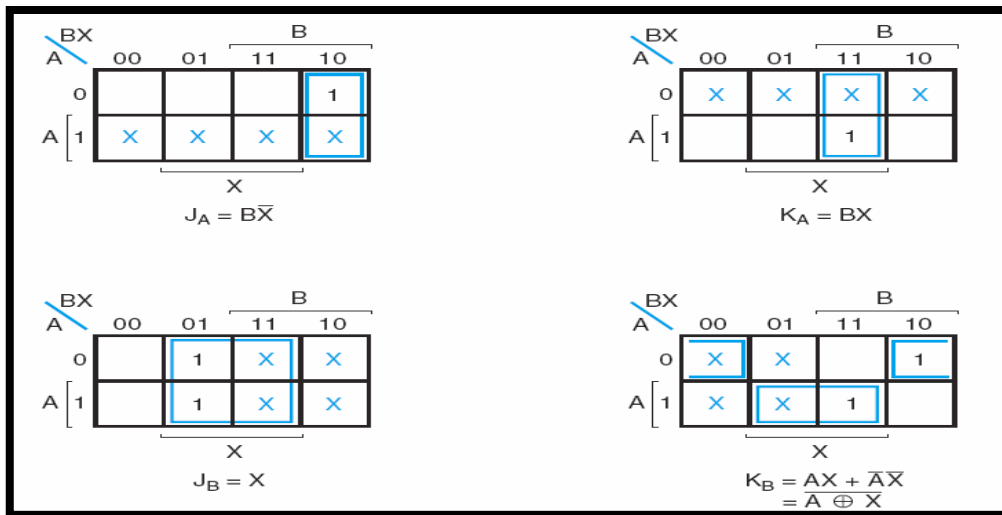

(2 marks)

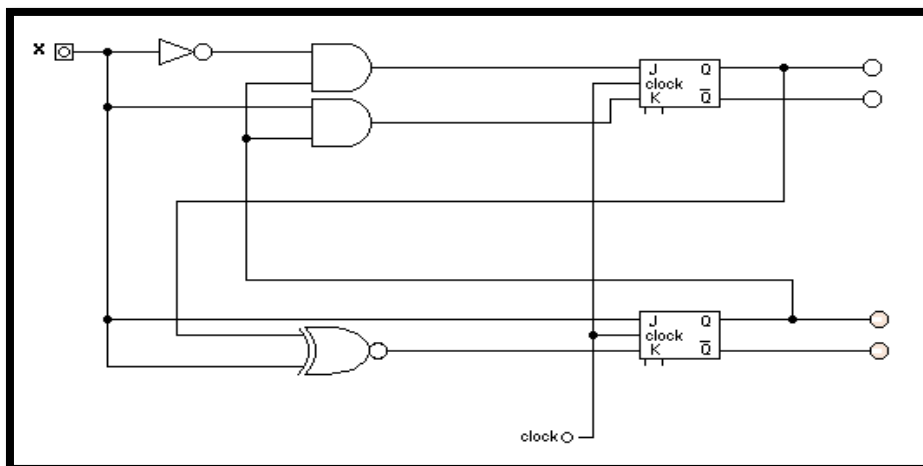

(1 mark)