



Philadelphia University

Faculty of Engineering

Marking Scheme

Exam Paper

BSc CE

Logic Circuits (630211)

Final Exam

First semester

Date: 28/01/2020

Section 1

Weighting 40% of the module total

Lecturer:

Dr. Qadri Hamarsheh

Coordinator:

Dr. Qadri Hamarsheh

Internal Examiner:

Eng. Anis Nazer

Marking Scheme Logic Circuits (630211)

The presented exam questions are organized to overcome course material through 6 questions. The *all questions* are compulsory requested to be answered.

Marking Assignments

Question 1 This question is attributed with **10 marks** if answered properly; the answers are the following:
Identify the choice that best completes the statement or answers the question.


1) The **binary** number **101110101111010** can be written in **octal** as _____.

- a) **51562₈** b) **56577₈**
 c) **56572₈** d) **65627₈**

2) The **excess-3** code of decimal number **26** is:

- a) **01001101** b) **01001001**
 c) **10001001** d) **01011001**

 3) In the circuit shown below, which logic function does this circuit generate?



- a) **OR** b) **AND**
 c) **NOR** d) **NAND**

4) The **dual** of the Boolean function $x + yz$ is:

- a) $\bar{x}(\bar{y} + \bar{z})$ b) $x(y + z)$
 c) $x + yz$ d) $\bar{x} + \bar{y}\bar{z}$

5) Applying **DeMorgan's theorem** to the expression $\overline{(X + Y) + Z}$, we get _____

- a) $(X+Y)Z$ b) $(\bar{X}+\bar{Y})\bar{Z}$
 c) $(\bar{X}+\bar{Y})Z$ d) $(X+Y)\bar{Z}$

6) The K-map for a Boolean function is shown in the figure. The number of **essential prime implicants** for this function is

CD \ AB	00	01	11	10
00	1	1	0	1
01	0	0	0	1
11	1	0	0	0
10	1	0	0	1

- a) **4** b) **5**
 c) **6** d) **8**


7) **Any** combinational circuit can be built using

1. *NAND gates.* 2. *NOR gates.*
 3. *EX-OR gates.* 4. *Multiplexers.*

Which of these are correct?

- a) **1, 2 and 3** b) **1, 3 and 4**
 c) **2, 3 and 4** d) **1, 2 and 4**

 8) Refer to the following figure, If **S₁=1** and **S₂=0** what will be the logic state at the output **X**?



- a) **X = A** b) **X = B**
 c) **X = C** d) **X = D**

9) **PRESET** and **CLEAR** inputs are normally **synchronous**.

- a) **True** b) **False**

10) When designing the circuit with the state table shown below using **JK** flip flops, then **J_A=...**, **K_A=...**

Present State		Input	Next State		JA	KA
A	B	X	A	B		
0	0	0	0	0		
0	0	1	0	1		
0	1	0	1	0		
0	1	1	0	1		
1	0	0	1	0		
1	0	1	1	1		
1	1	0	1	1		
1	1	1	0	0		

- a) $J_A = B'.x'$, $K_A = A'$
c) $J_A = B X$, $K_A = A'$

- b) $J_A = B.x$, $K_A = A$
d) $J_A = B.x'$, $K_A = B.x$

Question 2 This question is attributed with **6 marks** if answered properly; the answers are the following: (2 marks)

Solution

$$\begin{aligned}
&= (a.b.(c+\bar{b}+\bar{d})+\bar{a}+\bar{b}).c.d \quad (\text{De Morgan}) \\
&= (a.b.c+a.b.\bar{b}+a.b.\bar{d}+\bar{a}+\bar{b}).c.d \quad (\text{distribute}) \\
&= (a.b.c+a.b.\bar{d}+\bar{a}+\bar{b}).c.d \quad (a.b.\bar{b}=0) \\
&= a.b.c.d+a.b.\bar{d}.c.d+\bar{a}.c.d+\bar{b}.c.d \quad (\text{distribute}) \\
&= a.b.c.d+\bar{a}.c.d+\bar{b}.c.d \quad (a.b.\bar{d}.c.d=0) \\
&= (a.b+\bar{a}+\bar{b}).c.d \quad (\text{distribute}) \\
&= (a.b+\bar{a}.\bar{b}).c.d \quad (\text{DeMorgan}) \\
&= c.d \quad (a.b+\bar{a}.\bar{b}=1)
\end{aligned}$$

b) (4 marks)

Solution

	Function	Minterm list	Maxterm list
	F	$\sum XYZ (3; 5; 6; 7)$	$\prod XYZ (0; 1; 2; 4)$
	G	$\sum XYZ (1; 2; 4; 7)$	$\prod XYZ (0; 3; 5; 6)$

Question 3 This question is attributed with **6 marks** if answered properly; the answers are the following:

Solution

B_3B_2	00	01	11	10
B_1B_0				
00	m0 0	m4 0	m12 0	m8 0
01	m1 1	m5 1	m13 1	m9 1
11	m3 0	m7 0	m15 0	m11 0
10	m2 1	m6 1	m14 1	m10 1

B_3B_2	00	01	11	10
B_1B_0				
00	m0 0	m4 1	m12 1	m8 0
01	m1 0	m5 1	m13 1	m9 0
11	m3 1	m7 0	m15 0	m11 1
10	m2 1	m6 0	m14 0	m10 1

B_3B_2	00	01	11	10
B_1B_0				
00	m0 0	m4 1	m12 0	m8 1
01	m1 0	m5 1	m13 0	m9 1
11	m3 0	m7 1	m15 0	m11 1
10	m2 0	m6 1	m14 0	m10 1

$G_0 = B_0\bar{B}_1 + \bar{B}_0B_1 = B_0 \oplus B_1$

$G_1 = B_1\bar{B}_2 + \bar{B}_1B_2 = B_1 \oplus B_2$

$G_2 = B_2\bar{B}_3 + \bar{B}_2B_3 = B_2 \oplus B_3$

B_3B_2	00	01	11	10
B_1B_0				
00	m0 0	m4 0	m12 1	m8 1
01	m1 0	m5 0	m13 1	m9 1
11	m3 0	m7 0	m15 1	m11 1
10	m2 0	m6 0	m14 1	m10 1


logic circuit using XOR circuits

$G_3 = B_3$

Question 4 This question is attributed with **7 marks** if answered properly; the answers are the following:


a)

(2.5 marks)

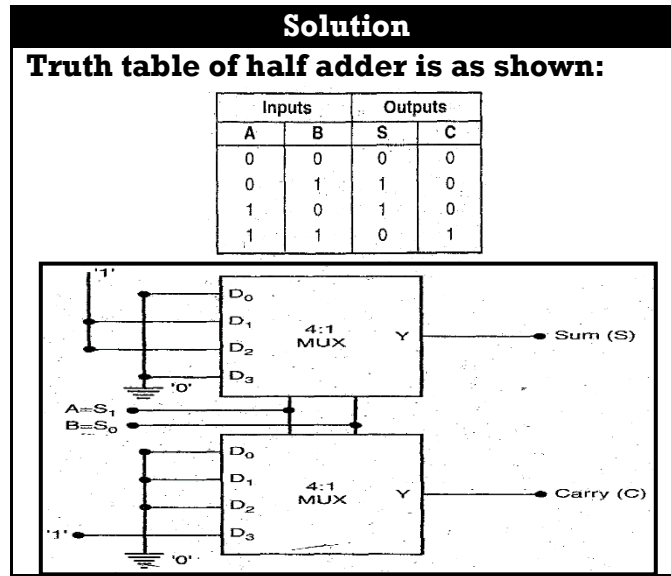


b)

(2 marks)

 

c)

(2.5 marks)

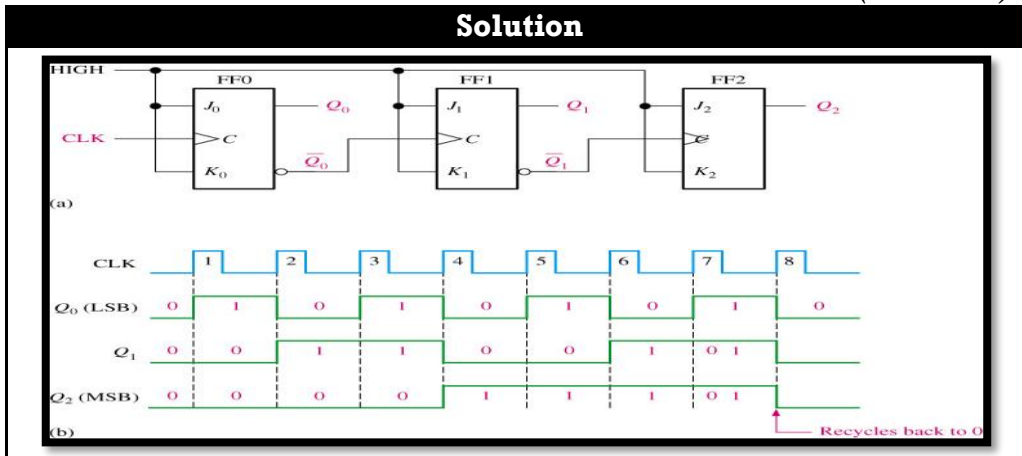


Question 5 This question is attributed with **5 marks** if answered properly; the answers are the following:

Solution

✓ Equations

- $A(t+1) = BC$ $Z = A$
- $B(t+1) = B'C + BC'$
- $C(t+1) = A'C'$

A	B	C	A'B'C'	Z
0	0	0	0 0 1	0
0	0	1	0 1 0	0
0	1	0	0 1 1	0
0	1	1	1 0 0	0
1	0	0	0 0 0	1
1	0	1	0 1 0	1
1	1	0	0 1 0	1
1	1	1	1 0 0	1

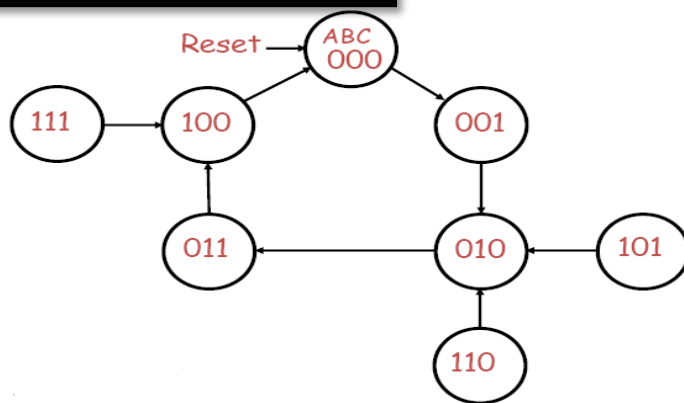

Question 6 This question is attributed with **6 marks** if answered properly; the answers are the following:

Solution

Quick table:

Present-state			Next-state		
Q ₂	Q ₁	Q ₀	Q ₂₊	Q ₁₊	Q ₀₊
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	1	1	0
1	1	0	1	1	1
1	1	1	1	0	1
1	0	1	0	0	1

Full table:

Present-state			Next-state		
Q ₂	Q ₁	Q ₀	Q ₂₊	Q ₁₊	Q ₀₊
0	0	0	x	x	x
0	0	1	0	1	1
0	1	0	1	1	0
0	1	1	0	1	0
1	0	0	x	x	x
1	0	1	0	0	1
1	1	0	1	1	1
1	1	1	1	0	1

Present-state			Next-state			Flip-flop input		
Q ₂	Q ₁	Q ₀	Q ₂₊	Q ₁₊	Q ₀₊	T ₂	T ₁	T ₀
0	0	1	0	1	1	0	1	0
0	1	1	0	1	0	0	0	1
0	1	0	1	1	0	1	0	0
1	1	0	1	1	1	0	0	1
1	1	1	1	0	1	0	1	0
1	0	1	0	0	1	1	0	0

Q ₂	T ₂				T ₁				T ₀			
	00	01	11	10	00	01	11	10	00	01	11	10
0	x	0	0	1	x	1	0	0	x	0	1	0
1	x	1	0	0	x	0	1	0	x	0	0	1

$T_2 = Q_2'Q_0' + Q_2Q_1'$ $T_1 = Q_2'Q_1' + Q_2Q_1Q_0$ $T_0 = Q_2Q_0' + Q_2'Q_1Q_0$

