



*Philadelphia University*  
*Faculty of Engineering*

**Marking Scheme**

Exam Paper

BSc CE

**Logic Circuits (630211)**

Second Exam

First semester

Date 02/01/2020

Section 1

Weighting 20% of the module total

Lecturer:

Dr. Qadri Hamarsheh

Coordinator:

Dr. Qadri Hamarsheh

Internal Examiner:

Eng. Anis Nazer

## Marking Scheme Logic Circuits (630211)

The presented exam questions are organized to overcome course material through 4 questions. The *all questions* are compulsory requested to be answered.

### Marking Assignments

#### Question 1: Multiple Choice

(5 marks)

1) The **sum** of ripple carry adder is

- a)  $S_i = A_i \oplus B_i \oplus C_i$
- b)  $S_i = A_i B_i + A_i C_i + B_i C_i$
- c)  $S_i = A_i + B_i + C_i$
- d)  $S_i = A_i B_i C_i$

2) A **BCD-to-7 segment decoder** has **0100** on its inputs. The active outputs are

- a) a, c, f, g
- b) b, c, f, g
- c) b, c, e, f
- d) b, d, e, g

3) A **6x64** line decoder can be built using:

- a) six 2x4 line decoders only
- b) nine 2x4 line decoders only
- c) seven 3x8 line decoders only
- d) nine 3x8 line decoders only

4) A **demultiplexer** can be used as

- a) Encoder
- b) Multiplexer
- c) Decoder
- d) None of the above

5) An **8-to-1** multiplexer has inputs **A**, **B** and **C** connected to the selection inputs **S2**, **S1** and **S0**, respectively. The data inputs **I0** through **I7**, are as follows:

$$I_1 = I_2 = 0; \quad I_3 = I_5 = I_7 = 1; \quad I_0 = I_4 = \bar{D} \quad \text{and} \quad I_6 = D$$

The **Boolean function** that the multiplexer implements is:

- a)  $F = \Sigma m(0, 6, 7, 8, 10, 11, 13, 14, 15)$
- b)  $F = \Sigma m(1, 2, 3, 4, 5, 9, 12)$
- c)  $F = \Sigma m(0, 6, 7, 8, 9, 11, 13, 14, 15)$
- d)  $F = \Sigma m(0, 6, 7, 9, 11, 14, 15)$

#### Question 2:

(7 marks)

a) (2 marks)

**Solution**

$$F(x, y, z) = m_2 + m_4 + m_5$$

b) (5 marks)

**Solution**


$F1 = (X+Y)' + XYZ = X'Y' + XYZ = X'Y'Z' + X'Y'Z + XYZ = \Sigma m(0,1,7)$   
 $F2 = (XZ)'Y = X'Y + YZ' = X'YZ + X'YZ' + XYZ' + X'YZ' = \Sigma m(3,2,6)$   
 $F3 = (X'+Y)' + X'Y'Z' = XY' + X'Y'Z' = XY'Z' + XY'Z + X'Y'Z' = \Sigma m(4,5,0)$

Question 3:

(5 marks)

**Solution**

A	B	C	D	F	
0	0	0	0	0	D
0	0	0	1	1	D
0	0	1	0	0	0
0	0	1	1	0	0
0	1	0	0	1	1
0	1	0	1	1	1
0	1	1	0	0	0
0	1	1	1	0	0
1	0	0	0	1	$\overline{D}$
1	0	0	1	0	$\overline{D}$
1	0	1	0	1	$\overline{D}$
1	0	1	1	0	$\overline{D}$
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	0	0

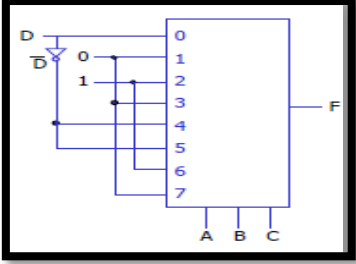

Question 4:

(3 marks)

**Solution**

