



Philadelphia University
Faculty of Engineering

Marking Scheme

Exam Paper

BSc CE

Logic Circuits (630211)

Second Quiz

First semester

Date 05/12/2019

Section 1

Weighting 6% of the module total

Lecturer:

Dr. Qadri Hamarsheh

Coordinator:

Dr. Qadri Hamarsheh

Internal Examiner:

Eng. Anis Nazer

Marking Scheme Logic Circuits (630211)

Marking Assignments

Question 1

(6 marks)

Solution

Decimal	Gray Code				BCD			
	A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	1	0	0	1	0
3	0	0	1	0	0	0	1	1
4	0	1	1	0	0	1	0	0
5	0	1	1	1	0	1	0	1
6	0	1	0	1	0	1	1	0
7	0	1	0	0	0	1	1	1
8	1	1	0	0	1	0	0	0
9	1	1	0	1	1	0	0	1
10	1	1	1	1	D	D	D	D
11	1	1	1	0	D	D	D	D
12	1	0	1	0	D	D	D	D
13	1	0	1	1	D	D	D	D
14	1	0	0	1	D	D	D	D
15	1	0	0	0	D	D	D	D

Karnaugh Map for W:

		A				
		00	01	11	10	
C	00	0	0	1	D	D
	01	0	0	1	D	
	11	0	0	D	D	
	10	0	0	D	D	
	10	0	0	D	D	
		B				

Minimal Expression for W:

$$W = A$$


Karnaugh Map for X:

		A				
		00	01	11	10	
C	00	0	1	0	D	D
	01	0	1	0	D	
	11	0	1	D	D	
	10	0	1	D	D	
	10	0	1	D	D	
		B				

Minimal Expression for X:

$$X = A'B$$

Karnaugh Map for Y:

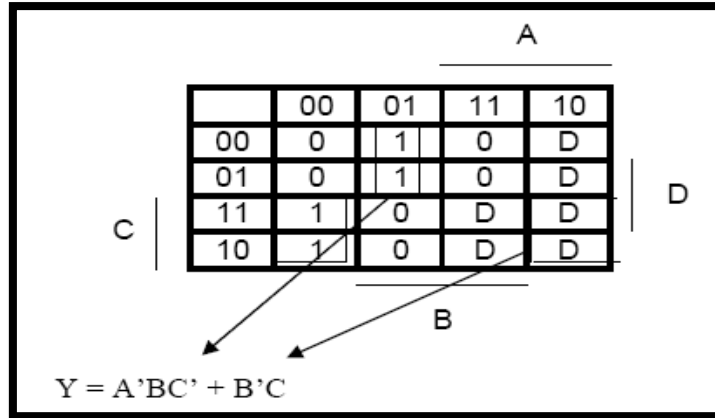

Karnaugh Map for Z:

