



Second Exam, Second Semester: 2018/2019  
Dept. of Computer Engineering

Course Title:	Logic Circuits	Date:	01/05/2019
Course No:	630211	Time Allowed:	50 minutes
Lecturer:	Dr. Qadri Hamarsheh	No. Of Pages:	4

Instructions:

- **ALLOWED:** pens and drawing tools (**no red color**).
- **NOT ALLOWED:** Papers, calculators, literatures and any handouts. Otherwise, it will lead to the non-approval of your examination.
- **Shut down** Telephones, and other communication devices.

Please note:

- This exam paper contains 4 questions totaling 20 marks
- Write your name and your matriculation number on every page of the solution sheets.
- All solutions together with solution methods (explanatory statement) must be inserted in the labelled position on the solution sheets.
- You can submit your exam after the first hour.

**Question 1 Multiple Choice**

(6 marks)

Identify the choice that best completes the statement or answers the question.

1) **BCD to 7 segments** is

- |                   |                 |
|-------------------|-----------------|
| a) <b>encoder</b> | b) <b>mux</b>   |
| c) <b>decoder</b> | d) <b>demux</b> |

2) To implement **binary full adder** using **decoders** we need:

- |   |
|---|
| a) <b>3-to-8 active high decoder with one AND logic gate</b>  |
| b) <b>3-to-8 active high decoder with two AND logic gates</b> |
| c) <b>3-to-8 active high decoder with one OR logic gate</b>   |
| d) <b>3-to-8 active high decoder with two OR logic gates</b>  |

3) The **carry propagation** in binary full adder can be expressed as \_\_\_\_\_.

- |   |   |
|---|---|
| a) <b><math>C_p = AB</math></b>         | b) <b><math>C_p = A + B</math></b>            |
| c) <b><math>C_p = A \oplus B</math></b> | d) <b><math>C_p = A \oplus \bar{B}</math></b> |

4) **Encoders 3x8** are made by three

- |                    |                     |
|--------------------|---------------------|
| a) <b>AND gate</b> | b) <b>OR gate</b>   |
| c) <b>XOR gate</b> | d) <b>NAND gate</b> |

5) If the input combination **S=1, R=1** is applied to **NOR** Based **SR** Latch circuit, the (steady state) output will be:

- |                     |                     |
|---------------------|---------------------|
| a) <b>Q=0, Q'=0</b> | b) <b>Q=0, Q'=1</b> |
| c) <b>Q=1, Q'=0</b> | d) <b>Q=1, Q'=1</b> |

6) Flip flop is:

- |                           |                             |
|---------------------------|-----------------------------|
| a) <b>level sensitive</b> | b) <b>Edge sensitive</b>    |
| c) <b>Both of a and b</b> | d) <b>None of the above</b> |

**Question 2**

**(3 marks)**

Explain the working of a **demultiplexer** with the help of the logic circuit

***Solution***

***Question 3:***

*(6 marks)*

Design **BCD to Excess-3** code converter using **decoder 4x16**.

**Solution**


Question 4:

(5 marks)


a) Implement **2 input NAND** gate function using a **2:1 multiplexer**.

(3 marks)

**Solution**

 

 b) Find the Boolean function **F(w, x, y)** and express it in the simplified **SOP** format. (2 marks)



**Solution**



**GOOD LUCK**