



Second Exam, First Semester: 2019/2020

Dept. of Computer Engineering

Course Title:	Logic Circuits	Date:	02/01/2020
Course No:	630211	Time Allowed:	50 minutes
Lecturer:	Dr. Qadri Hamarsheh	No. Of Pages:	4

Instructions:

- **ALLOWED:** pens and drawing tools (**no red color**).
- **NOT ALLOWED:** Papers, calculators, literatures and any handouts. Otherwise, it will lead to the non-approval of your examination.
- **Shut down** Telephones, and other communication devices.

Please note:

- This exam paper contains 4 questions totaling 20 marks
- Write your name and your matriculation number on every page of the solution sheets.
- All solutions together with solution methods (explanatory statement) must be inserted in the labelled position on the solution sheets.

**Question 1 Multiple Choice**

(5 marks)

**Identify the choice that best completes the statement or answers the question.**

1) The **sum** of ripple carry adder is

- a)  $S_i = A_i \oplus B_i \oplus C_i$
- b)  $S_i = A_i B_i + A_i C_i + B_i C_i$
- c)  $S_i = A_i + B_i + C_i$
- d)  $S_i = A_i B_i C_i$

2) A **BCD-to-7 segment decoder** has **0100** on its inputs. The active outputs are

- a) **a, c, f; g**
- b) **b, c, f; g**
- c) **b, c, e, f**
- d) **b, d, e, g**

3) A **6x64** line decoder can be built using:

- a) **six 2x4 line decoders only**
- b) **nine 2x4 line decoders only**
- c) **seven 3x8 line decoders only**
- d) **nine 3x8 line decoders only**

4) A **demultiplexer** can be used as

- a) **Encoder**
- b) **Multiplexer**
- c) **Decoder**
- d) **None of the above**

5) An **8-to-1** multiplexer has inputs **A, B** and **C** connected to the selection inputs **S2, S1** and **S0**, respectively. The data inputs  $I_0$  through  $I_7$  are as follows:

$$I_1 = I_2 = 0; \quad I_3 = I_5 = I_7 = 1; \quad I_0 = I_4 = \bar{D} \quad \text{and} \quad I_6 = D$$


The **Boolean function** that the multiplexer implements is:

- a)  $F = \Sigma m (0, 6, 7, 8, 10, 11, 13, 14, 15)$
- b)  $F = \Sigma m (1, 2, 3, 4, 5, 9, 12)$
- c)  $F = \Sigma m (0, 6, 7, 8, 9, 11, 13, 14, 15)$
- d)  $F = \Sigma m (0, 6, 7, 9, 11, 14, 15)$

**Question 2**

(7 marks)

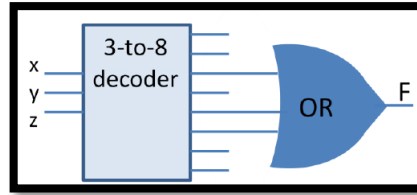- a) What function  $F(x, y, z)$  is implemented in the figure shown below? You may answer using the minterm notion. (2 marks)



**Solution**

- b) A combinational circuit is defined by the following three Boolean functions: (5 marks)

$$F1 = \overline{X} + \overline{Y} + XYZ$$

$$F2 = \overline{XZ} Y$$

$$F3 = \overline{\overline{X} + Y + \overline{XYZ}}$$

Design the circuit with a **3-to-8 decoder** and **external** gates.

**Solution**

*Question 3:*

*(5 marks)*

Design the function  $F(A, B, C, D) = \sum m(1, 4, 5, 8, 10, 12, 13)$  using **8x1 multiplexer**.

***Solution***

*Question 4*

*(3 marks)*

Construct a **1-to-32 demultiplexer** using only two types of **demultiplexers: 1-to-4 and 1-to-8**.

***Solution***

**GOOD LUCK**