

Philadelphia University



Student Name:

Faculty of Engineering

Student Number:

Dept. of Computer Engineering

Third Quiz, First Semester: 2019/2020

Course Title:	Logic Circuits	Date:	16/01/2020
Course No:	630211	Time Allowed:	10 minutes
Lecturer:	Dr. Qadri Hamarsheh	No. Of Pages:	1

Information for candidates

1. This Quiz paper contains 1 question totaling 6 marks
2. The marks for parts of question are shown in round brackets.

Advices to candidates

1. You should attempt all sub questions.
2. You should write your answers clearly.

Question 1

(6 marks)

Write brief summary of the Types of Flip-flop (**SR, JK, T and D**)

Hint: your summary must contain

- Flip-Flop Symbol
- Characteristic Table
- Characteristic Equation
- Excitation Table

Solution

GOOD LUCK