



Electric Circuits II

Resonance

Dr. Firas Obeidat

Table of Contents

1



- Parallel Resonance

Parallel Resonance

The parallel RLC circuit is the dual of the series RLC circuit. The admittance is

$$\mathbf{Y} = H(\omega) = \frac{\mathbf{I}}{\mathbf{V}} = \frac{1}{R} + j\omega C + \frac{1}{j\omega L}$$
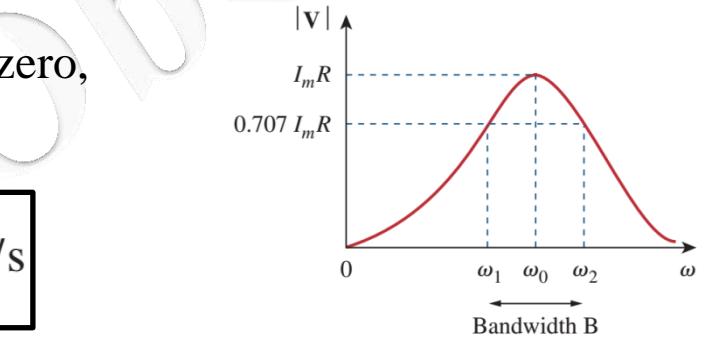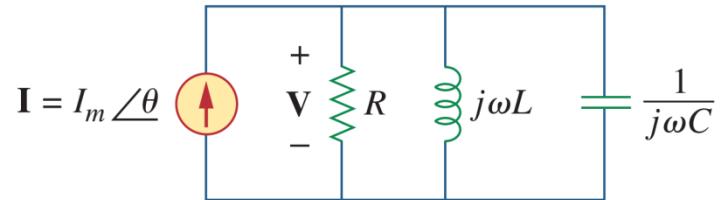
$$\mathbf{Y} = \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)$$



Resonance occurs when the imaginary part of \mathbf{Y} is zero,

$$\omega C - \frac{1}{\omega L} = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

Using duality between series and parallel circuits. By replacing R , L , and C in the expressions for the series circuit with $1/R$, C and L respectively, we obtain for the parallel circuit

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

Parallel Resonance

$$B = \omega_2 - \omega_1 = \frac{1}{RC}$$

$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

The half power frequencies in terms of the quality factor is

$$\omega_1 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} - \frac{\omega_0}{2Q}, \quad \omega_2 = \omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} + \frac{\omega_0}{2Q}$$

for high-Q circuits ($Q \geq 10$)

$$\omega_1 \approx \omega_0 - \frac{B}{2}, \quad \omega_2 \approx \omega_0 + \frac{B}{2}$$

Parallel Resonance

Example: In the parallel RLC circuit, let $R=8 \text{ k}\Omega$, $L=0.2 \text{ mH}$ and $C=8 \mu\text{F}$.

(a) Calculate ω_0 , Q , and B .

(b) Calculate ω_1 and ω_2 .

(c) Determine the power dissipated at ω_0 , ω_1 and ω_2 .

(a)

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.2 \times 10^{-3} \times 8 \times 10^{-6}}} = \frac{10^5}{4} = 25 \text{ krad/s}$$


$$Q = \frac{R}{\omega_0 L} = \frac{8 \times 10^3}{25 \times 10^3 \times 0.2 \times 10^{-3}} = 1,600$$

$$B = \frac{\omega_0}{Q} = 15.625 \text{ rad/s}$$

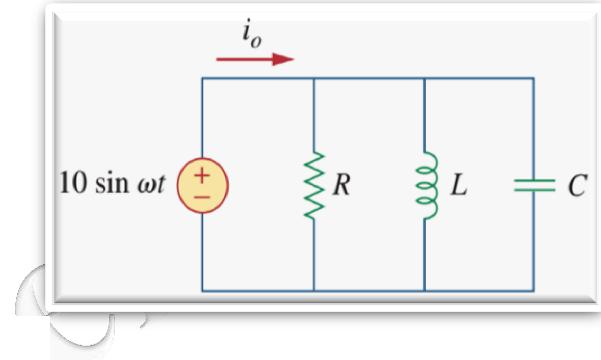(b) Due to the high value of Q , we can regard this as a high- Q circuit,
Hence,

$$\omega_1 = \omega_0 - \frac{B}{2} = 25,000 - 7.812 = 24,992 \text{ rad/s}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 25,000 + 7.812 = 25,008 \text{ rad/s}$$



Parallel Resonance

(c) At $\omega = \omega_0$, $\mathbf{Y} = 1/R$ or $\mathbf{Z} = R = 8 \text{ k}\Omega$. Then

$$\mathbf{I}_o = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{10 \angle -90^\circ}{8,000} = 1.25 \angle -90^\circ \text{ mA}$$

Yak

Since the entire current flows through R at resonance, the average power dissipated at $\omega = \omega_0$ is

$$P = \frac{1}{2} |\mathbf{I}_o|^2 R = \frac{1}{2} (1.25 \times 10^{-3})^2 (8 \times 10^3) = 6.25 \text{ mW}$$

or

$$P = \frac{V_m^2}{2R} = \frac{100}{2 \times 8 \times 10^3} = 6.25 \text{ mW}$$

At $\omega = \omega_1, \omega_2$,

$$P = \frac{V_m^2}{4R} = 3.125 \text{ mW}$$

Parallel Resonance

Example: A parallel resonance circuit has a resistance of $2 \text{ k}\Omega$ and half-power frequencies of 86 kHz and 90 kHz. Determine:

- (a) the capacitance
- (c) the resonant frequency
- (e) the quality factor

- (b) the inductance
- (d) the bandwidth

$$(a) B = \omega_2 - \omega_1 = 2\pi(f_2 - f_1) = 2\pi(90 - 86) \times 10^3 = 8\pi \text{ krad/s}$$

$$\omega_0 = \frac{1}{2}(\omega_1 + \omega_2) = 2\pi(88) \times 10^3 = 176\pi \times 10^3$$

$$B = \frac{1}{RC} \quad \longrightarrow \quad C = \frac{1}{BR} = \frac{1}{8\pi \times 10^3 \times 2 \times 10^3} = \underline{19.89 \text{ nF}}$$

$$(b) \omega_0 = \frac{1}{\sqrt{LC}} \quad \longrightarrow \quad L = \frac{1}{\omega_0^2 C} = \frac{1}{(176\pi \times 10^3)^2 \times 19.89 \times 10^{-9}} = \underline{164.45 \text{ }\mu\text{H}}$$

$$(c) \omega_0 = 176\pi = \underline{552.9 \text{ krad/s}}$$

$$(d) B = 8\pi = \underline{25.13 \text{ krad/s}}$$

$$(e) Q = \frac{\omega_0}{B} = \frac{176\pi}{8\pi} = \underline{22}$$

Parallel Resonance

Example: For the circuit:

- Calculate the resonant frequency ω_0 , the quality factor Q , and the bandwidth B .
- What value of capacitance must be connected in series with the $20 \mu\text{F}$ capacitor in order to double the bandwidth?.

(a) $L = 5 + 10 = 15 \text{ mH}$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{15 \times 10^{-3} \times 20 \times 10^{-6}}} = \underline{\underline{1.8257 \text{ k rad/sec}}}$$


$$Q = \omega_0 RC = 1.8257 \times 10^3 \times 25 \times 10^3 \times 20 \times 10^{-6} = \underline{\underline{912.8}}$$

$$B = \frac{1}{RC} = \frac{1}{25 \times 10^3 \times 20 \times 10^{-6}} = \underline{\underline{2 \text{ rad/s}}}$$

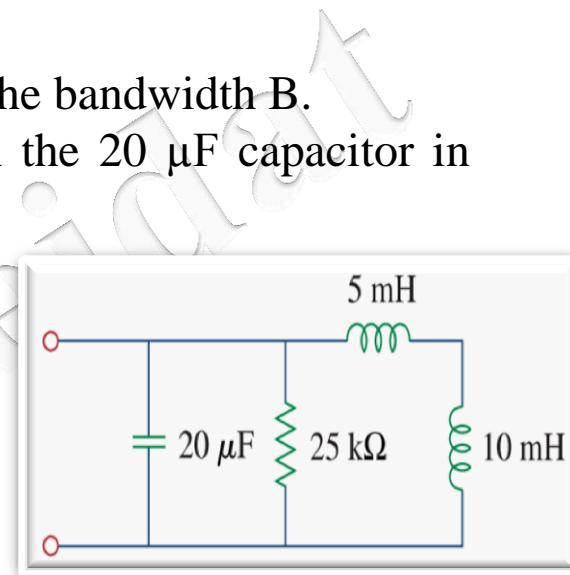(b) To increase B by 100% means that $B' = 4$.

$$C' = \frac{1}{RB'} = \frac{1}{25 \times 10^3 \times 4} = \underline{\underline{10 \mu\text{F}}}$$

Since $C' = \frac{C_1 C_2}{C_1 + C_2} = 10 \mu\text{F}$ and $C_1 = 20 \mu\text{F}$, we then obtain $C_2 = 20 \mu\text{F}$.



Series-Parallel Resonance

Example: Determine the resonant frequency of the circuit.

The input admittance is

$$Y = j\omega 0.1 + \frac{1}{10} + \frac{1}{2 + j\omega 2} = 0.1 + j\omega 0.1 + \frac{2 - j\omega 2}{4 + 4\omega^2}$$

At resonance, $\text{Im}(Y) = 0$ and

$$\omega_0 0.1 - \frac{2\omega_0}{4 + 4\omega_0^2} = 0$$

$$0.1\omega_0 = \frac{2\omega_0}{4 + 4\omega_0^2}$$

$$0.4\omega_0 + 0.4\omega_0^3 = 2\omega_0$$


$$0.4 + 0.4\omega_0^2 = 2$$

$$0.4\omega_0^2 = 2 - 0.4 = 1.6$$

$$\omega_0^2 = 1.6/0.4 = 4$$

$$\omega_0 = \pm\sqrt{4} = \pm 2$$

$$\omega_0 = 2 \text{ rad/s}$$

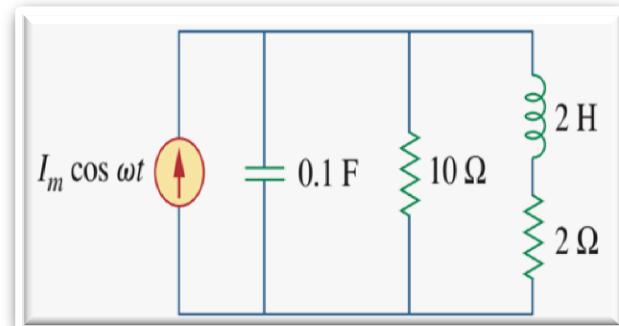

Series-Parallel Resonance

Example: Determine the resonant frequency of the circuit.

$$Z = jX_L + \frac{-jX_C R}{R - jX_C} \times \frac{R + jX_C}{R + jX_C} = jX_L + \frac{RX_C^2 - jR^2 X_C}{R^2 + X_C^2}$$

$$Z = \frac{RX_C^2}{R^2 + X_C^2} + j\left(X_L - \frac{R^2 X_C}{R^2 + X_C^2}\right)$$

At resonance, $\text{Im}(Z)=0$.

$$X_L - \frac{R^2 X_C}{R^2 + X_C^2} \rightarrow X_L = \frac{R^2 X_C}{R^2 + X_C^2}$$

$$X_L R^2 + X_L X_C^2 = R^2 X_C$$

$$\omega_o L R^2 + \frac{\omega_o L}{\omega_o^2 C^2} = \frac{R^2}{\omega_o C}$$

$$\omega_o^2 C L R^2 + \frac{\omega_o^2 C L}{\omega_o^2 C^2} = R^2$$

$$\omega_o^2 C L R^2 + \frac{L}{C} = R^2$$

$$\omega_o^2 + \frac{1}{C^2 R^2} = \frac{R^2}{C L R^2}$$

$$\omega_o^2 + \frac{1}{C^2 R^2} = \frac{1}{LC}$$


$$\omega_o^2 = \frac{1}{CL} - \frac{1}{C^2 R^2} \rightarrow \omega_o = \pm \sqrt{\frac{1}{LC} - \frac{1}{C^2 R^2}}$$

$$\omega_o = \pm \sqrt{\frac{1}{0.5 \times 10^{-3} \times 10 \times 10^{-3}} - \frac{1}{(0.5 \times 10^{-3})^2 \times 20^2}}$$

$$\omega_o = \pm \sqrt{0.2 \times 10^6 - 0.01 \times 10^6}$$

$$\omega_o = \pm \sqrt{0.19 \times 10^6} = \pm 0.4359 \times 10^3$$

$$\omega_o = 435.9 \text{ rad/s}$$

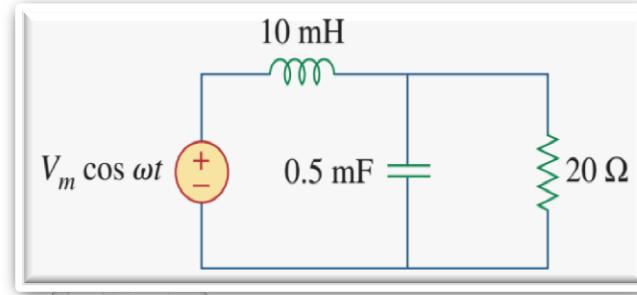

Series-Parallel Resonance

Example: For the circuit, find the resonant frequency ω_0 and $Z_{in}(\omega_0)$.

$$Z_{in} = (R_1 \parallel j\omega L) \parallel (R_2 + 1/j\omega C)$$

$$Z_{in} = \left(\frac{R_1 j\omega L}{R_1 + j\omega L} \right) \parallel \left(R_2 + \frac{1}{j\omega C} \right)$$

$$Z_{in} = \frac{\frac{j\omega R_1 L}{R_1 + j\omega L} \cdot \left(R_2 + \frac{1}{j\omega C} \right)}{R_2 + \frac{1}{j\omega C} + \frac{jR_1 \omega L}{R_1 + j\omega L}}$$

$$Z_{in} = \frac{j\omega R_1 L (1 + j\omega R_2 C)}{(R_1 + j\omega L)(1 + j\omega R_2 C) - \omega^2 L C R_1}$$

$$Z_{in} = \frac{-\omega^2 R_1 R_2 L C + j\omega R_1 L}{R_1 - \omega^2 L C R_1 - \omega^2 L C R_2 + j\omega (L + R_1 R_2 C)}$$

$$Z_{in} = \frac{(-\omega^2 R_1 R_2 L C + j\omega R_1 L)[R_1 - \omega^2 L C R_1 - \omega^2 L C R_2 - j\omega (L + R_1 R_2 C)]}{(R_1 - \omega^2 L C R_1 - \omega^2 L C R_2)^2 + \omega^2 (L + R_1 R_2 C)^2}$$


At resonance, $\text{Im}(Z_{in}) = 0$

$$0 = \omega^3 R_1 R_2 L C (L + R_1 R_2 C) + \omega R_1 L (R_1 - \omega^2 L C R_1 - \omega^2 L C R_2)$$

$$0 = \omega^3 R_1^2 R_2^2 L C^2 + R_1^2 \omega L - \omega^3 R_1^2 L^2 C$$

$$0 = \omega^2 R_2^2 C^2 + 1 - \omega^2 L C$$

$$\omega^2 (L C - R_2^2 C^2) = 1$$

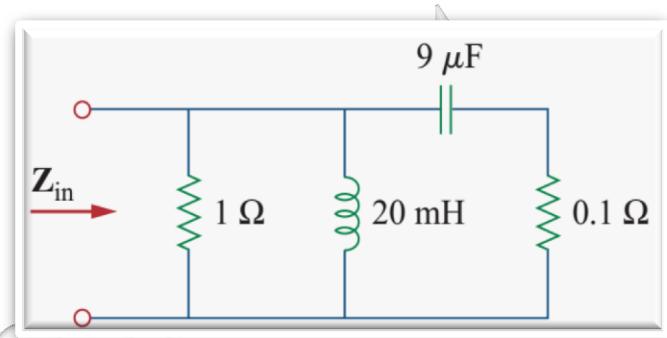

Series-Parallel Resonance

$$\omega_0 = \frac{1}{\sqrt{LC - R_2^2 C^2}}$$

$$\omega_0 = \frac{1}{\sqrt{(0.02)(9 \times 10^{-6}) - (0.1)^2 (9 \times 10^{-6})^2}}$$

$$\omega_0 = 2.357 \text{ krad/s}$$

At $\omega = \omega_0 = 2.357 \text{ krad/s}$,

$$j\omega L = j(2.357 \times 10^3)(20 \times 10^{-3}) = j47.14$$

$$R_1 \parallel j\omega L = \frac{j47.14}{1 + j47.14} = 0.9996 + j0.0212$$

$$R_2 + \frac{1}{j\omega C} = 0.1 + \frac{1}{j(2.357 \times 10^3)(9 \times 10^{-6})} = 0.1 - j47.14$$

$$Z_{in}(\omega_0) = (R_1 \parallel j\omega L) \parallel (R_2 + 1/j\omega C)$$

$$Z_{in}(\omega_0) = \frac{(0.9996 + j0.0212)(0.1 - j47.14)}{(0.9996 + j0.0212) + (0.1 - j47.14)}$$

$$Z_{in}(\omega_0) = 1 \Omega$$

Series and Parallel Resonance

Summary of the characteristics of resonant *RLC* circuits.

Characteristic	Series circuit	Parallel circuit
Resonant frequency, ω_0	$\frac{1}{\sqrt{LC}}$	$\frac{1}{\sqrt{LC}}$
Quality factor, Q	$\frac{\omega_0 L}{R}$ or $\frac{1}{\omega_0 R C}$	$\frac{R}{\omega_0 L}$ or $\omega_0 R C$
Bandwidth, B	$\frac{\omega_0}{Q}$	$\frac{\omega_0}{Q}$
Half-power frequencies, ω_1, ω_2	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$	$\omega_0 \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \pm \frac{\omega_0}{2Q}$
For $Q \geq 10$, ω_1, ω_2	$\omega_0 \pm \frac{B}{2}$	$\omega_0 \pm \frac{B}{2}$

Dr. Firas Obeidat

