

Second Exam

time allowed: 50 min

Eng. Laith R. Batarseh

Sunday 29/12/2013

Student Name:

Student ID number:

Problem #1: for the following experimental data, find the linear fitting equation:  $y = ax + b$  using the least square method (6marks)

$$a = \frac{n \sum x_i y_i - \sum x_i \sum y_i}{n \sum x_i^2 - (\sum x_i)^2} \quad b = \frac{\sum x_i \sum x_i^2 - \sum x_i y_i \sum x_i}{n \sum x_i^2 - (\sum x_i)^2}$$

$x_i$	$y_i$
1.2	9
1.6	11
1.8	12
2.4	15
3.2	19

$x_i$	$y_i$	$x_i y_i$	$x_i^2$
1.2	9	10.8	1.44

$$n = 5$$

1.6	11	17.6	2.56
-----	----	------	------

1.8	12	21.6	3.24
-----	----	------	------

2.4	15	36	5.76
-----	----	----	------

3.2	19	60.8	10.24
-----	----	------	-------

$$\sum = 10.2 \quad 66 \quad 146.8 \quad 23.24$$

$$a = \frac{(5)(146.8) - (10.2)(66)}{(5)(23.24) - (10.2)^2} = 5$$

$$b = \frac{(66)(23.24) - (146.8)(10.2)}{(5)(23.24) - (10.2)^2} = 3$$

$$y = 5x + 3$$


**Problem #2:** if the following spring - wire setup is used to measure the current ( $i$ ). if the spring constant is 550 N/m, the magnetic flux is  $365 \times 10^{-3}$  Weber, the length of the wire is 25cm and the deflection in the spring is 1.6 mm (4marks)

$$F_s = F$$


$$kx = B i L$$

$$i = \frac{k}{B L} x$$
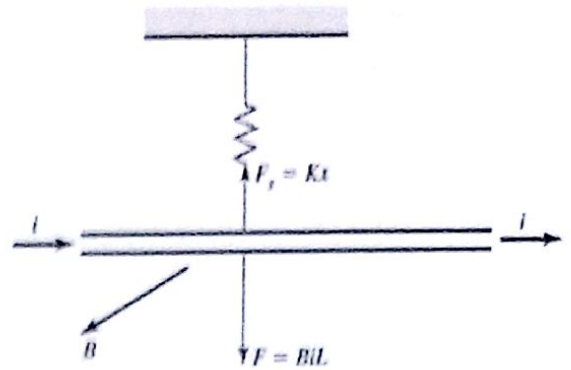
$$i = \frac{550}{365 \times 10^{-3} \times 0.25} (1.6 \times 10^{-3}) = 9.64 \text{ Ampere}$$



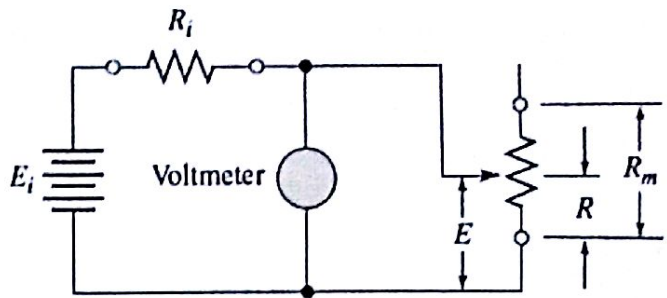Problem #3: for the basic electrical circuit shown, if  $R_m = 5\Omega$ ,  $R_i = 3\Omega$  the ratio  $E/E_i = 0.25$ . Find the value of transducer resistance ( $R$ ) in  $\Omega$ . (4marks)



$$\frac{E}{E_i} = \frac{iR}{i(R_i + R)}$$

$$= \frac{(R/R_m)(R_m/R_i)}{(R/R_m)(R_m/R_i) + 1}$$

Simply

$$\Rightarrow 0.25 = \frac{R}{3 + R} \Rightarrow (0.25)(3) + (0.25)R = R$$

$$\Rightarrow 0.75 R = 0.75 \Rightarrow R = 1\Omega$$




Problem #4:

(6marks)

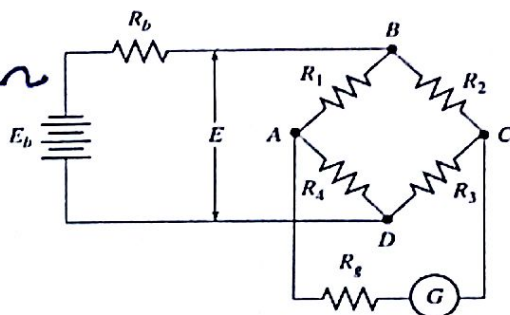1. Wheatstone bridge circuit has ratio arms ( $R_2$  and  $R_3$ ) of  $1000\Omega$  and  $500\Omega$  and the adjustable resistance  $R_1$  reads  $200\Omega$ . calculate the value of the unknown resistance  $R_4$  if this bridge is balanced (null condition)

$$R_4 = \frac{R_1 R_3}{R_2} = \frac{(200)(500)}{1000} = 100 \Omega$$



2. Now, if this bridge is deflected (unbalanced) and a galvanometer with a resistance of  $25\Omega$  and a sensitivity of  $0.2\mu A/mm$  is connected between B and D, . The galvanometer deflection is  $10\text{ mm}$ , and the battery voltage is  $5\text{ V}$ . assuming no internal battery resistance and the value of  $R_1$  is changed to  $280\Omega$ . Calculate the value of the unknown resistance  $R_4$

$$i_g = \frac{E_g}{R + R_g} \quad E_g = E \left[ \frac{R_1}{R_1 + R_4} - \frac{R_2}{R_2 + R_3} \right]$$

Substitute to find  $R_4$

$$R_4 = \frac{E R_1 R_3 - i_g [R_g R_1 (R_2 + R_3) + R_1 R_2 R_3]}{i_g (1 + R_1 + R_g) (R_2 + R_3) + E R_2}$$

Given:  $i_g = (0.2)(10) = 2\mu A = 2 \times 10^{-6} A$

$R_b = 20$   $R_1 = 280$   $R_2 = 1000$  ,  $R_3 = 500$  ,  $R_g = 25$

$E = 5\text{ V}$

$$R_4 = \frac{(5)(280)(500) - 2 \times 10^{-6} [(25)(280)(500 + 1000) + (280)(500)(1000)]}{2 \times 10^{-6} [(1 + 280 + 25)(1000 + 500)] + 5(1000)}$$

$$R_4 = \frac{699691}{5000.918} \approx 140 \Omega$$