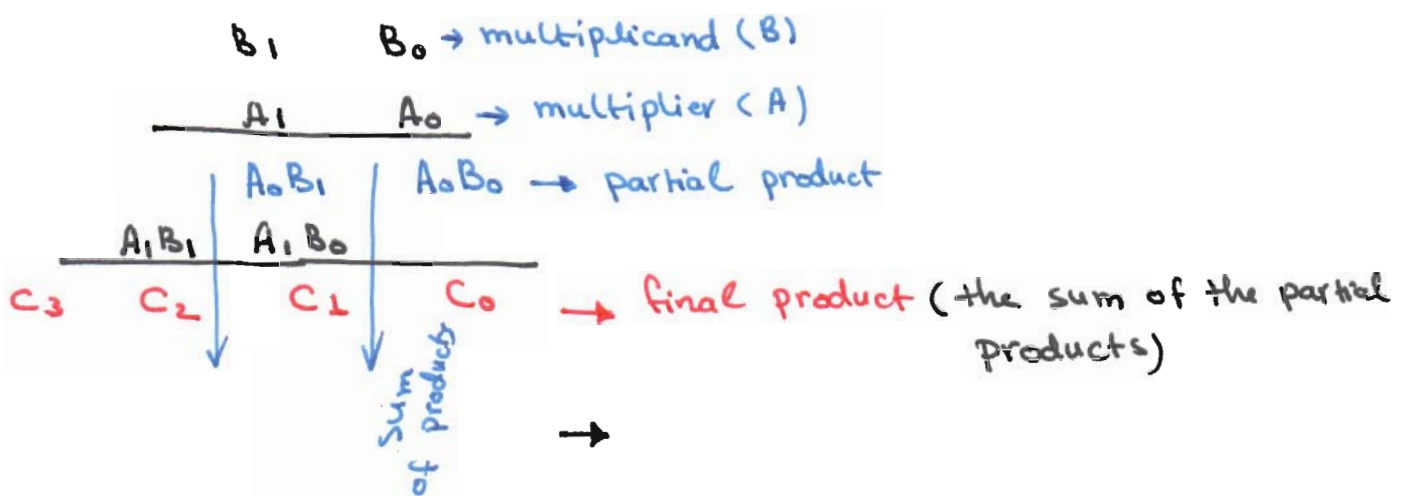


# Binary Multiplier


multiplication of binary numbers is performed in the same way as multiplication of decimal numbers.

1- multiplication of two 2-bit numbers:


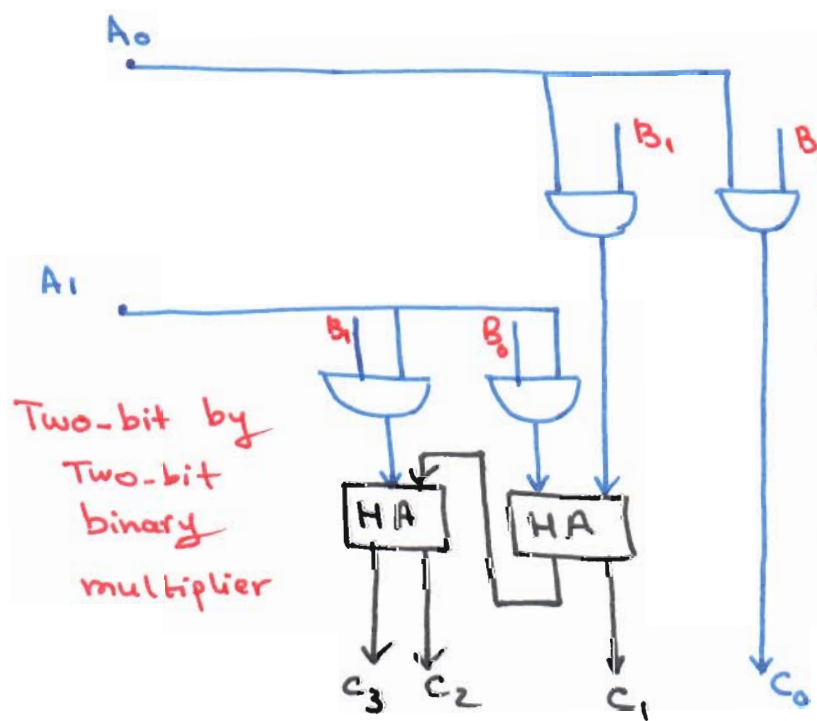
## Combinational Circuit.

- \* The multiplication of two bits such as  $A_0$  and  $B_0$  produces a 1 if both bits are 1; otherwise, it produces a 0. This is identical to an AND operation.
- \* The two partial products are added with two half-adder (HA) circuits. (if there are more than two bits, we must use full-adder (FA)).




## 2- Combinational Circuit of binary multiplier with more bits.


- \* For  $J$  multiplier bits and  $K$  multiplicand bits, we need:
  - $J \times K$  and gates.
  - $(J-1)K$ -bits adders
  - to produce a product of  $j+k$  bits.

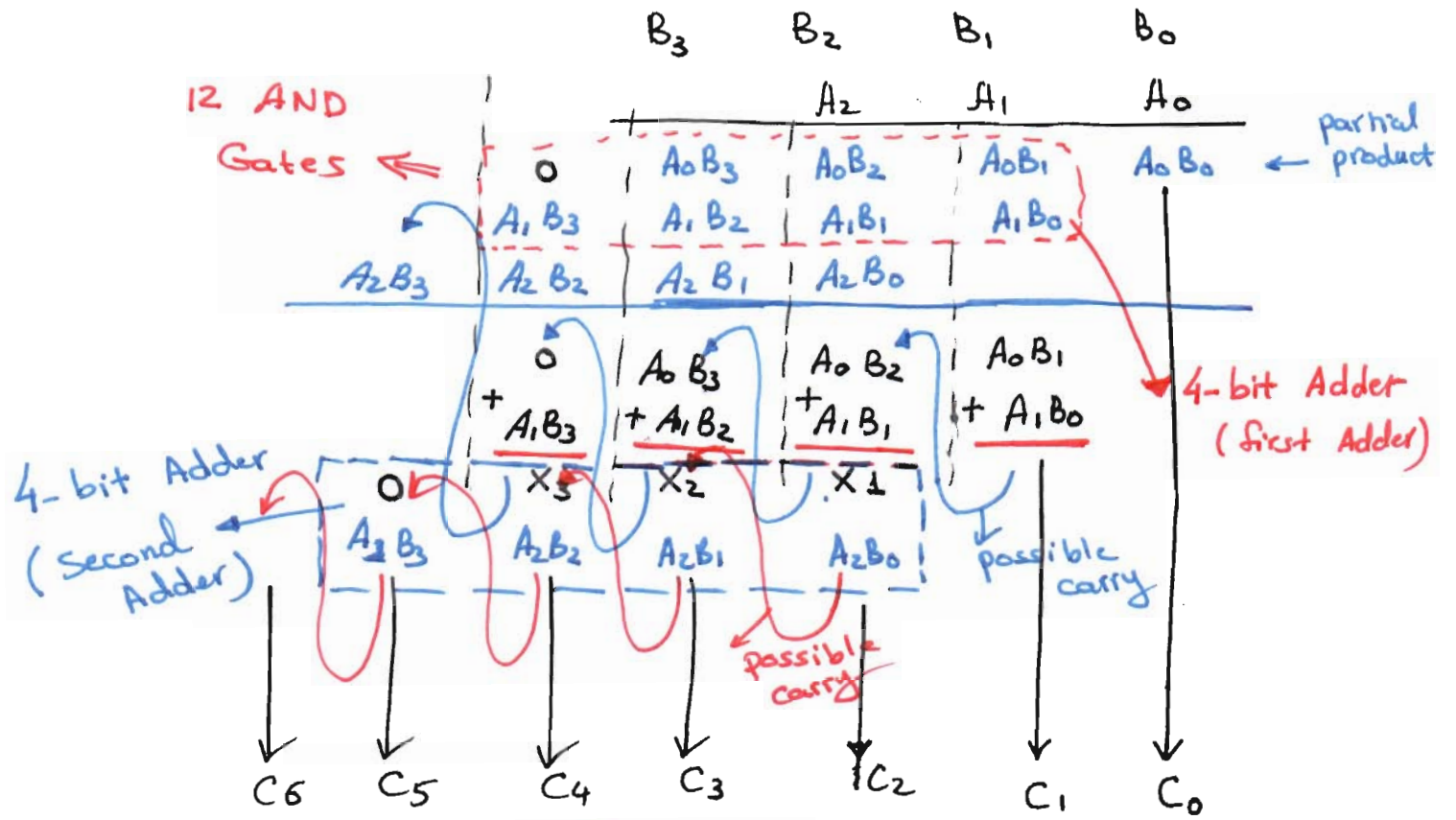Example: Create a logic circuit for

$$\begin{array}{r} B_3 B_2 B_1 B_0 \\ \times \\ \hline A_2 A_1 A_0 \\ \hline C_6 C_5 C_4 C_3 C_2 C_1 C_0 \end{array} \rightarrow \text{Answer.}$$



Circuit Implementation.

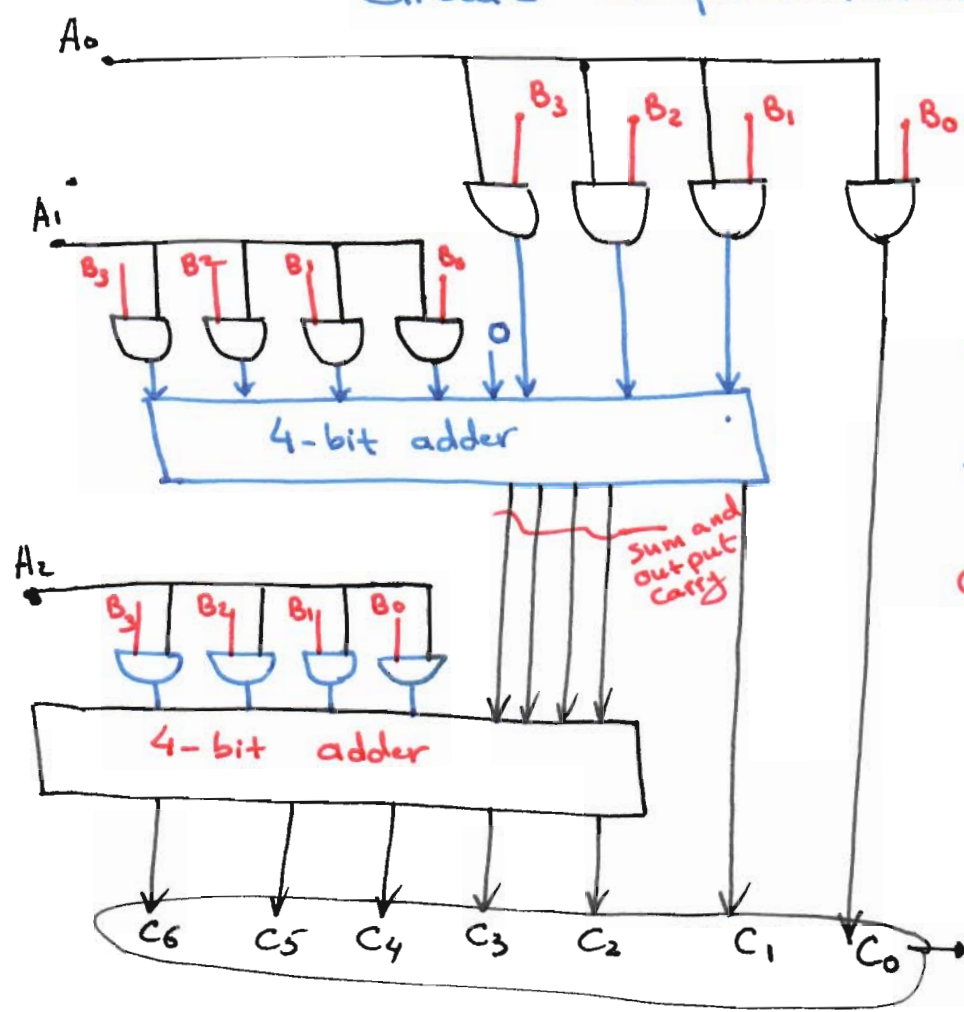

\*  $K = 4$   
 $J = 3$   
 So:  
 We need  
 12 AND Gates  
 and  
 2 four-bit Adders.  
 to produce a  
 product of seven bits:  
 $C_6 C_5 C_4 C_3 C_2 C_1 C_0$

Result.

# Decoders

Information is represented in digital systems by binary codes. A binary code of  $n$  bits is capable of representing up to  $2^n$  distinct elements of coded information.

A decoder is a combinational circuit that converts binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines.

The decoders are called  $n$ -to- $m$  line decoders, where  $m \leq 2^n$  (for example BCD-to-seven-segment decoder, or 3-to-8 decoder).


The purpose of the decoders is to generate the  $2^n$  (or fewer) minterms of  $n$  input variables.

\* Decoder is a circuit that allows us to activate an output line by specifying a control word, it is either active-high or active-low.

- Active-high sets a particular output to logic 1, while remaining other outputs to logic 0.

- Active-low sets a particular output to logic 0, other outputs to logic 1.

## 1. 2/4 decoder (Active-high).

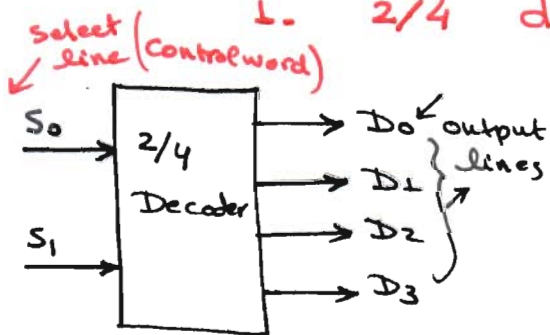

$S_0, S_1 \rightarrow$  select lines  
 $D_0, D_1, D_2, D_3 \rightarrow$  output lines.

$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

Truth table

1)  $S_1 = 0, S_0 = 0 \Rightarrow D_0 = 1$

$D_0 = \bar{S}_1 \cdot \bar{S}_0; D_1 = D_2 = D_3 = 0.$


2)  $S_1 = 1, S_0 = 0 \Rightarrow D_1 = 1$

$D_0 = D_2 = D_3 = 0; D_1 = S_1 \cdot \bar{S}_0$

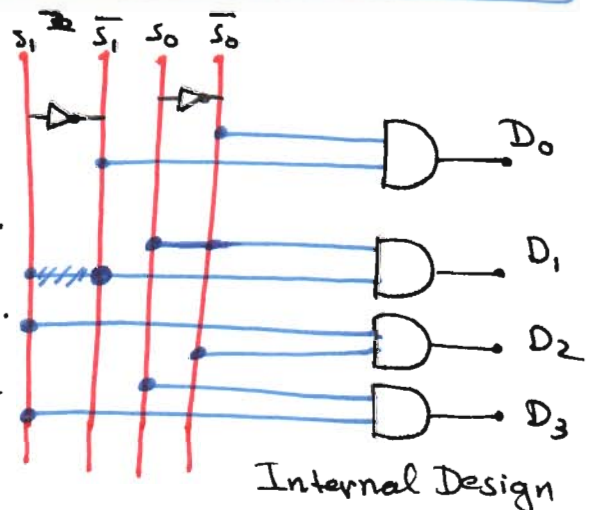3)  $D_2 = S_1 \cdot \bar{S}_0$       4)  $D_3 = S_1 \cdot S_0$

\* From truth table:


- two inputs are decoded to 4 outputs.
- each output represents one of the minterms of the three input variables.
- for each possible combination (input), there are 3 outputs that are equal to 0 and only one that is equal to 1.





• Active-Low Decoders:

S <sub>1</sub>	S <sub>0</sub>	D <sub>3</sub>	D <sub>2</sub>	D <sub>1</sub>	D <sub>0</sub>
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	1

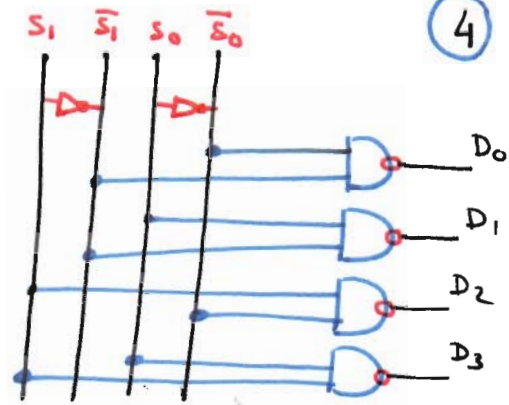

$D_0 = \overline{S_1 \cdot S_0} \rightarrow$  complement  
 $= S_1 + S_0$

$D_1 = \overline{S_1 \cdot \overline{S_0}} = S_1 + S_0$  ;  $D_2 = \overline{\overline{S_1} \cdot S_0}$  ;  $D_3 = \overline{\overline{S_1} \cdot \overline{S_0}}$  .


AND becomes NAND

- Decoders with enable inputs:

Some decoders include one or more enable inputs to control the circuit operation.

a two-to-four line decoder with an enable input constructed with NAND gate is the following:

E	A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	1

 

The circuit operates with

complemented outputs and a complemented enable input (Active-low enable)

$E = 0 \rightarrow$  The decoder is enabled [Active-low]


$E = 1 \rightarrow$  The decoder is disabled [enable]

\* The enable input may be activated with 0 or with a 1 signal.

2. three-to-eight-line decoder circuit

inputs			outputs							
X	Y	Z	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>	D <sub>4</sub>	D <sub>5</sub>	D <sub>6</sub>	D <sub>7</sub>
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Truth table.

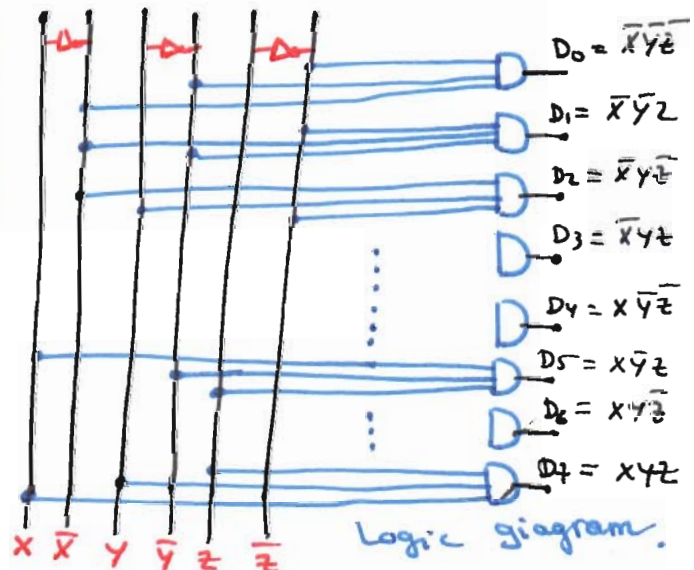


Logic diagram.
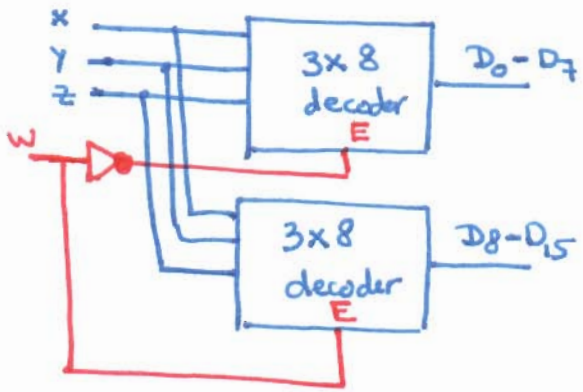
### 3. Larger decoder circuit.

decoders with enable inputs can be connected together to form a larger decoder circuit.

To design a 4-to-16 line decoder, using two 3-to-8 decoders with enable inputs, we do the following connection:



when  $w=0 \Rightarrow$  the top decoder is enable and the other is disable.

The bottom decoder outputs are all 0's, and the top eight outputs generate minterms 0000 to 0111.

\* when  $w=1 \Rightarrow$  the enable condition

is reversed, the bottom decoder outputs generate minterms 1000 to 1111.  
So, to connect more standard components, we can use the enable input.

### 4. Combinational logic implementation:

Since, A decoder provides the  $2^n$  minterms of  $n$  input, and any Boolean function can be expressed in sum-of-minterms form, A decoder that generates the minterms of the functions, together with an external OR gate that forms their logical sum, provides a hardware implementation of the function.

In this way, any combinational circuit with  $n$  inputs and  $m$  outputs can be implemented with an  $n$ -to- $2^n$  line decoder and  $m$  OR gates.

The procedure for implementing a combinational circuit by means of decoders and OR gates requires that the Boolean function for the circuit be expressed as a sum of minterms.

### example: implementation a full-adder circuit using decoders:

From the truth table of the full adder, we can obtain the functions for the sum and carry

in sum-of-minterms form:

$$S(x, y, C_{in}) = \sum (1, 2, 4, 7)$$

$$C_{out}(x, y, C_{in}) = \sum (3, 5, 6, 7)$$

We have 3 inputs:  $\Rightarrow$

So, we need a three-to-eight line decoder.

