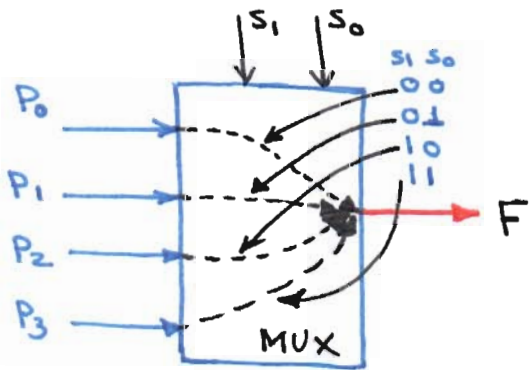


Multiplexers

A multiplexers (MUX) is a combinational logic component that has several inputs and only one output. MUX directs one of the input to its output line by using a control bit word (selection line) to its select lines.


4-to-1 multiplexers

- S_1, S_0 - Select lines.
- P_0, P_1, P_2, P_3 - Input lines.
- F - single output line.




Select lines		output (F)
S_1	S_0	F
0	0	P_0
0	1	P_1
1	0	P_2
1	1	P_3
 
$$F = \bar{S}_1 \bar{S}_0 \cdot P_0 + \bar{S}_1 S_0 P_1 + S_1 \bar{S}_0 P_2 + S_1 S_0 P_3$$




Internal logic circuit for 4-1 MUX

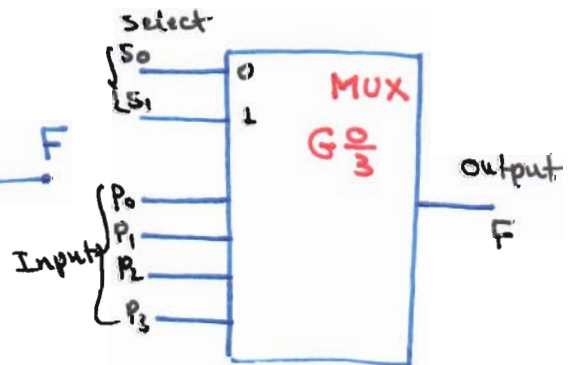

 4:1 MUX module "digital element".

Design of a 8:1 Multiplexer


How to construct a 8:1 MUX from two 4:1 MUX.



X_1 and X_2 are the two output lines of two 4:1 MUX.

$$X_1 = \bar{S}_1 \bar{S}_0 P_0 + \bar{S}_1 S_0 P_1 + S_1 \bar{S}_0 P_2 + S_1 S_0 P_3$$

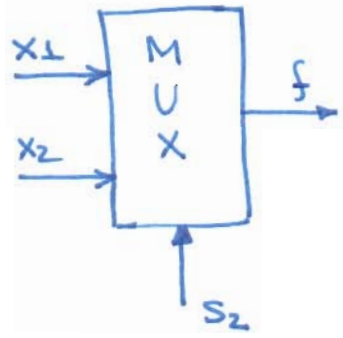
$$X_2 = \bar{S}_1 \bar{S}_0 P_0 + \bar{S}_1 S_0 P_1 + S_1 \bar{S}_0 P_2 + S_1 S_0 P_3$$



$$f = \bar{S}_2 X_1 + S_2 X_2$$

The multiplexer sometime is called Data Selector

A Design for a 8:1 MUX Network.

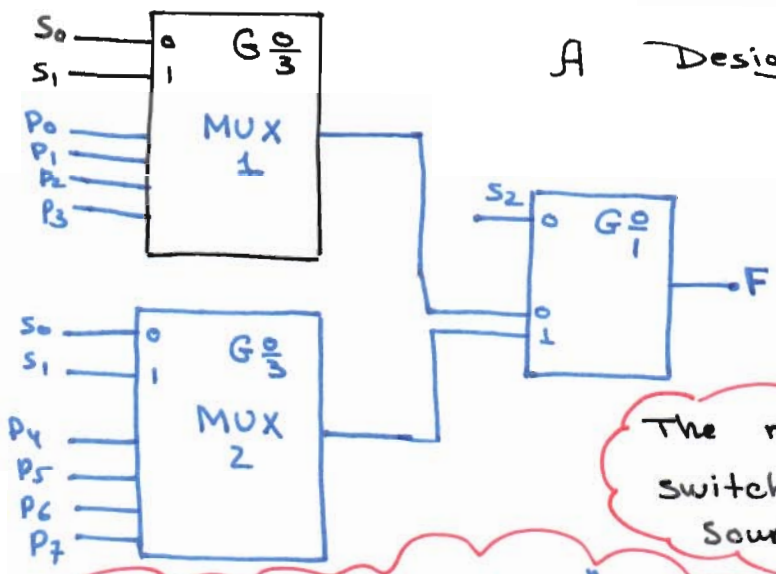

: n - select lines : S_0, S_1, S_2
 $2^n : 1 \rightarrow$ MUX.


The multiplexer acts like an electronic switch that selects one from different sources.

* Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected.

A multiplexer may have an enable input to control the operation of the unit.


Demultiplexers.

 The demultiplexer is a combinational logic circuit that performs the reverse operation of multiplexer. (Several output lines, one input line).




③

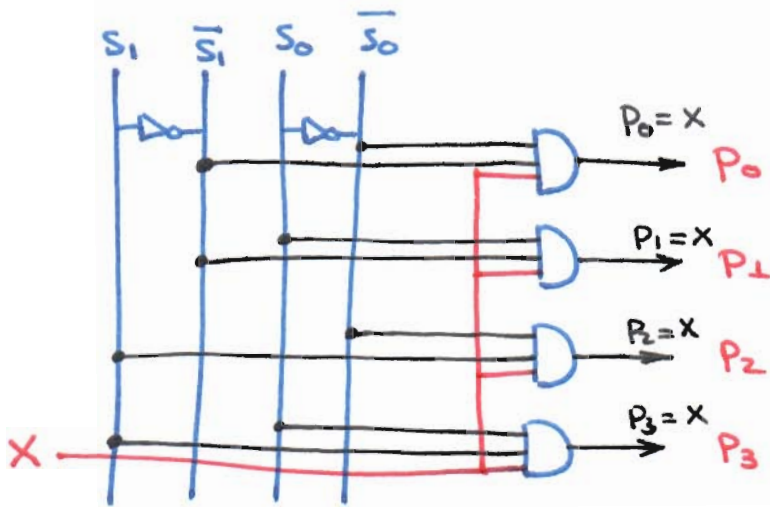Internal logic circuit for 1:4 demultiplexer



Explain:

 

Inputs		output
X	c	
0	0	0
0	1	0
1	0	0
1	1	1

when c=1 we get F=X

Two Select lines \Rightarrow four outputs

$\bar{S}_1 \bar{S}_0 = 00 \Rightarrow P_0 = X$

$S_1 \bar{S}_0 = 01 \Rightarrow P_1 = X$

$\bar{S}_1 S_0 = 10 \Rightarrow P_2 = X$

$S_1 S_0 = 11 \Rightarrow P_3 = X$

Encoders

An encoder is a digital circuit that performs the inverse operation of a decoder.

An encoder has 2^n (or fewer) input lines and n output lines.

Inputs								outputs		
D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	X	Y	Z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

Truth table of an Octal-to-Binary Encoder

The encoder can be implemented with ⁽⁴⁾ OR gates whose inputs are determined directly from the truth table.


* output Z is equal to 1 when the input digit is 1, 3, 5 or 7.

$$Z = D_1 + D_3 + D_5 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$X = D_4 + D_5 + D_6 + D_7$$

We need three OR gates

 

End of Part 2
