

1. Analysis with D Flip-flop.

Example: Consider the following equation (input equation) for D flip-flop.

$$D_A = A \oplus x \oplus y$$

Where: D_A - D flip-flop with output A.
 x and y are the inputs to the circuit.


Do the following:

- Draw the sequential circuit
- Construct the state table.
- Construct the state diagram.

Solution:

- No output equations are given.

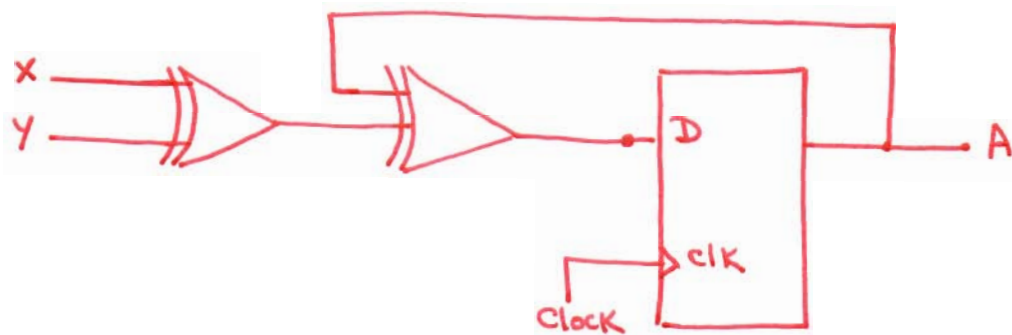a- The logic diagram is obtained from the input equation.



b- The state table has one column for the present state of flip-flop A, two columns for two inputs and one column for the next state.

The next state values are obtained from the state equation: $A(t+1) = A \oplus x \oplus y$

State table

Present State A	Inputs		Next State $A(t+1)$
	x	y	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



* A slash on the directed line is not needed because NO output from a combinational circuit.

* Two inputs \rightarrow four combinations

* one flip-flop \rightarrow Two combination

2. Analysis with JK Flip-flops.

(2)

State table consists of: present state, inputs, next state and outputs.

The output section is determined from the output equation.

The next state values are evaluated from the state equations.

* For D type: the equation is the same as the input equation.


When a flip-flop other than the D type is used, such as JK or T, it is necessary to refer to the corresponding characteristics table or characteristic equation to obtain the next-state values.

The next-state values for JK or T or SR Types can be derived as follows:

1. Determine the input equations (for flip-flop)
2. List the binary values.
3. Use characteristics table to determine the next-state values.

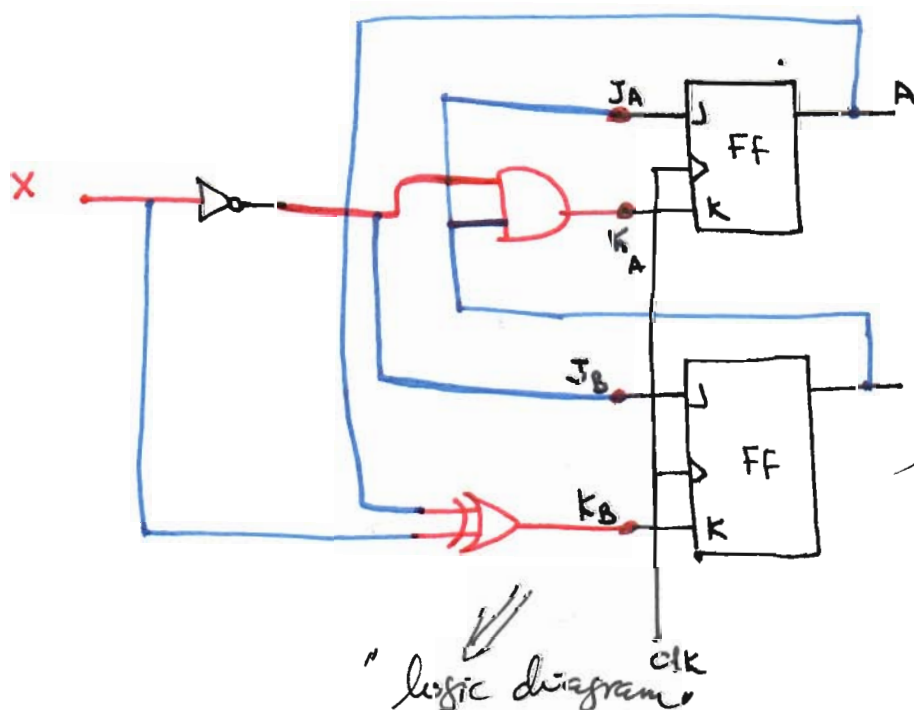example:

Consider the sequential circuit with two JK flip-flops A and B and one input X, the circuit has no outputs. (the state table does not need output column)



Input Equations:

$$\begin{aligned} J_A &= B \\ K_A &= B \cdot \bar{X} \end{aligned} \quad \left. \vphantom{\begin{aligned} J_A &= B \\ K_A &= B \cdot \bar{X} \end{aligned}} \right\} \text{Flip-flop A}$$

$$\begin{aligned} J_B &= \bar{X} \\ K_B &= A \oplus X \\ &= A\bar{X} + \bar{A}X \end{aligned} \quad \left. \vphantom{\begin{aligned} J_B &= \bar{X} \\ K_B &= A \oplus X \\ &= A\bar{X} + \bar{A}X \end{aligned}} \right\} \text{Flip-flop B}$$

③

Present state		Input X	Next state		Flip-Flop Inputs			
A	B		A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	1	1	0	0	1	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	1	1
1	1	1	1	1	0	0	0	0

No change
Complement

* The binary values listed under Flip-flop Inputs are not part of the state table.
 ② state table.
 * they are needed to calculate the next state value (step 2 of the procedure)

State table for JK Flip-flops

* The flip-flop inputs values are obtained directly from the input equations.

* The next state of each flip-flop is evaluated from the corresponding j and k inputs and the characteristics table of the JK flip-flop.

② The next-state values can be obtained by evaluating the state equation from the characteristic equation:

Procedure:

- Determine the flip-flop input equations.
- Substitute the input equations into the flip-flop characteristics equation to obtain the state equations.
- Use state equations to determine the next-state values in the state table.

1). $J_A = B$ $K_A = B\bar{X}$
 $J_B = \bar{X}$ $K_B = \bar{A}X + A\bar{X} = A \oplus X$ } input equations.

2) characteristics equations (substitute A or B instead of Q).

$A(t+1) = J\bar{A} + \bar{K}A$ → (for A flip flop)
 $B(t+1) = J\bar{B} + \bar{K}B$ (for B flip flop)

Characteristics equations for A and B flip-flop

substituting the values of J_A and K_A from the input equations, we obtain the state equations for A:


$$A(t+1) = B\bar{A} + (\overline{Bx}) \cdot A = \bar{A}B + A\bar{B} + Ax$$

and for the flip-flop B is:

$$B(t+1) = \bar{x}\bar{B} + (A \oplus x) \cdot B = \bar{B}\bar{x} + ABx + \bar{A}B\bar{x}$$

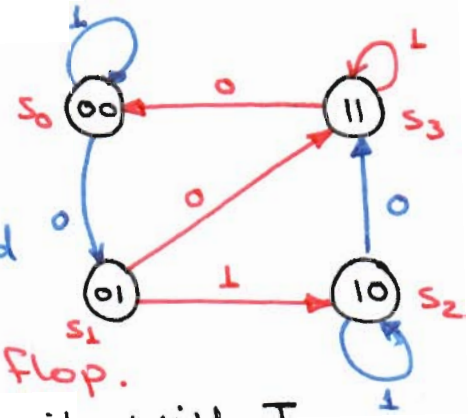3. Calculate the state table values from these equations.

The state diagram of the sequential circuit (Note: the circuit has no outputs, the directed lines marked with one binary number).



3. Analysis with T Flip-Flop.

The analysis of a sequential circuit with T flip-flop follows the same procedure as for JK flip-flops.

The next-state values in the state table can be obtained by using either the characteristics table or characteristic equation

$$Q(t+1) = T \oplus Q = \bar{T}Q + T\bar{Q}$$

example: consider the sequential circuit, with two flip-flops A and B, one input x and one output y, and has the following input equations and an output equation:


$$\begin{aligned} T_A &= Bx \\ T_B &= x \\ y &= AB \end{aligned}$$

Do the following:

1. Draw the logic diagram.
2. construct the state table
3. construct the state diagram.

Solution:

(5)

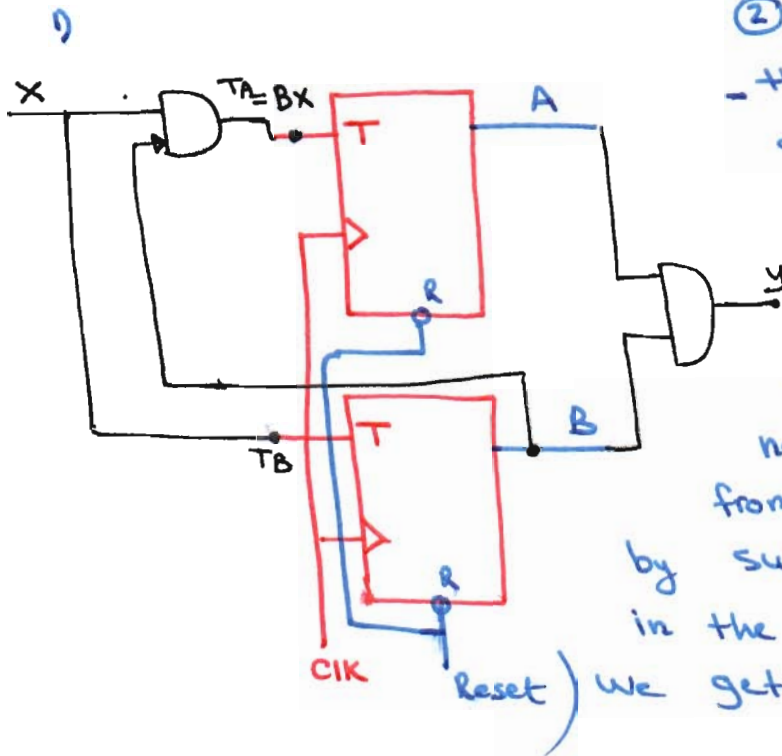

② * the state table:
 - the values of y are obtained from the output equation.


- the values for the next state can be derived from the state equations by substituting T_A and T_B in the characteristic equation, we get:

$$A(t+1) = (\overline{BX})A + (BX) \cdot \overline{A} = \overline{A}\overline{B} + A\overline{X} + \overline{A}BX$$

$$B(t+1) = X \oplus B.$$

Present state		Input X	Next state		output Y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	1

State table

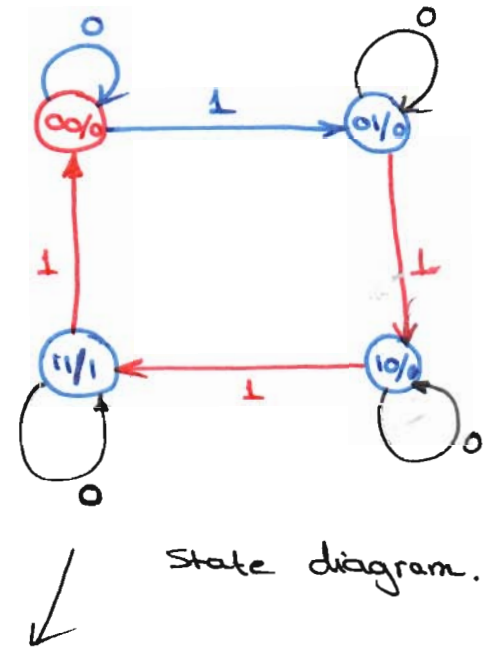

state diagram.


Notes: ● $X=1 \rightarrow$ the

Circuit behaves as a binary counter with sequence of states 00, 01, 10, 11, and back to 00.


- When $X=0 \rightarrow$ the circuit remains in the same state.
- Output y is equal to 1, when the present state is 11

Summary for state diagrams of various Flip-flops.


1. SR flip-flop:

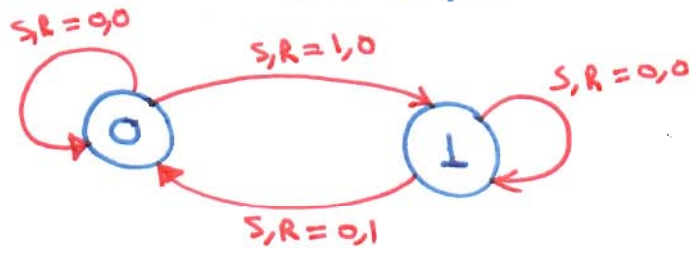


2. JK flip-flop:

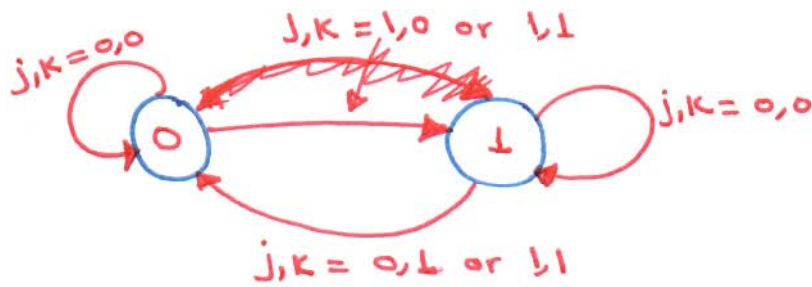

3. D flip-flop:

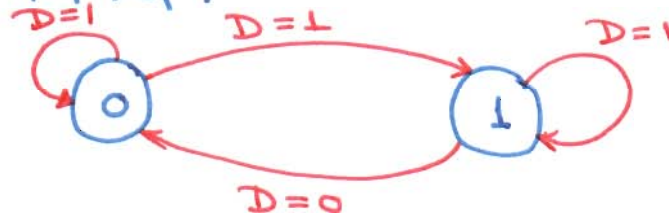


4. T flip-flop:

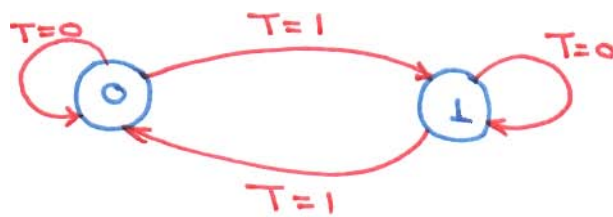

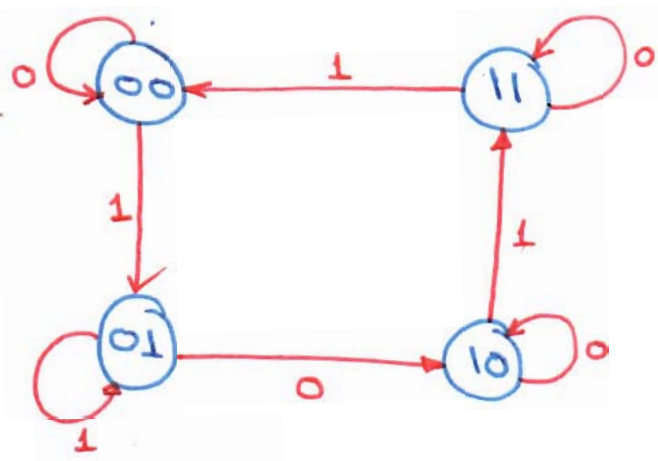Example :

Design a synchronous sequential circuit whose state diagram is shown and the type of flip-flop to be use is j-k.



Solution :

1. from the state diagram, we get state table :

Present state		Next state	
Q ₀	Q ₁	X=0	X=1
		Q ₀ Q ₁	Q ₀ Q ₁
0	0	0 0	0 1
0	1	1 0	0 1
1	0	1 0	1 1
1	1	1 1	0 0

* No output section for this circuit.

table 1

2. Construct the excitation table and the combinational structure.

- Excitation table for jk flip-flop :

* from table 1 and table 2.

Q(t)	Q(t+1)	j	k
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

table 2

Excitation table of the circuit.


Present state		Next state		Input X	Flip-flop Inputs	
Q ₀	Q ₁	Q ₀	Q ₁		J ₀ K ₀	J ₁ K ₁
0	0	0	0	0	0X	0X
0	0	0	1	1	0X	1X
0	1	1	0	0	1X	X1
0	1	0	1	1	0X	X0
1	0	1	0	0	X0	0X
1	0	1	1	1	X0	1X
1	1	1	1	0	X0	X0
1	1	0	0	1	X1	X1

table 3.

from table 3: first row: we have a transition for flip-flop Q₀ from 0 in the present state to 0 in the next state. ⇒ the input of JK as in table must be j=0 and K=X.

The output are j₀, K₀, j₁ and K₁, the inputs are Q₀, Q₁ and X.

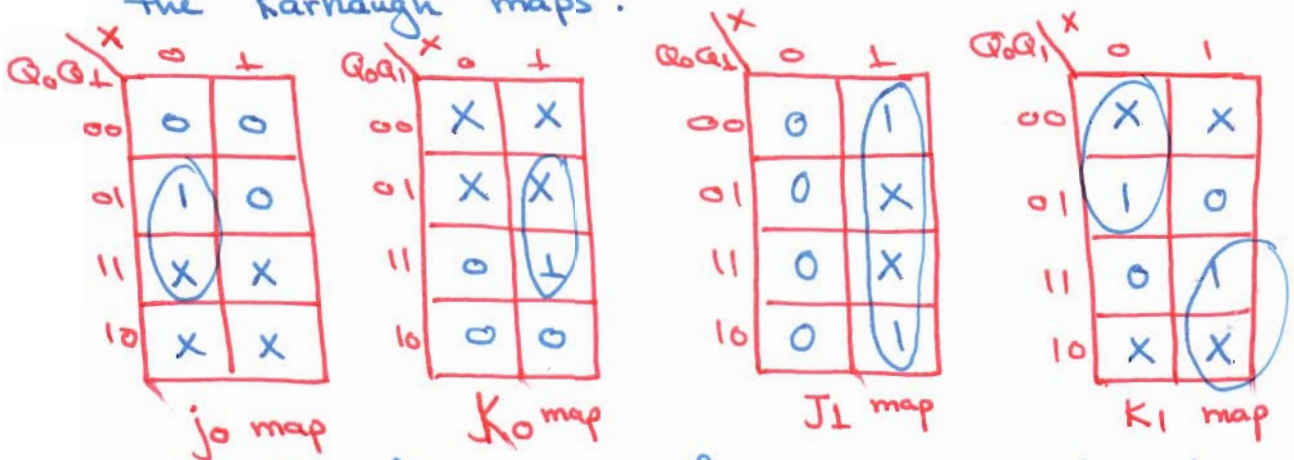* The information from the truth table is plotted on the Karnaugh maps:



The flip-flop input functions are derived:


$$J_0 = Q_1 \cdot \bar{X}$$

$$K_0 = Q_1 \cdot X$$

$$J_1 = X$$

$$K_1 = \bar{Q}_0 \cdot \bar{X} + Q_0 \cdot X = \overline{Q_0 \oplus X}$$

↓
exclusive NOR

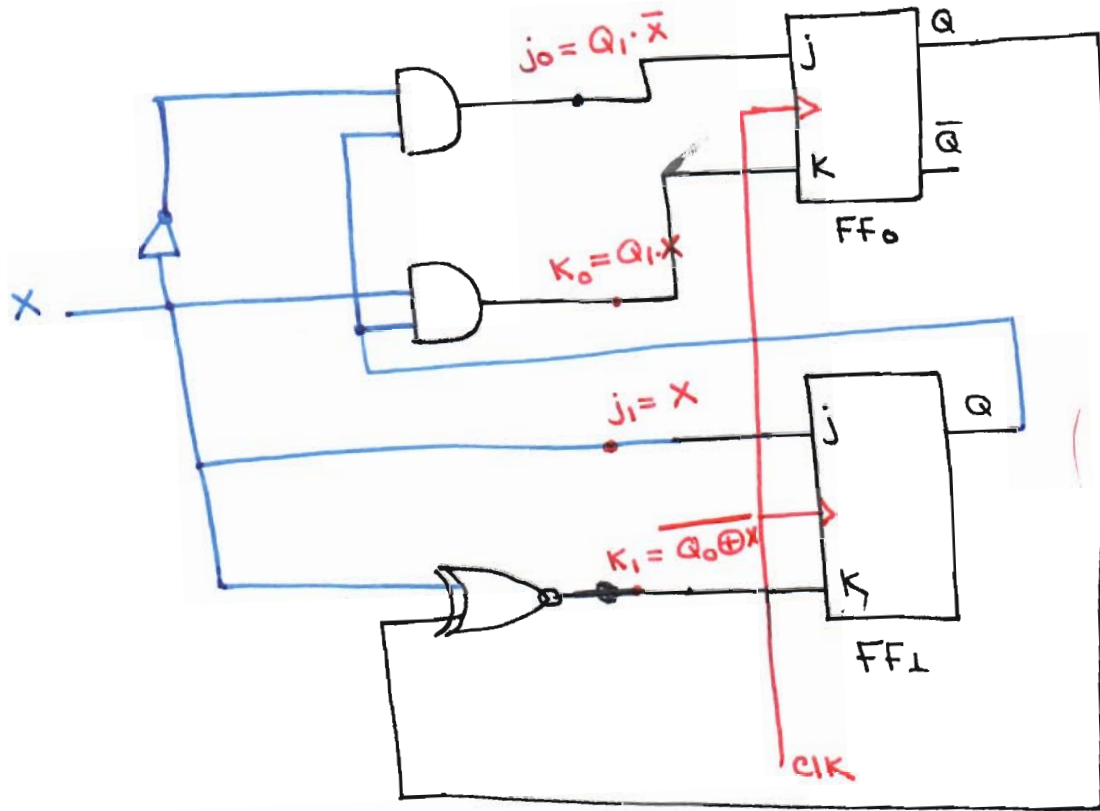

Logic Diagram of the Sequential Circuit.