

Boolean Algebra - I

Objectives:

1. Binary operators and their representations
2. Relationships between Boolean expressions, Truth tables and logic Circuits.
3. Logic Gates' Postulates, Laws and properties.

① Binary Operators and their representations:

Boolean Algebra is the basic mathematics needed for logic design of digital systems, Boolean algebra uses Boolean (logical) variables with two values (0 or 1). "Two-Valued Boolean Algebra".

Basic operations:


The basic operations of Boolean algebra are AND, OR, and NOT (complement).

1. NOT operation (NOT Gate):

$$\bar{I} = 0; \bar{0} = 1.$$

The not operator is also called the complement or the inverse:

\bar{X} is the complement of X .

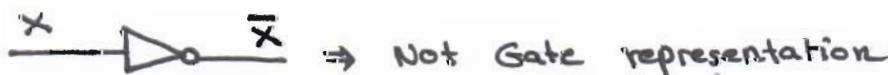

Truth table:

<u>X (input)</u>	<u>\bar{X} (output)</u>
-------------------------------	--------------------------------------

1 - High

0 - Low

0

1

1

0


} . output is opposite of input

Truth table: Truth table describes inputs and outputs in terms of 1s and 0s rather than physical (voltage) levels.

2. AND operation (AND Gate):

the output is 1 only if all inputs are 1, if any of the input is (0), then the output is 0.

Inputs

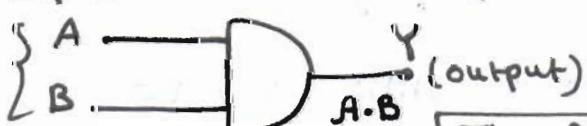

The truth table of 2-inputs, 1-output


AND Gate:

The AND operation is referred to as
Logical multiplication

Inputs	Output	
A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

3. OR operation (OR Gate)

(2)

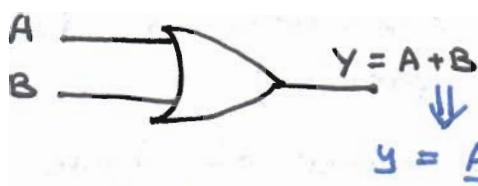

*the output is 1 if


- A is 1 or if
- B is 1

Truth table of OR Gate (2-inputs and 1-output)

Inputs		Output
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

OR operation is sometimes referred to as "inclusive OR" or Logical addition.

4. NAND Gate: (Not AND Gate)

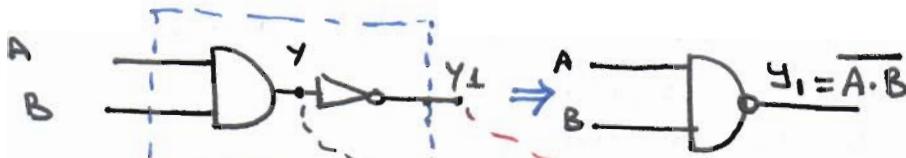


Truth table:

Inputs		Output	
A	B	y	y_1
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

⇒ 2-Inputs NAND = 2-Inputs AND

5. NOR Gate (Not OR):

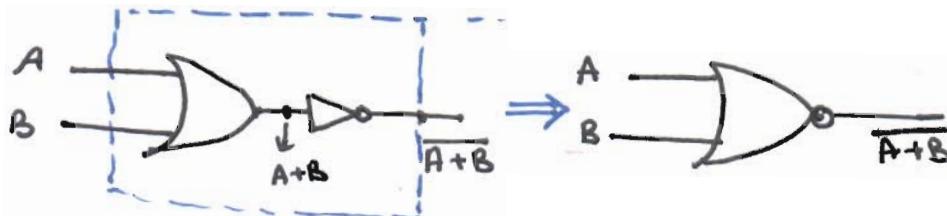


2- Inputs NOR = 2-Inputs OR

Truth table:

Inputs		$A + B$	$\overline{A + B}$
A	B		
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

② Relationships between Boolean expression,
Truth tables and logic circuits.

③

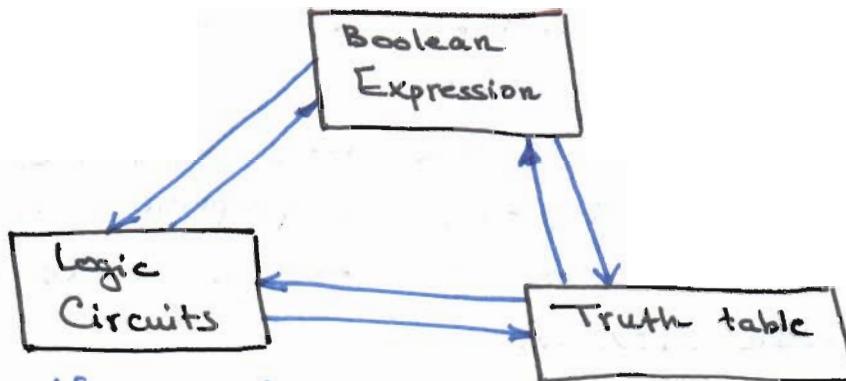

* if one is given, we can get the other.


Example: Boolean Expression \rightarrow logic circuit

To draw a circuit from a boolean expression:

- From the left, make an input line for each variable.
- Next, put a Not gate in for each variable, that appears negated in the expression.
- Still working, from left to right.

Examples:


① $z = A \cdot \bar{B}$

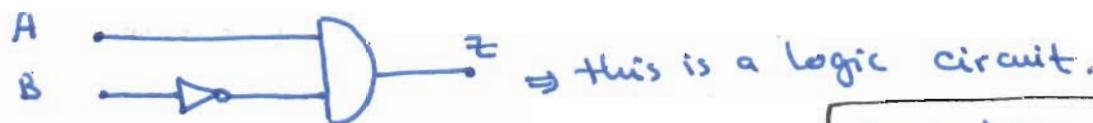

② Example 2:

$$A \cdot \bar{B} + (A + B) \cdot B$$

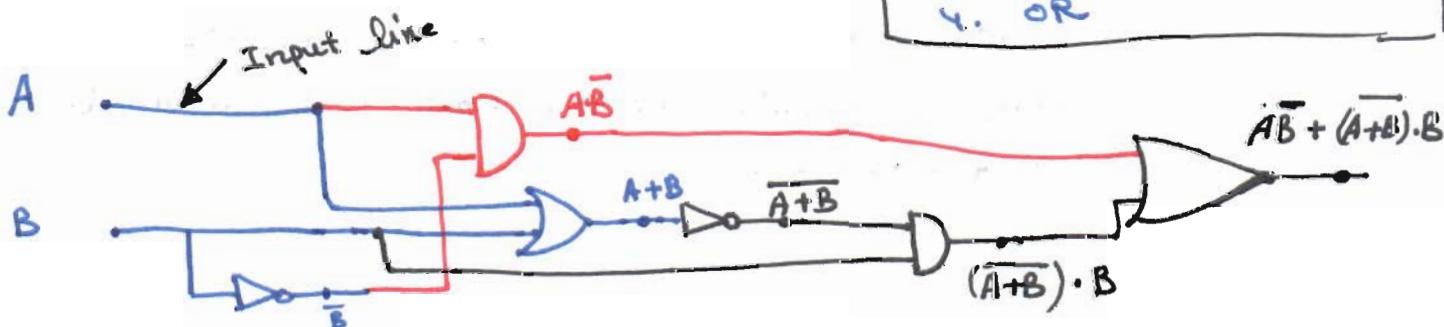precedence of operators:
1. parentheses.
2. Not
3. AND
4. OR



4

3. Logic Gates' postulates, laws and properties.

postulates are used to deduce the rules, theorems and properties.

L. postulates of Boolean Algebra :

$$P_1: A + 0 = A \Rightarrow A \cdot 1 = A$$

$$P_2: A + \bar{A} = 1 \Rightarrow A \cdot \bar{A} = 0$$

$$P_3: A + B = B + A \Rightarrow A \cdot B = B \cdot A$$

$$P_4: A \cdot (B + C) = A \cdot B + A \cdot C \Rightarrow A + BC = (A + B)(A + C)$$

Duality principle

Duality principle states that every algebraic expression is deducible if the operators and the identity elements are interchanged.

Identity elements : 0 for or
1 for and

2. Boolean Algebra Theorems:

There are six theorems of Boolean Algebra

T1: Idempotent Laws:

$$a) A + A = A \xrightarrow{\text{duality}} b) A \cdot A = A$$

T2: operations with 0 and 1

$$a) A + 1 = 1 \xrightarrow{\text{duality}} b) A \cdot 0 = 0$$

T3: Involution Law:

$$\bar{\bar{A}} = A$$

T4: Associative Laws:

$$a) A + (B + C) = (A + B) + C \rightarrow b) A \cdot (B \cdot C) = (A \cdot B) \cdot C$$

T5: De Morgan Laws (Inversion Law)

$$a) \overline{A+B} = \bar{A} \cdot \bar{B} \rightarrow b) \overline{AB} = \bar{A} + \bar{B}$$

T6: Absorption Laws:

$$a) A + AB = A \rightarrow b) A(A + B) = A$$

first way: Theorems of Boolean Algebra can be shown to hold by means of Truth table.

Example

A	B	AB	<u>$A + AB$</u>
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

$$\Rightarrow \underline{A + AB = A}$$

Example 2: Verify the DeMorgan's Law using a truth table. ⑤

\bar{x}	\bar{y}	\bar{x}'	\bar{y}'	$\bar{x} + \bar{y}$	$\bar{\bar{x} + \bar{y}}$	$\bar{x} \cdot \bar{y}'$	$\bar{x}' \cdot \bar{y}$	$\bar{x} \cdot \bar{y}$	$\bar{\bar{x} \cdot \bar{y}}$
0	0	1	1	0	1	0	0	0	1
0	1	1	0	1	0	0	0	0	1
1	0	0	1	1	0	0	0	1	0
1	1	0	0	1	0	1	1	0	0

$\bar{x} + \bar{y} = \bar{x} \cdot \bar{y}'$

$\bar{x} \cdot \bar{y}' = \bar{x} + \bar{y}$

Some details: \Rightarrow

- The duality principle is formed by replacing AND with OR, OR with AND, 0 with 1, 1 with 0, variables and complements are left unchanged.
- DeMorgan's Laws:
allow us to convert between types of gates; we can generalize them to n variables:

$$\begin{aligned} (x_1 + x_2 + x_3 + \dots + x_n) &= \bar{x}_1 \cdot \bar{x}_2 \cdot \bar{x}_3 \cdot \dots \cdot \bar{x}_n \\ \underline{(x_1 x_2 x_3 \dots x_n)} &= \bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \dots + \bar{x}_n \end{aligned}$$

↓ the right side.

they are equal.

Second Way: algebraically using the basic theorems.

Examples:

a) $A + AB = A$ b) $A(A+B) = A$

Proof (a):

$$A + AB = A \cdot 1 + AB = A(1 + B) = A \cdot 1 = A$$

Proof (b):

$$A(A+B) = A \rightarrow \text{by duality.}$$

Examples:


(6)

1) $(A\bar{B} + D)E + 1 = 1$

2) $(A\bar{B} + D) \cdot \overline{(A\bar{B} + D)} = 0$

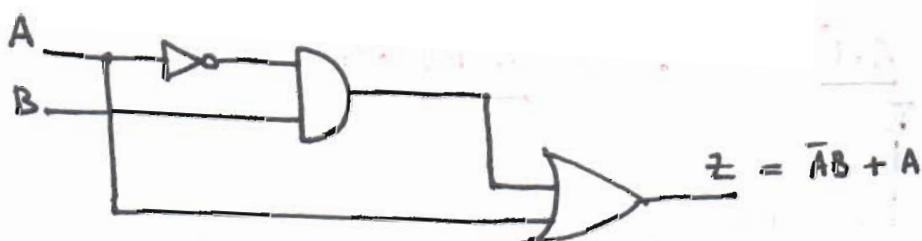- 3) An input A is inverted and applied to an AND Gate. The other input is B. The output of the AND gate is applied to an OR gate. A is the second input to OR gate.

Draw the logic circuit and the truth table.



truth table

A	B	Z
0	0	0
0	1	1
1	0	1
1	1	1

OR Gate

- 4) Proof the following Boolean Expression
"Theorems"

a) $X + XY = X$

Proof: $X + XY = X \cdot 1 + XY = X(1+Y) = X \cdot 1 = X$

b) $X(X+Y) = X$

Proof:

$$X(X+Y) = X \cdot X + X \cdot Y = X + XY = X(1+Y) = X \cdot 1 = X$$

c) $X\bar{Y} + Y = X + Y$

$$X\bar{Y} + Y = Y + X\bar{Y} = (Y+X)(Y+\bar{Y}) = (Y+X) \cdot 1 = Y+X$$

home work:

Proof the following theorems:

1. $XY + X\bar{Y} = X$

2. $(X+Y)(X+\bar{Y}) = X$

3. $(X+\bar{Y})Y = XY$.