

Simplifying Logic Circuit

①

Objectives:

1. Deriving of logical expression from truth tables
2. Logical Expression Simplification methods
 - 2.1. Algebraic manipulation
 - 2.2. Karnaugh map (K-map)

① Deriving of logical expression from truth tables

Definitions:

- literal: non-complemented or complemented version of a variable (A or \bar{A})
- product term: A series of literals related to one another through the AND operator (example: $A \cdot \bar{B} \cdot C$)
- sum term: A series of literals related to one another through the OR operator. (Ex: $A + B + \bar{C}$)
- SOP: (sum-of-products) form:

The logic-circuit simplification require the logic expression to be in SOP form, for example:

$$AB + \bar{A}\bar{B}\bar{C} + \bar{C}\bar{D} : \Rightarrow$$

- POS form (product-of-sum):

This form sometimes used in logic circuit, example:

$$(A + C) \cdot (C + \bar{D}) \cdot (\bar{B} + C)$$

The methods of circuit simplification and design that will be used are based on the SOP form.

- Canonical and standard form

- Product terms that consist of the variables of function are called "canonical product terms" or "minterms".

The term ABC is a minterm in a three variable logic function, but will be a non-minterm in a four variable logic function.

- Sum terms which contain all the variables of a Boolean function are called "canonical sum terms" or "Maxterms"

Example: $A + \bar{B} + C \rightarrow$ maxterm in a three variable logic function.

- For two variables A and B, there are four combination: $\bar{A}\bar{B}$, $\bar{A}B$, $A\bar{B}$, AB called minterm or standard product. (2)

<u>A</u>	<u>B</u>	
0	0	$\bar{A}\bar{B}$
0	1	$\bar{A}B$
1	0	$A\bar{B}$
1	1	AB

- For n variables there are 2^n minterms.

Example: Minterms for 3 variables:

A	B	C	Minterm	Designation	Maxterm	Designation
0	0	0	$\bar{A}\bar{B}\bar{C}$	m_0	$A+B+C$	M_0
0	0	1	$\bar{A}\bar{B}C$	m_1	$A+B+\bar{C}$	M_1
0	1	0	$\bar{A}BC$	m_2	$A+\bar{B}+C$	M_2
0	1	1	$A\bar{B}C$	m_3	$A+\bar{B}+\bar{C}$	M_3
1	0	0	$A\bar{B}\bar{C}$	m_4	$\bar{A}+B+C$	M_4
1	0	1	$A\bar{B}C$	m_5	$\bar{A}+B+\bar{C}$	M_5
1	1	0	ABC	m_6	$\bar{A}+\bar{B}+C$	M_6
1	1	1	$A\bar{B}C$	m_7	$\bar{A}+\bar{B}+\bar{C}$	M_7

Two important properties:

1. Any Boolean function can be expressed as a sum of minterms.

2. Any Boolean function can be expressed as a product of maxterms.

Example: majority function: (for 3 variables)

Output is one whenever majority of inputs is 1

Final Expression:

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

. SOP form
. Four product terms, because there are 4 rows with a 1 output

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

③

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

. POS form :

four sum terms, 4 rows with 0 output

$$F = (A+B+C) \cdot (A+B+\bar{C}) \cdot (A+\bar{B}+C) \cdot (\bar{A}+\bar{B}+C)$$

Derivation of Logical expression from truth tables "Summary"

- Sum-of-product (SOP) form.
- Product-of-sums (POS) form.
- SOP form:
 - . write an AND term for each input combination that produces a 1 output.
 - . write the variable if its value is 1, complement otherwise
 - . OR the AND terms to get the final expression
- POS form:
 - Dual of the SOP form.

2. Logical Expression Simplification Methods:

Two basic methods :

1. Algebraic manipulation: Use Boolean Laws to simplify the expression: (difficult to use and don't know if you have the simplified form).
2. Karnaugh map (K-map) method
 - Graphical method,
 - easy to use
 - can be used to simplify logical expressions with a few variables.

Algebraic manipulation: ⇒

Example 1: Design a logic circuit that has three inputs, A, B and C and whose output will be High only when a majority of the input are High. (complete Design Procedure)

Solution

Step 1: Set up the truth table
" See previous section"

Step 2: Write the AND term for each case where the output is a 1 : (See previous section)

Step 3: Write the sum-of-products expression for the output

$$F = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Step 4: Simplify the output expression.

- find the common term(s): ABC - common term .
- use the common term (ABC) to factor with other terms .

$$F = \bar{A}BC + ABC + A\bar{B}C + ABC + AB\bar{C} + ABC$$


- Factoring the appropriate pairs of terms :

$$F = BC(\bar{A}+A) + AC(B+\bar{B}) + AB(\bar{C}+C)$$

$$F = BC + AC + AB$$

Step 5: Implement the circuit

for the final expression

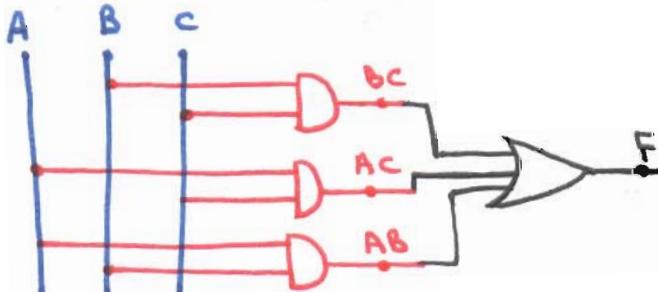

$$\boxed{\begin{aligned} &ABC + ABC + ABC \\ &= ABC \end{aligned}}$$

$$\boxed{A + \bar{A} = 1}$$

Example 2 : Simplify the boolean function

$$F = AB + \bar{A}C + BC$$

Solution: $\bar{A}C$ \rightarrow common term

$$\begin{aligned} F &= AB + \bar{A}C + BC \cdot 1 \\ &= AB + \bar{A}C + BC(A + \bar{A}) \\ &= AB + ABC + \bar{A}C + \bar{A}BC \\ &= AB(1+C) + \bar{A}C(1+B) \\ &= \underline{\underline{AB + \bar{A}C}} \text{ the result.} \end{aligned}$$

Example 3: Simplify the following Boolean function to a minimum number of literals. (5)

$$X = BC + A\bar{C} + AB + BCD$$

Solution:

$$\begin{aligned} X &= BC(1+D) + A\bar{C} + AB \\ &= BC + A\bar{C} + AB \end{aligned}$$

Example 4: Simplify the expression

$$Z = A\bar{B}\bar{C} + A\bar{B}C + ABC$$

Solution: (The expression is in SOP form)

$$\begin{aligned} Z &= A\bar{B}(\bar{C} + C) + ABC \\ &= A\bar{B}(1) + ABC = A\bar{B} + ABC \end{aligned}$$

$$Z = A(\bar{B} + BC) = \underline{A(\bar{B} + C)}$$

Example 5: Simplify

$$Z = \bar{A}C(\bar{\bar{A}}\bar{B}\bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

Solution:

First, use DeMorgan's theorem on the first term

$$Z = \bar{A}C(\bar{\bar{A}} + \bar{B} + \bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$Z = \bar{A}C(A + \bar{B} + \bar{D}) + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

Multiply, we get:

$$Z = \bar{A}CA + \bar{A}CB + \bar{A}CD + \bar{A}B\bar{C}\bar{D} + A\bar{B}C$$

$$\begin{array}{c} \cancel{\bar{A} \cdot A = 0} \\ \Rightarrow \\ Z = \bar{A}\bar{B}C + \bar{A}CD + \bar{A}B\bar{C}\bar{D} + A\bar{B}C \end{array}$$

* Check for the largest common factor between any two or more product terms.

$$\begin{aligned} Z &= \bar{B}C(\bar{A} + A) + \bar{A}\bar{D}(C + B\bar{C}) \\ &\quad \downarrow \qquad \qquad \qquad \downarrow \\ &= \bar{B}C + \bar{A}\bar{D}(B + C) \end{aligned}$$

We get

$$Z = \bar{B}C + \bar{A}\bar{D}(B + C). \quad (\text{The result can be obtained with other choices.})$$

(6)

Example 6 :

Find the complement of the following Boolean function

$$\bar{Z} = (\bar{B}\bar{C} + \bar{A}\bar{D})(\bar{A}\bar{B} + \bar{C}\bar{D})$$

Solution: using DeMorgan's Law:

$$\begin{aligned}\bar{Z} &= \overline{(\bar{B}\bar{C} + \bar{A}\bar{D})(\bar{A}\bar{B} + \bar{C}\bar{D})} = \overline{\underbrace{\bar{B}\bar{C} + \bar{A}\bar{D}}_{F_1}} + \overline{\underbrace{\bar{A}\bar{B} + \bar{C}\bar{D}}_{F_2}} \\ &= \bar{B}\bar{C} \cdot \bar{A}\bar{D} + \bar{A}\bar{B} \cdot \bar{C}\bar{D} \\ &= (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{D}) + (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) \\ &= (\bar{B} + c)(A + \bar{D}) + (\bar{A} + B)(\bar{C} + D)\end{aligned}$$

$$\bar{A} = A$$

It's not in standard form.

Example 7 :

Express the following function in a sum of minterms and product of maxterms.

$$Z = (AB + C)(B + AC)$$

• Sum of minterms:

multiply, we get:

$$Z = ABB + AABC + BC + ACC = AB + \underline{ABC} + BC + AC$$

$$= ABC + AB(c + \bar{c}) + BC(A + \bar{A}) + AC(B + \bar{B})$$

$$= \underline{ABC} + \underline{ABC} + \underline{ABC} + \underline{ABC} + \bar{ABC}$$

$$+ \underline{ABC} + \bar{ABC}$$

the only minterm in equation

$C + \bar{C} = 1$
$B + \bar{B} = 1$
$A + \bar{A} = 1$

$$A + A = A$$

$$Z = ABC + AB\bar{C} + \bar{A}BC + A\bar{B}C$$

$$\downarrow$$

$$\downarrow$$

$$\downarrow$$

$$\downarrow$$

So, we can write:

$$Z(A, B, C) = \sum m(3, 5, 6, 7)$$

• Sum of maxterms

using distributive law

$$(A + BC) \Rightarrow (A + B)(A + C)$$

in the $Z = (AB + C)(B + AC)$
we get:

$$= (A + C)(B + C)(B + A)(\cancel{B + C})$$

$$= (A + B)(B + C)(C + A)$$

A	B	C	min term	Z
0	0	0	$m_0 \rightarrow 0$	0
0	0	1	$m_1 \rightarrow 0$	0
0	1	0	$m_2 \rightarrow 0$	0
0	1	1	$m_3 \rightarrow 1$	1
1	0	0	$m_4 \rightarrow 0$	0
1	0	1	$m_5 \rightarrow 1$	1
1	1	0	$m_6 \rightarrow 1$	1
1	1	1	$m_7 \rightarrow 1$	1

sum of minterms

⊕

$$Z = (A+B)(B+C)(C+A)$$

we need C
we need A we need B

We can write

$$(A+B) = (A+B+0) = (A+B+C\bar{C}) =$$

$(A+B+C)(A+B+\bar{C})$

$$(B+C) = (B+C+0) = \boxed{(B+C+A)(B+C+\bar{A})}$$

$$(C+A) = \boxed{(C+A+B)(C+A+\bar{B})}$$

Substitute all of these terms in Z , we get :

$$Z = (A+B)(B+C)(C+A) = (A+B+C)(A+B+\bar{C})(B+C+A)\cancel{(B+C+A)}(B+C+\bar{A})$$

$(C+A+B)(C+A+\bar{B})$

$$Z = (A+B+C)(A+B+\bar{C})(B+C+\bar{A})(C+A+\bar{B})$$

$$Z = (A+B+C)(A+B+\bar{C}) \leftarrow (A+B+C)(A+\bar{B}+C)$$


\downarrow \downarrow \downarrow \downarrow
M₀ M₁ M₄ M₂

$$Z = M_0 \cdot M_1 \cdot M_4 \cdot M_2$$

A	B	C	max term	Z
0	0	0	M ₀	0
0	0	1	M ₁	0
0	1	0	M ₂	0
0	1	1	M ₃	1
1	0	0	M ₄	0
1	0	1	M ₅	1
1	1	0	M ₆	1
1	1	1	M ₇	1

Sum of maxterms

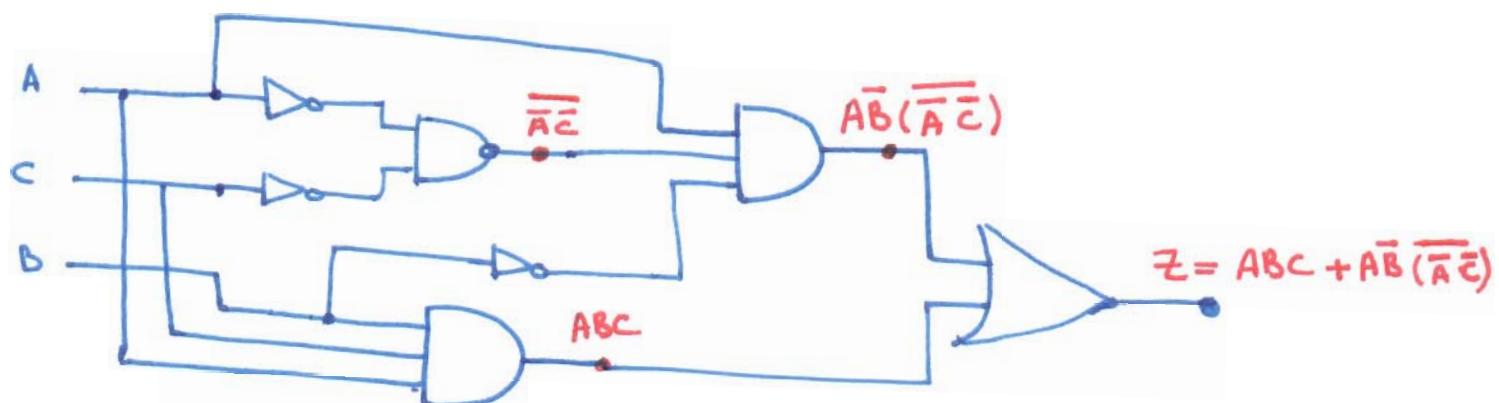Example 8 : Simplify the logic circuit shown in figure.



Solution :

$$Z = ABC + A\bar{B} \cdot (\bar{A}\bar{C}) \Rightarrow \text{using DeMorgan's Law and multiply out all terms :}$$

$$Z = ABC + A\bar{B}(\bar{A} + \bar{C}) \rightarrow \text{"DeMorgan's Law"}$$

$$Z = ABC + A\bar{B}(A + C) \rightarrow \text{"Cancel double inversion"}$$

$$Z = ABC + A\bar{B}A + A\bar{B}C \rightarrow \text{"multiply out"}$$

$$Z = ABC + A\bar{B} + A\bar{B}C \rightarrow \text{"A} \cdot \text{A} = \text{A"}$$

↓

SOP form

$$Z = AC(B + \bar{B}) + A\bar{B} \rightarrow \text{"Common terms and factoring"}$$

$$Z = AC \cdot 1 + A\bar{B} = AC + A\bar{B} = A(C + \bar{B})$$

