

Dept. of Electrical Engineering
First Exam, First Semester: 2017/2018

Course Title: Electrical Machines I

Date: 14/11/2017

Course No: (610314)

Time Allowed: 50 Minutes

Lecturer: Dr. M. Abu-Naser, Dr. F. Obeidat

No. of Pages: 3

Question 1:(5Mark)

Objectives: This question is related to multiple choices

- 1) The basic function of a transformer is to change:
 - a) The level of voltage.
 - b) The power level.
 - c) The frequency.
 - d) The power factor.
- 2) Transformers use laminated core to:
 - a) Reduce eddy current loss.
 - b) Reduce eddy current and hysteresis loss.
 - c) Ensure good magnetic coupling.
 - d) All of the above.
- 3) Transformer action requires
 - a) Constant magnetic flux.
 - b) Increasing magnetic flux.
 - c) Alternating magnetic flux.
 - d) None of the above.
- 4) The leakage flux of primary and secondary windings can be reduced to the minimum by
 - a) Winding primary and secondary coils on separate limbs.
 - b) Winding primary and secondary coils one upon the other coaxially.
 - c) Increase the number of turns.
 - d) Employing low permeability magnetic material core.
- 5) Which of the following windings will be placed nearest to the core of transformer to reduce insulation requirements?
 - a) Primary
 - b) Secondary
 - c) High voltage
 - d) Low voltage

Question 2:

(5Mark)

Objectives: This question is related to open circuit and short circuit tests

A single phase 10 KVA, 500/250V, 50 Hz transformer has the following constants:

primary reactance (X_1) = 0.2 Ω

secondary reactance (X_2) = 0.05 Ω

primary resistance (R_1) = 0.4 Ω

secondary resistance (R_2) = 0.1 Ω

core resistance (R_c) = 1500 Ω

magnetization reactance (X_m) = 750 Ω

What would be the reading of the instruments (wattmeter, voltmeter and ammeter) when the transformer is connected for the open circuit and short circuit tests (both tests are performed from primary side)?

From O.C test

$$I_{mxc} = \frac{V_1}{R_c} = \frac{500}{1500} = \frac{1}{3} \text{ A}$$

$$I_m = \frac{V_1}{X_m} = \frac{500}{750} = \frac{2}{3} \text{ A}$$

$$I_0 = \sqrt{I_{mxc}^2 + I_m^2} = \sqrt{\left(\frac{1}{3}\right)^2 + \left(\frac{2}{3}\right)^2} = 0.745 \text{ A}$$

$$V_{oc} = 500 \text{ V}$$

$$P_{oc} = V_0 I_0 \cos \phi_0 = V_0 I_{mxc} = 500 \times \frac{1}{3} = 166.6 \text{ W}$$

$$V_{oc} = 500 \text{ V}$$

$$I_{oc} = 0.745 \text{ A}$$

$$P_{oc} = 166.6 \text{ W}$$

From S.C test

$$R_{eq} = R_1 + R_2' = R_1 + a^2 R_2$$

$$a = \frac{V_1}{V_2} = \frac{500}{250} = 2$$

$$R_{eq} = 0.4 + 4 \times 0.1 = 0.8 \Omega$$

$$X_{eq} = X_1 + a^2 X_2 = 0.2 + 4 \times 0.05 = 0.4 \Omega$$

$$Z_{eq} = \sqrt{R_{eq}^2 + X_{eq}^2} = \sqrt{(0.8)^2 + (0.4)^2} = \sqrt{0.64 + 0.16} = \sqrt{0.8} = 0.894 \Omega$$

$$I_{sc} = \frac{10000}{500} = 20 \text{ A}$$

$$V_{sc} = I_{sc} Z_{eq} = 20 \times 0.894 = 17.88 \text{ V}$$

$$P_{sc} = I_1^2 R_{eq} = 20^2 \times 0.8 = 320 \text{ W}$$

$$I_{sc} = 20 \text{ A}$$

$$V_{sc} = 17.88 \text{ V}$$

$$P_{sc} = 320 \text{ W}$$

Question 3:

(10Mark)

Objectives: This question is related to transformer performance

A 15-kVA 8000/230-V distribution transformer has impedance referred to the primary of $80 + j300 \Omega$. The components of the excitation branch referred to the primary side are $R_c = 350k\Omega$ and $X_m = 70k\Omega$

- (a) If the primary voltage is 8000 V and the load impedance is $Z_L = 3.2 + j1.5 \Omega$, what is the secondary voltage of the transformer? What is the voltage regulation of the transformer? What is the efficiency?
- (b) If the load is disconnected and a capacitor of $-j3.5 \Omega$ is connected in its place, what is the secondary voltage of the transformer? What is its voltage regulation under these conditions? What is the efficiency?


(a)
$$a = \frac{V_1}{V_2} = \frac{8000}{230} = 34.78$$

$$Z_i = (a)^2 Z_L = (34.78)^2 (3.2 + j1.5) = 3871 + j1815 \Omega$$

$$I_2' = \frac{V_1}{(R_{eq} + jX_{eq}) + (Z_i)}$$

$$= \frac{8000}{80 + j300 + 3871 + j1815}$$
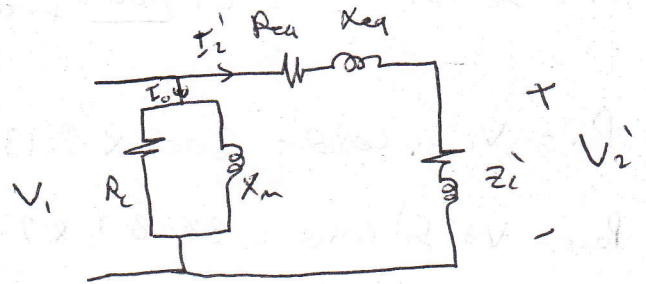
$$= \frac{8000}{4481 \angle 28.2} = 1.78 \angle -28.2 \text{ A}$$



$$V_2' = I_2' Z_i = (1.78 \angle -28.2) \times (3871 + j1815) = 7610 \angle -3.1$$

$$V_2 = \frac{V_2'}{a} = \frac{7610 \angle -3.1}{34.78} = 218.8$$

$$VR = \frac{V_{NL} - V_{FL} \times 100\%}{V_{FL}} = \frac{230 - 218.8}{218.8} \times 100\% = 5.1\%$$

$$Y_m = \frac{1}{R_c} + \frac{1}{jX_m} = \frac{1}{350k} + \frac{1}{j70k} = (2.8 + j14.2) \mu S = 14.5 \angle 78.6 \mu S$$

$$I_0 = V_1 Y_m = 8000 \times 14.5 \times 10^{-6} \angle 78.6 = 0.11 \angle 78.6$$

$$I_1 = I_0 + I_2' = 0.11 \angle 78.6 + 1.78 \angle -28.2 = 1.59 - j0.72 = 1.749 \angle -24.5$$

$$P_{in} = V_1 I_1 \cos \theta = 8000 \times 1.749 \cos(-24.5) = 12732 \text{ W}$$

$$P_{out} = V_2 I_2' \cos \theta = 218.8 \times 1.78 \cos(-28.2 + 3.1) = 12266 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100 = \frac{12266}{12732} \times 100\% = 96.3\%$$

$$b) Z_i = a^2 Z_L = (34.78)^2 (-j3.5) = -j4233.7 \Omega$$

$$I_2 = \frac{V_1}{Z_{eq} + Z_i} = \frac{8000}{80 + j300 - j4233.7} = 0.0413 \times j2.03 = 2.03 \angle 88.8$$

$$V_2 = I_2 Z_i = 2.03 \angle 88.8 \times 4233.7 \angle -90 = 8606.5 - j175 = 8608.3 \angle -1.2$$

$$V_2 = \frac{V_2'}{a} = \frac{8608.3 \angle -1.2}{34.78} = 247.4 - j5 = 247.5 \angle -1.2$$

$$VR = \frac{V_{nl} - V_{fl}}{V_{fl}} \times 100\% = \frac{230 - 247.5}{247.5} \times 100\% = -7.07\%$$

$$I_1 = I_0 + I_2' = 2.03 \angle 88.8 + 0.11 \angle 78.6 = 0.064 + j2.13 = 2.13 \angle 88.2$$

$$P_{in} = V_1 I_1 \cos \theta = 8000 \times 2.13 \cos 88.2 = 535.2 \text{ W}$$

$$P_{out} = V_2' I_2' \cos \theta = 8608.3 \times 2.03 \cos (88.8 + 1.2) = 0$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = 0\%$$