

Chapter 28

1

Direct Current Circuits

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Circuit Analysis

2

- Simple electric circuits may contain batteries, resistors, and capacitors in various combinations.
- For some circuits, analysis may consist of combining resistors.
- In more complex complicated circuits, Kirchhoff's Rules may be used for analysis.
 - These Rules are based on conservation of energy and conservation of electric charge for isolated systems.

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Direct Current

3

- When the current in a circuit has a constant direction, the current is called **direct current**.
- Because the potential difference between the terminals of a battery is constant, the battery produces direct current.

Electromotive Force

4

- The battery is known as a source of electromotive force (*emf*) (\mathcal{E}).
- The *emf* of a battery is the maximum possible voltage the battery can provide between its terminals.
- The phrase electromotive force is an unfortunate historical term, describing not a force, but rather a potential difference in volts.
- The battery will normally be the source of energy in the circuit.
- The positive terminal of the battery is at a higher potential than the negative terminal.
- We consider the wires to have no resistance.

Internal Battery Resistance

5

• If the internal resistance is zero, the terminal voltage equals the *emf*.

• In a real battery, there is internal resistance, r .


• The terminal voltage:

$$\Delta V = V_d - V_a$$

$$\Delta V = \varepsilon - Ir$$

• The *emf* is equivalent to the *open-circuit* voltage.

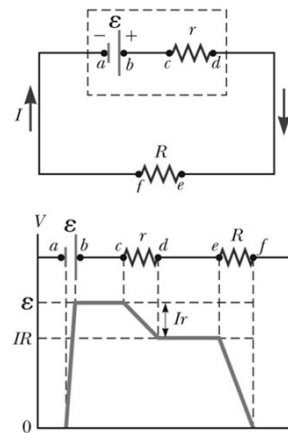- This is the terminal voltage when no current is in the circuit.
- This is the voltage labeled on the battery.



Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Load Resistance

6


• The actual potential difference between the terminals of the battery depends on the current in the circuit.

• The terminal voltage also equals the voltage across the external resistance.

$$\Delta V = V_e - V_f$$

$$\Delta V = IR$$

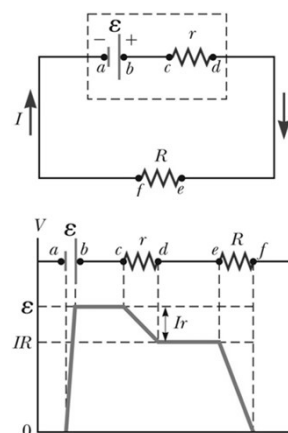- The load resistance is just the external resistor.
- In general, the load resistance could be any electrical device.



Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Current:

7

- The current in this simple circuit:

$$V_e - V_f = V_d - V_a$$


$$IR = \varepsilon - Ir$$

$$I = \frac{\varepsilon}{R+r}$$

- Note that:

$$\Delta V = \varepsilon$$
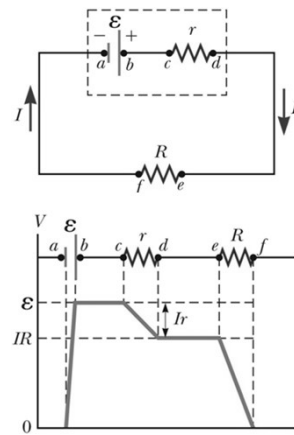
$$I = \begin{cases} I = 0, & \text{open circuit} \\ r = 0, & \text{NO internal resistance} \end{cases}$$



Power

8

- The total power output of the battery is

$$P = I\Delta V = I\varepsilon$$


- This power is delivered to the external resistor (I^2R) and to the internal resistor (I^2r).

$$I\varepsilon = I^2R + I^2r$$

Resistors in Series

9

- When two or more resistors are connected end-to-end, they are said to be in series.
- For a series combination of resistors, the currents are the same in all the resistors because the amount of charge that passes through one resistor must also pass through the other resistors in the same time interval.
- The potential difference will divide among the resistors such that the sum of the potential differences across the resistors is equal to the total potential difference across the combination.

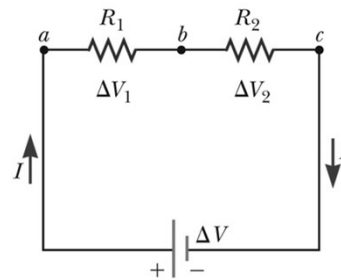

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Resistors in Series, cont

10


- Currents are the same

$$I = I_1 = I_2 = \dots$$

- Potentials add

$$\Delta V = \Delta V_1 + \Delta V_2 + \dots$$

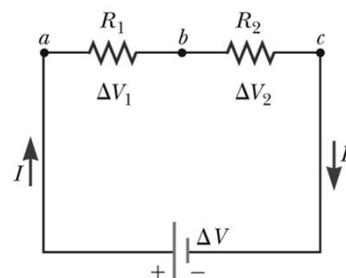- Consequence of **Conservation of Energy**



Mustafa Al-Zyout - Philadelphia University

21-Feb-21


Equivalent Resistance – Series

11

- The equivalent resistance has the same effect on the circuit as the original combination of resistors.

$$R_{eq} = R_1 + R_2 + \dots$$

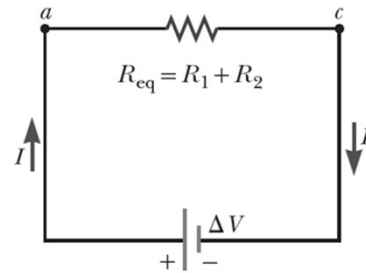- The equivalent resistance of a series combination of resistors is the algebraic sum of the individual resistances.
 - If one device in the series circuit creates an open circuit, all devices are inoperative.
- The equivalent is **always larger than** the largest resistor in the group.



Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Resistors in Parallel

12


- The potential difference across each resistor is the same because each is connected directly across the battery terminals.

$$\Delta V = \Delta V_1 = \Delta V_2 = \dots$$

- A **junction** is a point where the current can split.
- The current, I , that enters junction must be equal to the total current leaving that junction.

$$I = I_1 + I_2 + \dots$$

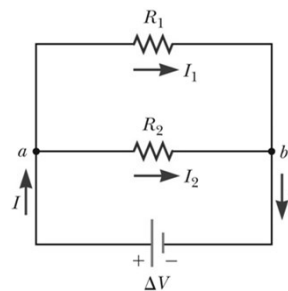- The currents are generally not the same.
- Consequence of **conservation of electric charge**



Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Equivalent Resistance – Parallel


13

- Equivalent Resistance.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

- The inverse of the equivalent resistance of two or more resistors connected in parallel is the algebraic sum of the inverses of the individual resistance.

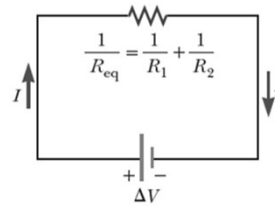- The equivalent **is always less than** the smallest resistor in the group.



Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Resistors in Parallel, Final

14

- In parallel, each device operates independently of the others so that if one is switched off, the others remain on.
- In parallel, all of the devices operate on the same voltage.
- The current takes all the paths.
 - The lower resistance will have higher currents.
 - Even very high resistances will have some currents.
- Household circuits** are wired so that electrical devices are connected in **parallel**.

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Kirchhoff's Rules

15

There are ways in which resistors can be connected so that the circuits formed cannot be reduced to a single equivalent resistor.

Two rules, called Kirchhoff's rules, can be used instead.

Kirchhoff's Junction Rule

16

• **Junction Rule: the sum of the currents at any junction must equal zero.**

Currents directed into the junction are entered into the equation as $(+I)$ and those leaving as $(-I)$.


A statement of **Conservation of Charge**

Mathematically,

$$\sum_{\text{junction}} I = 0$$

In the figure:

$$I_1 - I_2 - I_3 = 0$$

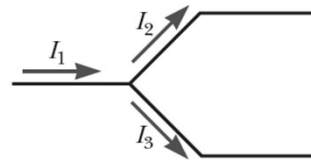

Kirchhoff's Loop Rule

17

- Loop Rule

- The sum of the potential differences across all elements around any closed circuit loop must be zero.
- ✱ A statement of **Conservation of Energy**

- Mathematically,

$$\sum_{\text{closed loop}} \Delta V = 0$$

More about the Loop Rule

18

- ❖ **Traveling from a to b:**



- In (a), the resistor is traversed in the direction of the current, the potential across the resistor is

$$\Delta V = V_b - V_a = -IR$$

- ❖ **Traveling from a to b:**

- In (b), the resistor is traversed in the direction opposite of the current, the potential across the resistor is:

$$\Delta V = V_b - V_a = +IR$$

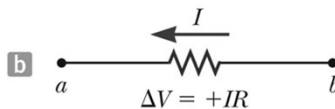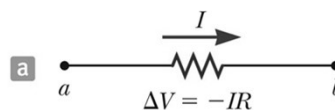

Loop Rule, final

19

•**Traveling from a to b:**



•In (c), the source of emf is traversed in the direction of the emf (from $-$ to $+$), and the change in the potential difference is

$$\Delta V = V_b - V_a = \mathcal{E}$$

•**Traveling from a to b:**

•In (d), the source of emf is traversed in the direction opposite of the emf (from $+$ to $-$), and the change in the potential difference is

$$\Delta V = V_b - V_a = -\mathcal{E}$$

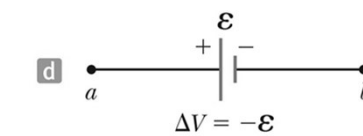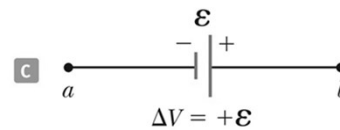


RC Circuits

20

In direct current circuits containing capacitors, the current may vary with time.

The current is still in the same direction.

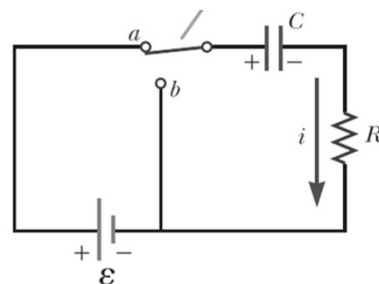An RC circuit will contain a series combination of a resistor and a capacitor.



Charging a Capacitor

21

- When the circuit is completed, the capacitor starts to charge.
- At the instant the switch is closed, the charge on the capacitor is zero.
- The capacitor continues to charge until it reaches its maximum charge ($Q = C\mathcal{E}$).
- Once the capacitor is fully charged, the current in the circuit is zero.
- As the plates are being charged, the potential difference across the capacitor increases, such that:

$$\mathcal{E} = V_C + V_R$$


Mustafa Al-Zyout - Philadelphia University

21-Feb-21

22

Charging a Capacitor

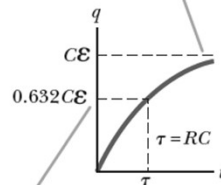
The charge approaches its maximum value $C\mathcal{E}$ as t approaches infinity.



After a time interval equal to one time constant τ has passed, the charge is 63.2% of the maximum value $C\mathcal{E}$.

a

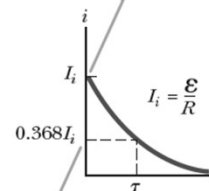The current has its maximum value $I_i = \mathcal{E}/R$ at $t = 0$ and decays to zero exponentially as t approaches infinity.



After a time interval equal to one time constant τ has passed, the current is 36.8% of its initial value.

b

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Time Constant

23

τ is the *time constant*

$$\tau = RC$$

The time constant represents the time required for the charge to increase from zero to 63.2% of its maximum.

τ has units of time (s)

Charging a Capacitor, Equations

24

When the circuit is completed, the capacitor starts to charge. At the instant the switch is closed ($t = 0 \text{ s}$)

The **charge** on the **capacitor** is **zero**:

$$\bullet Q_C = 0$$

The **potential** difference across the **capacitor** is **zero**:

$$\bullet V_C = 0$$

The **potential** difference across the **resistor** is **maximum**:

$$\bullet V_R = \varepsilon$$

The **current** in the circuit is **maximum**:

$$\bullet I_{max.} = \frac{\varepsilon}{R}$$

Charging a Capacitor , Equations

(25)

After a very long time ($t \rightarrow \infty$),

the **charge** on the **capacitor** is **maximum**:

$$\bullet Q_{max.} = C \varepsilon$$

The **potential** difference across the **capacitor** is **maximum**:

$$\bullet V_C = \varepsilon$$

The **potential** difference across the **resistor** is **zero**:

$$\bullet V_R = 0$$

The **current** in the circuit is **zero**:

$$\bullet I = 0$$

The **energy** stored in the capacitor is **maximum**:

$$\bullet U_{max.} = \frac{1}{2} Q \varepsilon = \frac{1}{2} C \varepsilon^2$$

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Charging a Capacitor , Equations

(26)

While charging the capacitor ($0 < t < \infty$),

The **charge** on the **capacitor** **increases** with time:

$$\bullet Q(t) = Q_{max.} (1 - e^{-\frac{t}{\tau}})$$

The **potential** difference across the **capacitor** **increases** with time:

$$\bullet V_C(t) = \varepsilon (1 - e^{-\frac{t}{\tau}})$$

The **energy** stored in the **capacitor** **increases** with time:

$$\bullet U(t) = U_{max.} (1 - e^{-\frac{2t}{\tau}})$$

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Charging a Capacitor , Equations

27

The **potential** difference across the **resistor** decreases with time:

$$\bullet V_R(t) = \varepsilon e^{-\frac{t}{\tau}}$$

The **current** in the circuit decreases with time:

$$\bullet I(t) = I_{max} e^{-\frac{t}{\tau}}$$

Discharging a Capacitor

28


- Imagine that the capacitor in the figure shown is completely charged.
- The initial potential difference across the capacitor is:

$$V_C = \frac{Q_i}{C}$$

- There is zero potential difference across the resistor because $i = 0$.

$$V_R = 0$$


$$I = 0$$

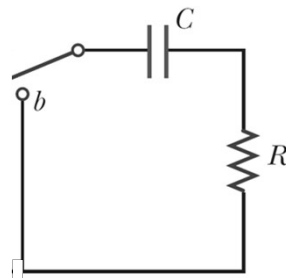

Discharging a Capacitor

29

- When the switch is closed, charge begins to flow through resistor R from the right side of the capacitor toward the left side, until the capacitor is fully discharged.
- The voltage across the resistor at any instant **equals** that across the capacitor.
- At some time t during the discharge, the current in the circuit is $I(t)$ and the charge on the capacitor is $Q(t)$.
- As the capacitor discharges, the current direction is opposite its direction when the capacitor was being charged.


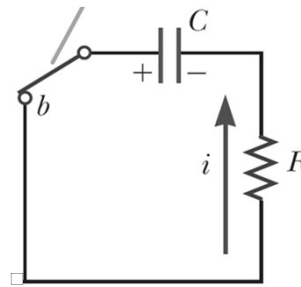


Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Discharging a Capacitor

30

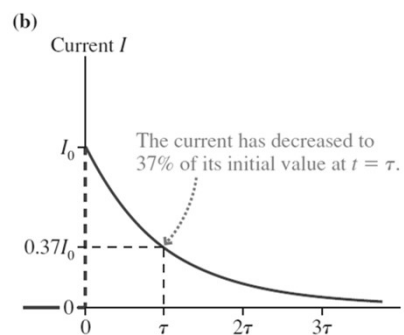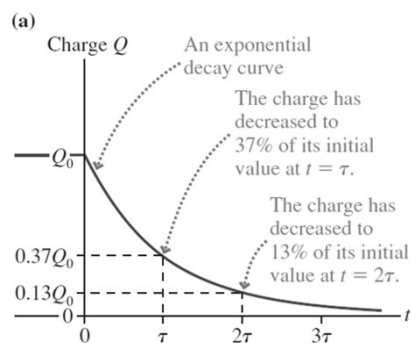

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Discharging a Capacitor , Equations

31

When the capacitor starts to discharge. At the instant the switch is closed ($t = 0 \text{ s}$)

The **charge** on the **capacitor** is **maximum**:

$$\bullet Q_C = Q_{max.}$$

The **potential** difference between the plates of the **capacitor** is **maximum**:

$$\bullet V_C = \frac{Q_{max.}}{C}$$

The **potential** difference between the ends of the **resistor** is **maximum**:

$$\bullet V_R = V_C = \frac{Q_{max.}}{C}$$

The **current** in the circuit is **maximum**:

$$\bullet I_{max.} = \frac{V_R}{R} = \frac{Q_{max.}}{RC}$$

The **energy** stored in the capacitor is **maximum**:

$$\bullet U_{max.} = \frac{Q^2}{2C}$$

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Discharging a Capacitor , Equations

32

After a very long time ($t \rightarrow \infty$),

The **charge** on the **capacitor** is **zero** :

$$\bullet Q = 0$$

The **potential** difference between the plates of the **capacitor** is **zero** :

$$\bullet V_C = 0$$

The **potential** difference between the ends of the **resistor** is **zero**:

$$\bullet V_R = 0$$

The **current** in the circuit is **zero**:

$$\bullet I = 0$$

The **energy** stored in the capacitor is **zero** :

$$\bullet U = 0$$

Mustafa Al-Zyout - Philadelphia University

21-Feb-21

Discharging a Capacitor , Equations

33

While discharging the capacitor ($0 < t < \infty$),

The **charge** on the **capacitor** decreases with time:

$$\bullet q(t) = Q_{max} \cdot e^{-\frac{t}{\tau}}$$

The **potential** difference between the plates of the **capacitor** decreases with time:

$$\bullet V_C(t) = \frac{Q_{max}}{C} \cdot e^{-\frac{t}{\tau}}$$

The **energy** stored in the **capacitor** decreases with time:

$$\bullet U(t) = \frac{Q^2}{2C} e^{-\frac{2t}{\tau}}$$

Discharging a Capacitor , Equations

34

The **potential** difference between the ends of the **resistor** decreases with time:

$$\bullet V_R(t) = \frac{Q_{max}}{C} \cdot e^{-\frac{t}{\tau}}$$

The **current** in the circuit **decreases** with time:

$$\bullet I(t) = \frac{Q_{max}}{RC} \cdot e^{-\frac{t}{\tau}}$$